

Topic :- Alternating current

1 (b)

$$e = 300\sqrt{2} \sin \omega t$$

$$I_0 = \frac{e_0}{Z} = \frac{300\sqrt{2}}{\sqrt{(30)^2 + (10 - 10)^2}}$$
$$\{ \because Z = \sqrt{R^2 + (X_L - X_C)^2} \}$$
$$= \frac{300\sqrt{2}}{30} = 10\sqrt{2} \text{ A}$$

$$\therefore \text{Current } I = \frac{I_0}{\sqrt{2}} = 10 \text{ A}$$

2 (a)

Natural frequency is nothing but resonant frequency.

In this case $X_L = X_C$

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

3 (a)

At angular frequency ω , the current in RC circuit is given by

$$i_{rms} = \frac{V_{rms}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \quad \dots(i)$$

$$\text{Also } \frac{i_{rms}}{2} = \frac{V_{rms}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = \frac{V_{rms}}{\sqrt{R^2 + \frac{9}{\omega^2 C^2}}} \dots \text{(ii)}$$

From equation (i) and (ii), we get

$$3R^2 = \frac{5}{\omega^2 C^2} \Rightarrow \frac{1}{\omega C} = \sqrt{\frac{3}{5}} \Rightarrow \frac{X_C}{R} = \sqrt{\frac{3}{5}}$$

4 **(d)**

$$\text{Resistance of coil } (R) = \frac{200}{1} = 200 \Omega$$

$$\text{Current, } I = \frac{200}{\sqrt{R^2 + X_L^2}}$$

$$\text{or } 0.5 = \frac{200}{\sqrt{R^2 + X_L^2}}$$

$$\text{or } R^2 + (2\pi fL)^2 = (400)^2$$

$$\text{or } \left(2\pi f \times \frac{2\sqrt{3}}{\pi}\right)^2 = (400)^2 - (200)^2$$

$$= 120000$$

$$\text{or } 4f\sqrt{3} = 200\sqrt{3}$$

$$\text{or } f = 50 \text{ Hz}$$

5 **(a)**

$\cos \phi = \frac{R}{Z}$. In choke coil $\phi = 90^\circ$ so $\cos \phi \approx 0$

6 **(b)**

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{6} \sqrt{\frac{1}{17.36 \times 10^{-6}}} = 40$$

7 **(a)**

$$P = E_{rms} i_{rms} \cos \phi = \frac{E^2 R}{Z^2} = \frac{E^2 R}{\left[R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2\right]}$$

8 **(b)**

$$R = \frac{P}{i_{rms}^2} = \frac{240}{16} = 15 \Omega; Z = \frac{V}{i} = \frac{100}{4} = 25 \Omega$$

$$\text{Now } X_L = \sqrt{Z^2 - R^2} = \sqrt{(25)^2 - (15)^2} = 20 \Omega$$

$$\therefore 2\pi vL = 20 \Rightarrow L = \frac{20}{2\pi \times 50} = \frac{1}{5\pi} \text{ Hz}$$

9 **(b)**

$$P = \frac{1}{2} V_0 i_0 \cos \phi \Rightarrow P = P_{peak} \cdot \cos \phi$$

$$\Rightarrow \frac{1}{2} (P_{peak}) = P_{peak} \cos \phi \Rightarrow \cos \phi \frac{1}{2} \Rightarrow \phi = \frac{\pi}{3}$$

10 (d)

When a ring moves in a magnetic field in a direction perpendicular to its plane, we replace the ring by a diameter ($2r$) perpendicular to the direction of motion. The emf is induced across this diameter. Current flow in the ring will be through the two semicircular portions in parallel.

$$\text{Induced emf} = B(2r)v.$$

$$\text{Resistance of each half of ring} = R/2$$

As the two halves are in parallel, therefore, equivalent resistance = $R/4$

$$\therefore \text{Current in the section} = \frac{B(2r)v}{R/4}$$

$$I = \frac{8Brv}{R}$$

13 (c)

$$Z = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$

From above equation at $f = 0$, $Z = \infty$

When $f = \frac{1}{2\pi\sqrt{LC}}$ (resonant frequency) $\Rightarrow Z = R$

For $f > \frac{1}{2\pi\sqrt{LC}} \Rightarrow Z$ starts increasing

i.e., for frequency $0 - f_r$, Z decreases and for f_r to ∞ , Z increases

This is justified by graph c

14 (a)

$$X_C = \frac{1}{2\pi\nu C} \Rightarrow \frac{1}{1000} = \frac{1}{2\pi \times \nu \times 5 \times 10^{-6}}$$

$$\Rightarrow \nu = \frac{100}{\pi} \text{ MHz}$$

15 (a)

$$i_{rms} = \frac{i_0}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.536 \text{ A}$$

16 (a)

$$X_L = \omega L.$$

$$\text{or } L = \frac{X_L}{\omega} = \frac{10}{20} = 0.5 \text{ H}$$

17 (b)

When a circuit contains inductance only, then the current lags behind the voltage by the phase difference of $\frac{\pi}{2}$ or 90° .

While in a purely capacitive circuit, the current leads the voltage by a phase angle of $\frac{\pi}{2}$ or 90° .

In a purely resistive circuit current is in phase with the applied voltage.

18 **(b)**

At $t = 0$, inductor behaves like an infinite resistance. So at

$$t = 0, i = \frac{V}{R_2}$$


And at $t = \infty$, inductor behaves like a conducting wire,

$$i = \frac{V}{R_{eq}} = \frac{V(R_1 + R_2)}{R_1 R_2}$$


19 **(c)**

Hot wire ammeter reads *rms* value of current. Hence its peak value $= i_{rms} \times \sqrt{2}$
 $= 14.14 \text{ amp}$

20 **(c)**

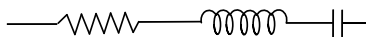


$$\frac{X_C}{R} = \tan \frac{\pi}{3}$$

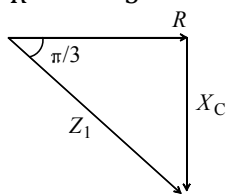

$$X_C = R \tan \frac{\pi}{3} \quad \dots(i)$$

$$\frac{X_L}{R} = \tan \frac{\pi}{3}$$

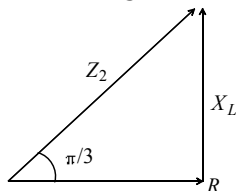

$$X_L = R \tan \frac{\pi}{3} \quad \dots(ii)$$

$$\text{Net impedance } Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\text{Power factor } \cos \phi = \frac{R}{Z} = 1$$

PEE

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	B	A	A	D	A	B	A	B	B	D
Q.	11	12	13	14	15	16	17	18	19	20
A.	C	D	C	A	A	A	B	B	C	C

PE