

Topic :- Alternating current

1

(a)

Impedance of LCR circuit will be minimum at resonant frequency so

$$V_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{1 \times 10^{-3} \times 0.1 \times 10^{-6}}}$$

$$= \frac{10^5}{2\pi} \text{ Hz}$$

2


(b)

Here, resistance of rod $= 2\Omega$, $r = 0.1 \text{ m}$, $B = 50 \text{ T}$, along z – axis $\omega = 20 \text{ rads}^{-1}$.

Potential difference between centre of the ring and the rim is

$$V = \frac{1}{2}B\omega r^2 = \frac{1}{2} \times 50 \times 20 \times (0.1)^2 = 5 \text{ V}$$

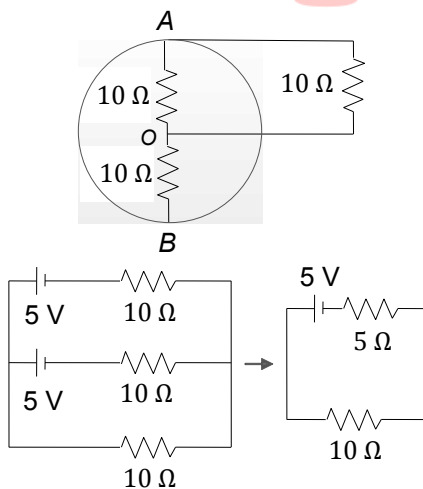The equivalent circuit of the arrangement is shown in figure



Current through external resistance,

$$i = \frac{E}{R+r} = \frac{5}{10+5} = \frac{1}{3} \text{ A}$$

3

(c)

$$\tan \phi = \frac{\omega L}{R} = \frac{2\pi \times 50 \times 0.21}{12} = 5.5 \Rightarrow \phi = 80^\circ$$

5 **(d)**

$$e = L di/dt = 4 \times \frac{5}{1/1500} = 30000V = 30kV$$

7 **(a)**

$$X_L = 2\pi fL = 2\pi \left(\frac{50}{\pi}\right) \times 1 = 100\Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2\pi \left(\frac{50}{\pi}\right) \times 20 \times 10^{-6}}$$

$$= 500\Omega$$

$$\text{Impedance } Z = \sqrt{(R)^2 + (X_C - X_L)^2}$$

$$= \sqrt{(300)^2 + (400)^2}$$

$$= 500\Omega$$

9 **(d)**

$$Z = \sqrt{(R)^2 + (X_L - X_C)^2};$$

$$R = 10\Omega, X_L = \omega L = 2000 \times 5 \times 10^{-3} = 10\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2000 \times 50 \times 10^{-6}} = 10\Omega, \text{ i.e., } Z = 10\Omega$$

$$\text{Maximum current } i_0 = \frac{V_0}{Z} = \frac{20}{10} = 2A$$

$$\text{Hence } i_{rms} = \frac{2}{\sqrt{2}} = 1.4A \text{ and } V_{rms} = 4 \times 1.41 = 5.64V$$

11 **(d)**

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\therefore V_R = V \therefore V_L = V_C$$

$$\therefore \text{Reading of voltmeter} = 220V$$

$$\text{Reading of ammeter } I_{rms} = \frac{E_{rms}}{Z}$$

$$= \frac{220}{100} = 2.2A$$

12 **(a)**

Motion emf induced in the connector


$$e = Blv = 2(1)(2) = 4V$$

This acts as a cell of emf 4V and internal resistance 2 Ω . 6 Ω and 3 Ω resistors are in

parallel.

$$\therefore \frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6} = \frac{3}{6} = \frac{1}{2}$$

$$R_p = 2 \Omega$$

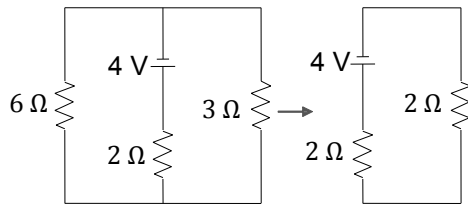

\therefore Current through the connector (i)

$$= \frac{E}{R_p + r} = \frac{4}{2+2} = 1 \text{ A.}$$

Magnetic force on the connector

$$= Bil = (1)(1) = 2 \text{ N}$$

Therefore, to keep the connector moving with a constant velocity, a force of 2 N has to be applied to the right side.

13 (c)

Heat produced by ac = 3 × Heat produced by dc

$$\therefore i_{rms}^2 R t = 3 \times i^2 R t \Rightarrow i_{rms}^2 = 3 \times 2^2$$

$$\Rightarrow i_{rms} = 2\sqrt{3} = 3.46 \text{ A}$$

14 (d)

Brightness $\propto P_{consumed} \propto \frac{1}{R}$ For bulb, $R_{ac} = R_{dc}$, so brightness will be equal in both the Cases

15 (c)

$$E = 141 \sin 628t$$

$$\therefore E_{rms} = \frac{E_0}{\sqrt{2}}$$

$$= \frac{141}{1.41} = 100 \text{ V}$$

and $v = \frac{\omega}{2\pi}$

$$= \frac{628}{2 \times 3.14} = 100 \text{ Hz}$$

16 (c)

Here, $R = 10 \Omega$. As is known,

$$|dq| = \frac{d\phi}{R} = |i dt| = \text{area under } i - t \text{ graphs.}$$

$$\therefore \frac{d\phi}{R} = \frac{(4)(0.1)}{2} = 0.2$$

$$d\phi = 0.2 R = 0.2 \times 10 = 2 \text{ Wb}$$

17 (a)

From $\phi = Mi$

$$\frac{M_1}{M_2} = \frac{\phi_1}{\phi_2} = \frac{10^{-3} \times 200}{0.8 \times 10^{-3} \times 400} = \frac{10}{16} = 0.625$$

18 (a)

Here, $V_{rms} = 220V$, $\nu = 50 \text{ Hz}$

Peak value of voltage $V_0 = \sqrt{2} V_{rms} = 220\sqrt{2} \text{ V}$

\therefore The instantaneous value of voltage is


$$V = V_0 \sin 2\pi\nu t = 220\sqrt{2} \sin 2\pi \times 50t \\ = 220\sqrt{2} \sin 100\pi t$$

19 (d)

$$e = \frac{Mdl}{dt} = 0.09 \times \frac{20}{0.006} = 300V$$

20 (a)

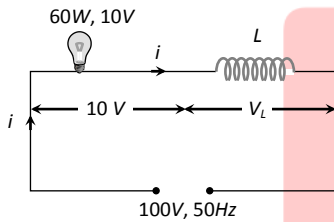Current through the bulb $i = \frac{P}{V} = \frac{60}{10} = 6A$



$$V = \sqrt{V_R^2 + V_L^2} \\ (100)^2 = (10)^2 + V_L^2 \\ \Rightarrow V_L = 99.5 \text{ Volt}$$

Also $V_L = iX_L = i \times (2\pi\nu L)$

$$\Rightarrow 99.5 = 6 \times 2 \times 3.14 \times 50 \times L$$

$$\Rightarrow L = 0.052 \text{ H}$$

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	A	B	C	C	D	B	A	B	D	D
Q.	11	12	13	14	15	16	17	18	19	20
A.	D	A	C	D	C	C	A	A	D	A

PE