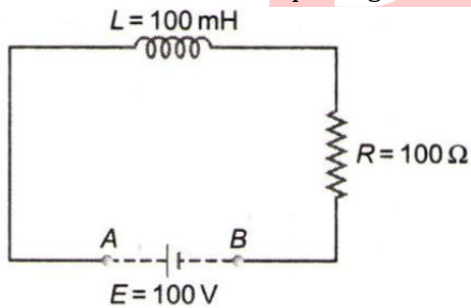


### Topic :- Alternating current

1      **(b)**  
 $Z = \sqrt{R^2 + X_L^2}, X_L = \omega L \text{ and } \omega = 2\pi f$   
 $\therefore Z = \sqrt{R^2 + 4\pi^2 f^2 L^2}$

3      **(b)**  
 $V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{120}{1.414} = 84.8 \text{ V}$

4      **(a)**  
 This is a combined example of growth and decay of current in an  $L - R$  circuit.




The current through circuit just before shorting the battery,

$$I_0 = \frac{E}{R} = 1 \text{ A}$$

(as inductor would be shorted in steady state)

After this decay of current starts in the circuit according to the equation  $I = I_0 e^{-t/\tau}$

Where  $\tau = L/R$ .

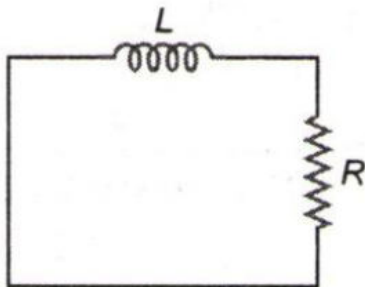

$$I = 1 \times e^{-(1 \times 10^{-3}) / (100 \times 10^{-3} / 100)} = (1/e) \text{ A}$$

5 **(d)**

$$\frac{R}{L} = \frac{e/i}{edt/di} = \frac{1}{dt} = \text{frequency.}$$

6 **(a)**

Phase difference relative to the current

$$\phi = \left(314t - \frac{\pi}{6}\right) - (314t) = -\frac{\pi}{6}$$

7 **(b)**

At  $t = 0$ , phase of the voltage is zero, while phase of the current is  $-\frac{\pi}{2}$ , i.e., voltage leads by  $\frac{\pi}{2}$

8 **(d)**

$$\begin{aligned} Z^2 &= R^2 + (2\pi fL)^2 \\ &= (30)^2 + \left(2\pi \times 50 \times \frac{0.4}{\pi}\right)^2 \\ &= (900 + 1600) = 2500 \end{aligned}$$

$$\text{or } Z = 50 \Omega$$

$$\text{Also, } I = \frac{V}{Z} = \frac{200}{50} = 4 \text{ A}$$

10 **(b)**

We know that  $Q$ - factor of series resonant circuit is given as

$$Q = \frac{\omega_r L}{R}$$

Here,  $L = 8.1 \text{ mH}$ ,  $C = 12.5 \mu\text{F}$ ,  $R = 10 \Omega$ ,  $f = 500 \text{ Hz}$

$$\begin{aligned} \therefore Q &= \frac{\omega_r L}{R} = \frac{2\pi fL}{R} \\ &= \frac{2 \times \pi \times 500 \times 8.1 \times 10^{-3}}{10} = \frac{8.1\pi}{10} = 2.5434 \end{aligned}$$

11 **(b)**

For capacitive circuits  $X_C = \frac{1}{\omega C}$

$$\therefore i = \frac{V}{X_C} = V\omega C \Rightarrow i \propto \omega$$

12 **(b)**

$$V_0 = \sqrt{2} V_{rms} = 10\sqrt{2}$$

13 **(a)**

In L-R circuit, the growing current at time  $t$  is given by  $i = i_0 \left[1 - e^{-\frac{t}{\tau}}\right]$  where  $i_0 = \frac{E}{R}$  and  $\tau = \frac{L}{R}$

$\therefore$  Charge passed through the battery in one time constant is

$$\begin{aligned} q &= \int_0^\tau i dt = \int_0^\tau i_0 (1 - e^{-t/r}) dt \\ q &= i_0 \tau - \left[ \frac{i_0 e^{-t}}{-2/\tau} \right]_0^\tau = i_0 \tau + i_0 \tau [e^{-1} - 1] \\ &= i_0 \tau - i_0 \tau + \frac{i_0 \tau}{e} \\ q &= \frac{i_0 \tau}{e} = \frac{(E/R)(L/R)}{e} = \frac{eL}{eR^2} \end{aligned}$$

14 **(b)**  
 $P_i = 240 \times 0.7 = 168 \text{ W}, P_0 = 140 \text{ W}$   
 $\eta = \frac{P_0}{P_i} \times 100 = \frac{140}{168} \times 100 \approx 80\%$

15 **(c)**  
 Energy stored in a inductor  $L$  carrying  
 Current  $i$  is  $U = \frac{1}{2} L i^2$   
 Rate at which energy is stored  
 $= \frac{dU}{dt} = \frac{1}{2} L 2i \left(\frac{di}{dt}\right) = Li \left(\frac{di}{dt}\right)$   
 At  $t = 0, i = 0, \therefore \frac{dU}{dt} = 0$

At  $t = \infty, i = i_0$  (constant),  $\therefore \frac{di}{dt} = 0$   
 16 **(d)**  
 Required time  $t = T/4 = \frac{1}{4 \times 50} = 5 \times 10^{-3} \text{ sec}$


17 **(a)**  
 Maximum voltage is AC circuit  
 $V_0 = 282 \text{ V}$   
 $V = \frac{V_0}{\sqrt{2}} = \frac{282}{\sqrt{2}}$   
 $V = \frac{282}{1.41} = \frac{28200}{141}$   
 $V = 200 \text{ V}$



18 **(b)**  
 $X_C = \frac{1}{2\pi\nu C} = \frac{1}{0} = \infty$

19 **(b)**  
 $Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (2\pi \times 60 \times 2)^2} = 753.7$   
 $\therefore i = \frac{120}{753.7} = 0.159 \text{ A}$

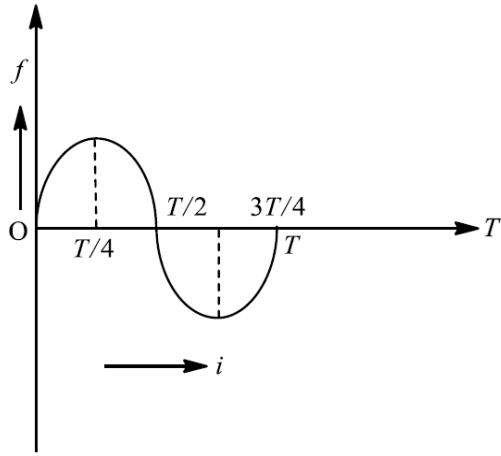20 **(b)**  
 An alternating current is one whose magnitude changes continuously with time between zero and a maximum value and whose direction reverses periodically. The relation between frequency ( $f$ ) and time ( $T$ ) is.



$$T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s}$$

As is clear from the figure time taken to reach the maximum value is

$$\frac{T}{4} = \frac{0.02}{4} = 0.005 \text{ s}$$

PE

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	B	C	B	A	D	A	B	D	D	B
Q.	11	12	13	14	15	16	17	18	19	20
A.	B	B	A	B	C	D	A	B	B	B

**PE**