

### Topic :- Alternating current

1 (b)

$$\text{From } e = L \frac{dI}{dt} \Rightarrow dI = \frac{e}{L} = \frac{1}{1} = 1 \text{ As}^{-1}$$

2 (a)

After time  $t$ , thickness of liquid will remain  $\left(\frac{d}{3} - vt\right)$ .

Now, time constant as function of time  
 $\tau_c = CR$

$$\begin{aligned} &= \frac{\varepsilon_0(1).R}{\left(d - \frac{d}{3} + vt\right) + \frac{d/3 - vt}{2}} \left( \text{Applying } C = \frac{\varepsilon_0 A}{d - t + \frac{t}{k}} \right) \\ &= \frac{6\varepsilon_0 R}{5d + 3vt} \end{aligned}$$

3 (d)

When wire is thick, its resistance reduces. Therefore, Joules' heating loss is reduced.

4 (c)

$$\text{Peak value} = 220\sqrt{2} = 311 \text{ V}$$

5 (c)

$I_L$  lags behind  $I_R$  by a phase of  $\frac{\pi}{2}$ , while  $I_C$  leads by a phase of  $\frac{\pi}{2}$

6 (b)

Time constant of  $R - C$  circuit is  $\tau = RC$

Here effective resistance of the circuit

$$\begin{aligned} &= \frac{2R \times 3R}{2R + 3R} = \frac{6R}{5} \\ \therefore \tau &= \frac{6R}{5} \times C = \frac{6RC}{5} \end{aligned}$$

7 (b)

$$e = \frac{M di}{dt} = \left( \frac{\mu_0 N_1 N_2 A}{l} \right) \frac{di}{dt}$$

$$= \frac{4\pi \times 10^{-7} \times 2000 \times 300 \times 1.2 \times 10^{-3} (4)}{0.3 \times 0.25}$$

$$= 4.8 \times 10^{-2} \text{ V}$$

8

(a)

$$V = 5 \cos \omega t = 5 \sin \left( \omega t + \frac{\pi}{2} \right) \text{ and } i = 2 \sin \omega t$$

$$\text{Power} = V_{r.m.s.} \times i_{r.m.s.} \times \cos \phi = 0$$

$$[\text{Since } \phi = \frac{\pi}{2}, \text{ therefore } \cos \phi = \cos \frac{\pi}{2} = 0]$$

9

(d)

$$i = \frac{V}{Z} = \frac{4}{\sqrt{4^2 + (1000 \times 3 \times 10^{-3})^2}} = 0.8 \text{ A}$$

10

(a)

$$X_L = 31 \Omega, X_C = 25 \Omega, R = 8 \Omega$$

Impedance of series LCR is

$$Z = \sqrt{(R)^2 + (X_L - X_C)^2}$$

$$= \sqrt{(8)^2 + (31 - 25)^2} = \sqrt{64 + 36} = 10 \Omega$$

$$\text{Power factor, } \cos \phi = \frac{R}{Z} = \frac{8}{10} = 0.8$$

11

(d)

$$B = \frac{\phi}{A} = \frac{\mu_0 N_1 A i}{L A} = \frac{\mu_0 N^2 i}{L}$$

12

(c)

$$P = E_{rms} i_{rms} \cos \phi = \frac{E_0}{\sqrt{2}} \times \frac{i_0}{\sqrt{2}} \times \frac{R}{Z}$$


$$\Rightarrow \frac{E_0}{\sqrt{2}} \times \frac{E_0}{Z \sqrt{2}} \times \frac{R}{Z} \Rightarrow P = \frac{E_0^2 R}{2Z^2}$$

$$\text{Given } X_L = R \text{ so, } Z = \sqrt{2} R \Rightarrow P = \frac{E_0^2}{4R}$$

13

(a)

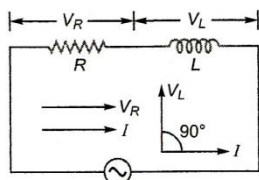Since, current lags behind the voltage in phase by a constant angle, then circuit must contain  $R$  and  $L$ .




We find that in  $R - L$  circuit, voltage leads the current by a phase angle  $\phi$ , where

$$\tan \phi = \frac{AK}{OA} = \frac{OL}{OA}$$

$$= \frac{V_L}{V_R} = \frac{I_0 X_L}{I_0 R}$$

$$\therefore \tan \phi = \frac{X_L}{R}$$

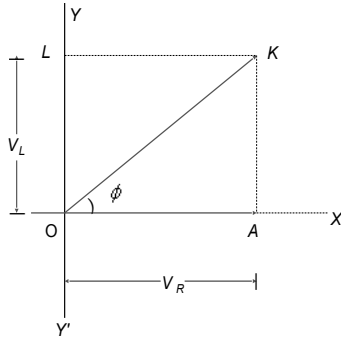

14 (d)

Current will be max at first time when

$$100\pi t + \pi/3 = \pi/2 \Rightarrow 100\pi t = \pi/6 \Rightarrow t = 1/600 \text{ s}$$

15 (d)

The current will lag behind the voltage when reactance of inductance is more than the reactance of condenser.

$$\text{Thus, } \omega L > \frac{1}{\omega C} \text{ or } \omega > \frac{1}{\sqrt{LC}}$$

$$\text{or } n > \frac{1}{2\pi\sqrt{LC}} \text{ or } n > n_r \text{ where } n_r = \text{resonant frequency}$$

16 (b)

$$e = L \frac{di}{dt} = \frac{edt}{dt} = \frac{8(0.05)}{(4-2)} = 0.2 \text{ H}$$

17 (c)

In  $L-R$  circuit, current at any time  $t$  is given by

$$i = \frac{E}{R} \left(1 - e^{-\frac{R}{L}t}\right) = \frac{E}{R} - \frac{E}{R} e^{-\frac{R}{L}t}$$

$$\frac{di}{dt} = \frac{E}{R} e^{-\frac{R}{L}t} \left(\frac{R}{L}\right) = \frac{E}{L} e^{-\frac{R}{L}t}$$

$$\text{Induced emf} = L \frac{di}{dt} = E e^{-\frac{R}{L}t}$$

$$\text{From Eq. (i), } iR = E - E e^{-\frac{R}{L}t}$$

$$\text{Using Eq. (ii), } iR = E - e \quad \text{or} \quad e = E - iR$$

Therefore, graph between  $e$  and  $i$  is a straight line with negative slope and positive intercept. The choice (c) is correct.

18 (c)

$$U = \frac{1}{2C} q^2 = \frac{1}{2C} (q_0 e^{-t/\tau})^2 = \frac{q_0^2}{2C} e^{-2t/\tau} \text{ (where } \tau = CR)$$

$$U = U_i e^{-2t/\tau}$$

$$\frac{1}{2}U_i = U_i e^{-2t_1/\tau}$$

$$\frac{1}{2} = e^{-2t_1/\tau}$$

⇒

$$t_1 = \frac{\tau}{2} \ln 2$$

Now

$$q = q_0 e^{-t/\tau}$$

$$\frac{1}{2}q_0 = q_0 e^{-t_2/\tau}$$

$$t_2 = \tau \ln 4 = 2\tau \ln 2$$

∴

$$\frac{t_1}{t_2} = \frac{1}{4}$$

19

**(a)**

At resonance *LCR* series circuit behaves as pure resistive circuit. For resistive circuit

$$\phi = 0^\circ$$

20

**(b)**

$$Z = \sqrt{R^2 + X^2} = \sqrt{4^2 + 3^2} = 5$$

$$\therefore \cos \phi = \frac{R}{Z} = \frac{3}{5} = 0.6$$

PE

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	B	A	D	C	C	B	B	A	D	A
Q.	11	12	13	14	15	16	17	18	19	20
A.	D	C	A	D	D	B	C	C	A	B

PE