

## Topic :- Alternating current

2 (c)

$$\text{As } e = M \frac{di}{dt}$$

$$\therefore 30 \times 10^3 = 3 \times \frac{10}{dt},$$

$$d = \frac{30}{30 \times 10^3} = 10^{-3} \text{ s}$$

3 (b)

Wheatstone bridge is balanced. Current through  $AC$  is zero. Effective resistance  $R$  of bridge is

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3}, R = 3\Omega$$

$$\text{Total resistance} = 1 + 3 = 4\Omega$$

Induced emf

$$e = iR = Blv$$

$$\therefore v = \frac{iR}{Bl} = \frac{1 \times 10^{-3} \times 4}{2 \times 0.1} \\ = 2 \times 10^{-2} \text{ ms}^{-1}$$

4 (b)

Motional emf across  $PQ$

$$V = Blv = 4(1)(2) = 8 \text{ volt}$$

This is the potential to which the capacitor is charged.

$$\text{As } q = CV$$

$$\therefore q = (10 \times 10^{-6})8 = 10^{-5} \text{ C} = 80 \mu \text{ C}$$

As magnetic force on electron in the conducting rod  $PQ$  is towards  $Q$ , therefore,  $A$  is positively charged and  $B$  is negatively charged

$$\text{ie, } q_A = +80 \mu \text{ C} \text{ and } q_B = -80 \mu \text{ C}$$

5 (c)

The DC generator must be mixed wound to withstand the load variation.

- 6 **(a)**  
For imparting max power

$$X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega^2 L} = \frac{1}{(2\pi f)^2 \times L} = \frac{1}{(100\pi)^2 \times 10} = 1 \times 10^{-6} = 1\mu F$$

- 8 **(c)**

$$Z = \sqrt{R^2 + \left(\frac{1}{2\pi\nu C}\right)^2} = \sqrt{(3000)^2 + \frac{1}{\left(2\pi \times 50 \times \frac{2.5}{\pi} \times 10^{-6}\right)^2}}$$


$$\Rightarrow Z = \sqrt{(3000)^2 + (4000)^2} = 5 \times 10^3 \Omega$$

$$\text{So power factor } \cos \phi = \frac{R}{Z} = \frac{3000}{5 \times 10^3} = 0.6 \text{ and power}$$

$$P = V_{rms} i_{rms} \cos \phi = \frac{V_{rms}^2 \cos \phi}{Z} \Rightarrow P = \frac{(200)^2 \times 0.6}{5 \times 10^3} = 4.8W$$

- 10 **(d)**

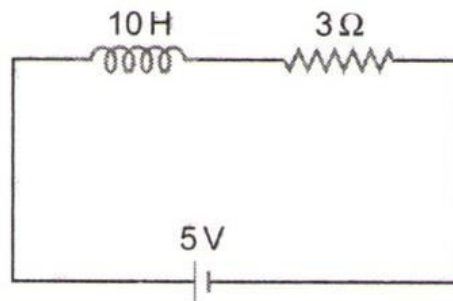Rise of current in  $L - R$  circuit is given by



$$I = I_0(1 - e^{-t/\tau})$$

$$\text{Where, } I_0 = \frac{E}{R} = \frac{5}{5} = 1 \text{ A}$$

$$\text{Now, } \tau = \frac{L}{R} = \frac{10}{5} = 2 \text{ s}$$

After 2s, i.e, at  $t = 2 \text{ s}$

$$\text{Rise of current } I = (1 - e^{-1})\text{A}$$

- 11 **(b)**

As  $e = M di/dt$ ,

$$\therefore M = \frac{edt}{di} = -\frac{15000 \times 0.001}{3} = 5\text{H}$$

- 12 **(b)**

At resonance,  $LCR$  circuit behaves as purely resistive circuit. For purely resistive circuit power factor = 1

- 13 **(a)**  
Voltage across the capacitors will increase from 0 to 10 V exponentially. The voltage at time  $t$  will be given by

$$V = 10(1 - e^{-t/\tau_C})$$

$$\text{Here } \tau_C = C_{\text{net}}R_{\text{net}} = (1 \times 10^6)(4 \times 10^{-6}) = 4 \text{ s}$$

$$\therefore V = 10(1 - e^{-t/4})$$

Substituting  $V = 4$  volt, we have,

$$4 = 10(1 - e^{-t/4})$$

$$e^{-t/4} = 0.6 = \frac{3}{5}$$

Taking log both sides we have,

$$-\frac{t}{4} = \ln 3 - \ln 5$$

$$\text{or } t = 4(\ln 5 - \ln 3) = 2 \text{ s.}$$

- 14 **(c)**

$$\text{From } L = \frac{\mu_0 N^2 A}{l} = \frac{\mu_0 \mu_r N^2 A}{l},$$

When  $\mu = 1000$  and  $N$  becomes  $\frac{1}{10}$

$$\therefore L \text{ becomes } 1000 \times \left(\frac{1}{10}\right)^2 = 10 \text{ times}$$

$$\text{i.e., } L = 10 \times 0.1 = 1 \text{ H}$$

- 15 **(b)**

$$\text{From } R = \frac{E - V}{i}$$

$$0.5 = \frac{120 - V}{8}$$

$$V = 116 \text{ V}$$

- 17 **(b)**

In non resonant circuits

Impedance  $Z = \frac{1}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}}$ , with rise in frequency  $Z$  decreases, i.e., current increases so circuit behaves as capacitive circuit

- 18 **(c)**

Phase difference in  $R - L$  circuit,

$$\phi = \tan^{-1} \frac{X_L}{R}$$

$$\text{or } \tan 45^\circ = \frac{X_L}{R}$$

$$\text{or } X_L = R$$

- 19 **(d)**

At resonant frequency current in series  $LCR$  circuit is maximum

- 20 **(d)**

Magnetic field at the centre of primary coil  $B = \mu_0 i_1 / 2R_1$ . Considering it to be uniform,

magnetic flux passing through secondary coil is

$$\phi = BA = \frac{\mu_0 i_1}{2R_1} (\pi R_2^2)$$

$$\text{Now, } M = \frac{\phi_2}{i_1} = \frac{\mu_0 \pi R_2^2}{2R_1}$$

$$\therefore M \propto \frac{R_2^2}{R_1}$$

PE

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	A	C	B	B	C	A	D	C	C	D
Q.	11	12	13	14	15	16	17	18	19	20
A.	B	B	A	C	B	C	B	C	D	D

PE