
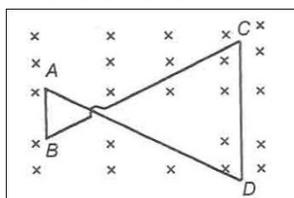


Topic :-Alternating Current

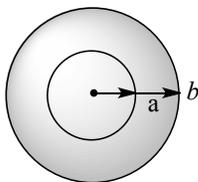1. A conducting wire frame is placed in a magnetic field, which is directed into the paper, figure. The magnetic field is increasing at a constant rate. The directions of induced current in wires AB and CD are



- a) A to B and C to D b) B to A and C to D
 c) A to B and D to C d) B to A and D to C
2. A pure inductive coil of 30 mH is connected to an AC source of 220 V, 50 Hz. The rms current in the coil is
 a) 50.35 A b) 23.4 A c) 30.5 A d) 12.3 A
3. In an ac circuit, V and I are given by
 $V = 100\sin(100t)$ volts, $I = 100\sin(100t + \frac{\pi}{3})$ mA. The power dissipated in circuit is
 a) 10^4 watt b) 10 watt c) 2.5 watt d) 5 watt
4. Two concentric and coplanar circular coils have radii a and b as shown in figure. Resistance of the inner coil is R . Current in the other coil is increased from 0 to i , then the total charge circulating the inner coil is



- a) $\frac{\mu_0 i a b}{2 R}$ b) $\frac{\mu_0 i a \pi b^2}{2 a b}$ c) $\frac{\mu_0 i b}{2 \pi R}$ d) $\frac{\mu_0 i a^2}{2 R b}$
5. A circuit area is 0.01 m^2 is kept inside a magnetic field which is normal to its plane. The magnetic field changes from 2 T to 1 T in 1 millisecond. If the resistance of the circuit is 2Ω . The amount of heat evolved is
 a) 0.05 J b) 50 J c) 0.50 J d) 500 J
6. In an AC circuit the emf(e) and the current (i) at any instant are given respectively by


$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is

- a) $\frac{E_0 I_0}{2}$ b) $\frac{E_0 I_0}{2} \sin \phi$ c) $\frac{E_0 I_0}{2} \cos \phi$ d) $E_0 I_0$

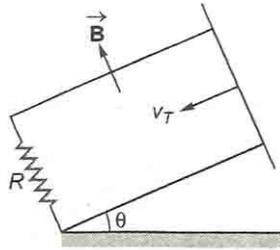7. A copper rod of mass m slides under gravity on two smooth parallel rails l distance apart and set at an angle θ to the horizontal. At the bottom, the rails are joined by a resistance R , figure. There is a uniform magnetic field B perpendicular to the plane of the rails. The terminal velocity of the rod is



- a) $\frac{mgR \tan \theta}{B^2 l^2}$ b) $\frac{mgR \cot \theta}{B^2 l^2}$ c) $\frac{mgR \sin \theta}{B^2 l^2}$ d) $\frac{mgR \cos \theta}{B^2 l^2}$

8. Reactance of a capacitor of capacitance $C \mu F$ for ac frequency $\frac{400}{\pi} Hz$ is 25Ω . The value C is

- a) $50 \mu F$ b) $25 \mu F$ c) $100 \mu F$ d) $75 \mu F$

9. A choke coil has

- a) High inductance and low resistance b) Low inductance and high resistance
c) High inductance and high resistance d) Low inductance and low resistance

10. Two coils A and B have coefficient of mutual inductance $M = 2H$. The magnetic flux passing through coil A changes by $4 Wb$ in $10 s$ due to change in current in B . Then

- a) Change in current in B in this time interval is $0.5 A$ b) Change in current in B in this time interval is $8 A$
c) The change in current in B in this time interval is $2 A$ d) A change in current of $1 A$ in coil A will produce a change in flux passing through B by $4 Wb$

11. In an ac circuit the reactance of a coil is $\sqrt{3}$ times its resistance, the phase difference between the voltage across the coil to the current through the coil will be

- a) $\pi/3$ b) $\pi/2$ c) $\pi/4$ d) $\pi/6$






12. The phase difference between the voltage and the current in an ac circuit is $\pi/4$. If the frequency is $50 Hz$ then this phase difference will be equivalent to a time of

- a) $0.02 s$ b) $0.25 s$ c) $2.5 ms$ d) $25 ms$


13. In AC series circuit, the resistance, inductive reactance and capacitive reactance are 3Ω , 10Ω and 14Ω respectively. The impedance of the circuit is

- a) 5Ω b) 4Ω c) 7Ω d) 10Ω

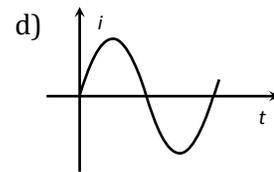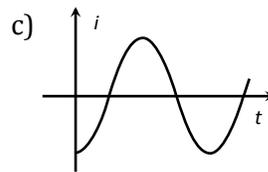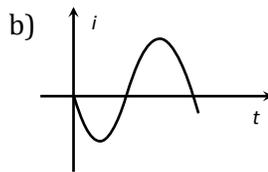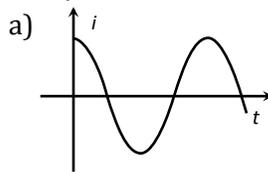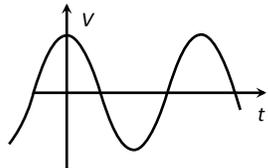14. The voltage across a pure inductor is represented by the following diagram. Which of the following diagrams will represent the current



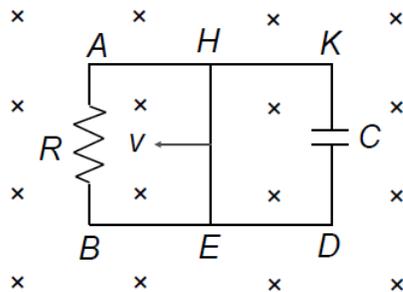15. Q-factor can be increased by having a coil of
- Large inductance, small ohmic resistance
 - Large inductance, large ohmic resistance
 - Small inductance, large ohmic resistance
 - Small inductance, small ohmic resistance
16. The current which does not contribute to the power consumed in an AC circuit is called
- non-ideal current
 - wattles current
 - convectonal current
 - inductance current
17. In the circuit shown in figure, a conducting wire HE is moved with a constant speed v towards left. Th complete circuit is placed in a uniform magnetic field \vec{B} perpendicular to the plane of circuit inwards. The current in $HKDE$ is



- Anti-clock-wise
 - Clock-wise
 - Alternating
 - Zero
18. The current passing through a choke coil of 5 H is decreasing at the rate of 2 As^{-1} . The emf developed across the coil is
- -10 V
 - $+10\text{ V}$
 - 2.5 V
 - -2.5 V
19. A light bulb is rated 100 W for a 220 V supply. The resistance of the bulb and the peak voltage of the source respectively are
- $242\ \Omega$ and 311 V
 - $484\ \Omega$ and 311 V
 - $484\ \Omega$ and 440 V
 - $242\ \Omega$ and 440 V
20. If number of turns in primary and secondary coils is increased to two times each, the mutual

inductance

- a) Becomes 4 times
- c) Becomes $1/4$ times

- b) Becomes 2 times
- d) Remains unchanged

PE