

Topic :- Alternating Current

- A resistor $30\ \Omega$, inductor of reactance $10\ \Omega$ and capacitor of reactance $10\ \Omega$ are connected in series to an AC voltage source $e = 300\sqrt{2}\sin(\omega t)$. The current in the circuit is
 - $10\sqrt{2}\ \text{A}$
 - $10\ \text{A}$
 - $30\sqrt{11}\ \text{A}$
 - $30/\sqrt{11}\ \text{A}$
- The natural frequency (ω_0) of oscillations in $L - C$ circuit is given by
 - $\frac{1}{2\pi}\frac{1}{\sqrt{LC}}$
 - $\frac{1}{2\pi}\sqrt{LC}$
 - $\frac{1}{\sqrt{LC}}$
 - \sqrt{LC}
- An ac source of angular frequency ω is fed across a resistor r and a capacitor C in series. The current registered is I . If the frequency of source is changed to $\omega/3$ (maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of reactance to resistance at the original frequency ω
 - $\frac{\sqrt{3}}{\sqrt{5}}$
 - $\frac{\sqrt{2}}{\sqrt{5}}$
 - $\frac{1}{\sqrt{5}}$
 - $\frac{\sqrt{4}}{\sqrt{5}}$
- When a DC voltage of $200\ \text{V}$ is applied to a coil of self-inductance $(\frac{2\sqrt{3}}{\pi})\ \text{H}$, a current of $1\ \text{A}$ flows through it. But by replacing DC source with AC source of $200\ \text{V}$, the current in the coil is reduced to $0.5\ \text{A}$. Then the frequency of AC supply is
 - $100\ \text{Hz}$
 - $75\ \text{Hz}$
 - $60\ \text{Hz}$
 - $50\ \text{Hz}$
- The power factor of good choke coil is
 - Nearly zero
 - Exactly zero
 - Nearly one
 - Exactly one
- A resistor of $R = 6\ \Omega$, an inductor of $L = 1\ \text{H}$ and a capacitor of $C = 17.36\ \mu\text{F}$ are connected in series with an AC source. Find the Q -factor.
 - 3.72
 - 40
 - 2.37
 - 80
- Power dissipated in an LCR series circuit connected to an a.c. source of $emf\ E$ is

$$a) E^2 R / \left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]$$

$$b) \frac{E^2 \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2}}{R}$$

$$c) \frac{E^2 \left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]}{R}$$

$$d) \frac{E^2 R}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2}}$$

8. A virtual current of $4A$ and 50 Hz flows in an ac circuit containing a coil. The power consumed in the coil is 240 W . If the virtual voltage across the coil is 100 V its inductance will be

$$a) \frac{1}{3\pi}\text{ H}$$

$$b) \frac{1}{5\pi}\text{ H}$$

$$c) \frac{1}{7\pi}\text{ H}$$

$$d) \frac{1}{9\pi}\text{ H}$$

9. A lamp consumes only 50% of peak power in an a.c. circuit. What is the phase difference between the applied voltage and the circuit current


$$a) \frac{\pi}{6}$$

$$b) \frac{\pi}{3}$$

$$c) \frac{\pi}{4}$$

$$d) \frac{\pi}{2}$$

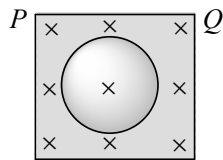10. A vertical ring of radius r and resistance R falls vertically. It is in contact with two vertical rails which are joined at the top, figure. The rails are without friction and resistance. There is a horizontal uniform magnetic field of magnitude B perpendicular to the plane of the ring and the rails. When the speed of the ring is v , the current in the section PQ is



a) Zero

$$b) \frac{2 Rrv}{R}$$

$$c) \frac{4 Rrv}{R}$$

$$d) \frac{8 Rrv}{R}$$

11. Voltage V and current i in AC circuit are given by

$$V = 50 \sin(50t) \text{ volt}$$

$$i = 50 \sin \left(50t + \frac{\pi}{3} \right) \text{ mA}$$

The power dissipated in circuit is

a) 5.0 W

b) 2.5 W

c) 1.25 W

d) Zero

12. In an LCR series resonant circuit which one of the following cannot be the expression for the Q-factor


$$a) \frac{\omega L}{R}$$

$$b) \frac{1}{\omega CR}$$

$$c) \sqrt{\frac{L}{C}} \frac{1}{R}$$

$$d) \frac{R}{LC}$$

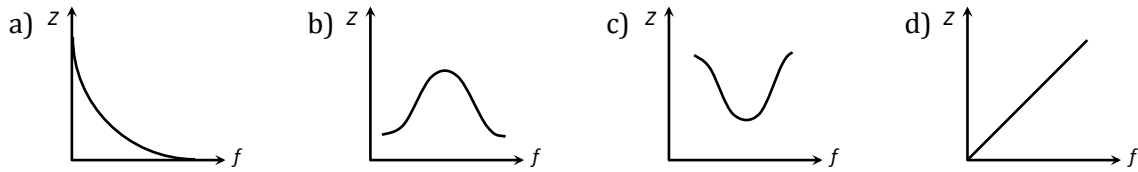13. Which one of the following curves represents the variation of impedance (Z) with frequency f in series LCR circuit



14. The frequency for which a $5 \mu F$ capacitor has a reactance of $\frac{1}{1000} \text{ohm}$ is given by

- a) $\frac{100}{\pi} \text{MHz}$ b) $\frac{1000}{\pi} \text{Hz}$ c) $\frac{1}{1000} \text{Hz}$ d) 1000Hz

15. The peak value of an alternating current is 5 A and its frequency is 60 Hz. Find its rms value and time taken to reach the peak value of current starting from zero.

- a) 3.536A; 4.167 ms b) 3.536 A; 15 ms c) 6.07 A; 10 ms d) 2.536 A; 4.167 ms


16. The resistance of an $R-L$ circuit is 10Ω . An emf E_0 applied across the circuit at $\omega = 20 \text{ rad s}^{-1}$. If the current in the circuit is $\frac{i_0}{\sqrt{2}}$, what is the value of L ?

- a) 0.5 H b) 2.25 H c) 3.9 H d) 1.0 H

17. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$, the circuit will contain which of the following?

- a) Only R b) Only C c) R and C d) Only L

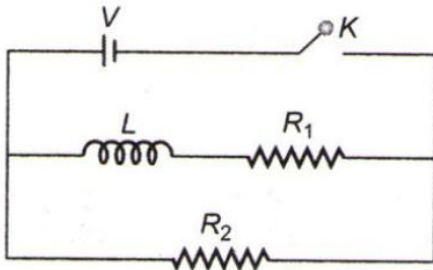18. In the circuit shown below, the key K is closed at $t = 0$. The current through the battery is



- a) $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$ at $t = 0$ and $\frac{V}{R_2}$ at $t = \infty$
 b) $\frac{V}{R_2}$ at $t = 0$ and $\frac{V(R_1 + R_2)}{R_1R_2}$ at $t = \infty$
 c) $\frac{V}{R_2}$ at $t = 0$ and $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$ at $t = \infty$

d) $\frac{V(R_1 + R_2)}{R_1 R_2}$ at $t = 0$ and $\frac{V}{R_2}$ at $t = \infty$

19. In a circuit, the value of the alternating current is measured by hot wire ammeter as 10 *ampere*. Its peak value will be

- a) 10 A b) 20 A c) 14.14 A d) $7.07 A$

20. In an electrical circuit R, L, C and an a.c. voltage source are all connected in series. When L is removed from the circuit, the phase difference between the voltage and the current in the circuit is $\pi/3$. If instead, C is removed from the circuit, the phase difference is again $\pi/3$. The power factor of the circuit is

- a) $1/2$ b) $1/\sqrt{2}$ c) 1 d) $\sqrt{3}/2$

PE