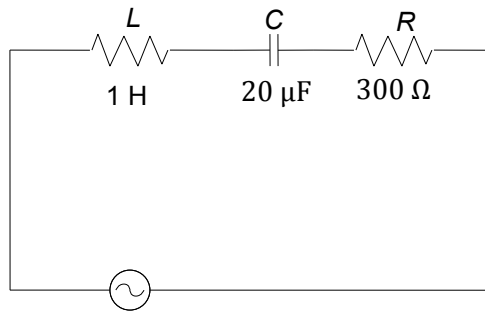


Topic :-Alternating Current

- An LCR circuit contains $R = 50 \Omega$, $L = 1 \text{ mH}$ and $C = 0.1 \mu\text{F}$. The impedance of the circuit will be minimum for a frequency of
 - $\frac{10^5}{2\pi} \text{ s}^{-1}$
 - $\frac{10^6}{2\pi} \text{ s}^{-1}$
 - $2\pi \times 10^5 \text{ s}^{-1}$
 - $2\pi \times 10^6 \text{ s}^{-1}$
- A metal rod of resistance 20Ω is fixed along a diameter of a conducting ring of radius 0.1 m and lies on $x - y$ plane. There is a magnetic field $\vec{B} = (50 \text{ T}) \hat{k}$. The ring rotates with an angular velocity $\omega = 20 \text{ rads}^{-1}$ about its axis. An external resistance of 10Ω is connected across the centre of the ring and rim. The current through external resistance is
 - $\frac{1}{2} \text{ A}$
 - $\frac{1}{3} \text{ A}$
 - $\frac{1}{4} \text{ A}$
 - Zero
- A 12 ohm resistor and a 0.21 henry inductor are connected in series to an ac source operating at 20 volts , 50 cycle/second . The phase angle between the current and the source voltage is
 - 30°
 - 40°
 - 80°
 - 90°
- The ratio of peak value and $r.m.s.$ value of an alternating current is
 - 1
 - $\frac{1}{2}$
 - $\sqrt{2}$
 - $1/\sqrt{2}$
- In an induction coil, the coefficient of mutual inductance is 4H . If current of 5A in the primary coil is cut off in $1/1500\text{s}$, the emf at the terminals of the secondary coil will be
 - 15 kV
 - 60 kV
 - 10 kV
 - 30 Kv
- The coil of choke in a circuit
 - Increases the current
 - Decreases the current
 - Do not change the current
 - Has high resistance to dc circuit

7. In the L - C - R circuit shown, the impedance is




- a) 500Ω b) 300Ω c) 100Ω d) 200Ω

8. The frequency of ac mains in India is

- a) 30 c/s or Hz b) 50 c/s or Hz c) 60 c/s or Hz d) 120 c/s or Hz

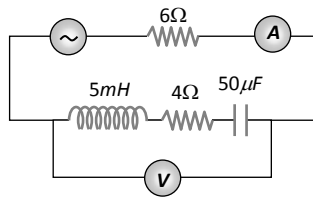9. In the circuit shown in the figure, the ac source gives a voltage $V = 20\cos(2000t)$. Neglecting source resistance, the voltmeter and ammeter reading will be




- a) $0V, 0.47A$ b) $1.68V, 0.47A$ c) $0V, 1.4 A$ d) $5.6V, 1.4 A$

10. An LCR series ac circuit is at resonance with $10 V$ each across L, C and R . If the resistance is halved, the respective voltage across L, C and R are

- a) $10 V, 10 V$ and $5 V$ b) $10 V, 10 V$ and $10 V$ c) $20 V, 20 V$ and $5 V$ d) $20 V, 20 V$ and $10 V$

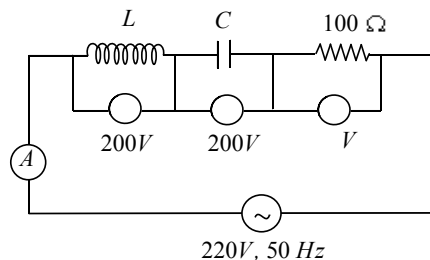11. The readings of ammeter and voltmeter in the following circuit are respectively



- a) $2A, 200V$ b) $1.5A, 100V$ c) $2.7A, 220V$ d) $2.2A, 220V$

a) $220\sqrt{2}\sin 100\pi t$ b) $220 \sin 100\pi t$ c) $220\sqrt{2}\sin 50\pi t$ d) $220 \sin 50\pi t$

19. Two circuits have mutual inductance of 0.09 H. Average emf induced in the secondary by a change of current from 0 to 20 A in 0.006 s in primary will be

a) 120 V b) 200 V c) 180 V d) 300 V

20. One 10 V, 60 W bulb is to be connected to 100 V line. The required induction coil has self inductance of value ($f = 50 \text{ Hz}$)

a) 0.052 H b) 2.42 H c) 16.2 mH d) 1.62 mH

PE