
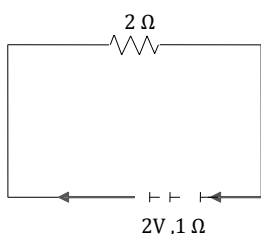


## Topic :- Current Electricity

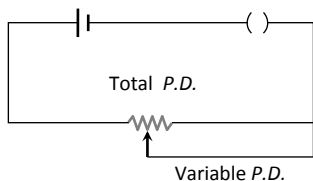1. In the electric circuit shown each cell has an emf of 2V and internal resistance of  $1\Omega$ . The external resistance is  $2\Omega$ . The value of the current  $I$  is (in ampere)




- a) 2      b) 1.25      c) 0.4      d) 1.2
2.  $A, B, C$  and  $D$  are four resistances of  $2\Omega, 2\Omega, 2\Omega$  and  $3\Omega$  respectively. They are used to form a Wheatstone bridge. The resistance  $D$  is short circuited with a resistance  $R$  in order to get the bridge balanced. The value of  $R$  will be
- a)  $4\Omega$       b)  $6\Omega$       c)  $8\Omega$       d)  $3\Omega$
3. The arrangement as shown in figure is called as



- a) Potential divider      b) Potential adder  
c) Potential subtractor      d) Potential multiplier
4. If the balance point is obtained at the  $35^{\text{th}}$  cm in a meter bridge, the resistances in the left and right gaps are in the ratio of
- a) 7 : 13      b) 13 : 7      c) 9 : 11      d) 11 : 9
5. Two electric bulbs rated  $P_1$  watt  $V$  volts and  $P_2$  watt  $V$  volts are connected in parallel and  $V$  volts are applied to it. The total power will be
- a)  $P_1 + P_2$  watt      b)  $\sqrt{P_1 P_2}$  watt      c)  $\frac{P_1 P_2}{P_1 + P_2}$  watt      d)  $\frac{P_1 + P_2}{P_1 P_2}$  watt

6. In a meter bridge a  $30\Omega$  resistance is connected in the left gap and a pair of resistances  $P$  and  $Q$  in the right gap. Measured from the left, the balance point is  $37.5$  cm, when  $P$  and  $Q$  are in series and  $71.4$  cm when they are parallel. The values of  $P$  and  $Q$  (in ohm) are  
 a) 40, 10                      b) 35, 15                      c) 30, 20                      d) 25, 25
7. In an experiment to measure the internal resistance of a cell by potentiometer, it is found that the balance point is at a length of  $2m$  when the cell is shunted by a  $5\Omega$  resistance; and is at a length of  $3m$  when the cell is shunted by a  $10\Omega$  resistance. The internal resistance of the cell is, then  
 a)  $1.5\Omega$                       b)  $10\Omega$                       c)  $15\Omega$                       d)  $1\Omega$
8. Two electroplating cells, one of silver and another of aluminium are connected in series. The ratio of the number of silver atoms to that of aluminium atoms deposited during time  $t$  will be  
 a) 1 : 3                      b) 3 : 1                      c) 1 : 9                      d) 9 : 1
9. A coil of wire of resistance  $50\Omega$  is embedded in a block of ice and a potential difference of  $210$  V is applied across it. The amount of ice which melts in 1 sec is  
 a)  $0.262$  g                      b)  $2.62$  g                      c)  $26.2$  g                      d)  $0.0262$  g
10. The resistance of  $1$  A ammeter is  $0.018\Omega$ . To convert it into  $10$  A ammeter, the shunt resistance required will be  
 a)  $0.18\Omega$                       b)  $0.0018\Omega$                       c)  $0.002\Omega$                       d)  $0.12\Omega$
11. When current flows through a conductor, then the order of drift velocity of electrons will be  
 a)  $10^{10}m/sec$                       b)  $10^{-2}cm/sec$                       c)  $10^4cm/sec$                       d)  $10^{-1}cm/sec$
12. Which of the following statements is wrong  
 a) Voltmeter should have high resistance  
 b) Ammeter should have low resistance  
 c) Ammeter is placed in parallel across the conductor in a circuit  
 d) Voltmeter is placed in parallel across the conductor in a circuit
13. A material  $B$  has twice the specific resistance of  $A$ . A circular wire made of  $B$  has twice the diameter of a wire made of  $A$ . Then for the two wires to have the same resistance, the ratio  $l_B/l_A$  of their respective lengths must be  
 a) 1                      b)  $1/2$                       c)  $1/4$                       d) 2

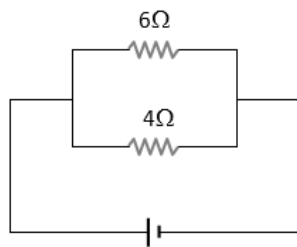14. In the circuit shown below, the power developed in the  $6\Omega$  resistor is 6 watt. The power in watts developed in the  $4\Omega$  resistor is



- a) 16                      b) 9                      c) 6                      d) 4
15. The value of internal resistance of an ideal cell is  
a) Zero                      b)  $0.5\ \Omega$                       c)  $1\ \Omega$                       d) Infinity
16. If the electronic charge is  $1.6 \times 10^{-19}\ \text{C}$ , then the number of electrons passing through a section of wire per second, when the wire carries a current of 2 A is  
a)  $1.25 \times 10^{17}$     b)  $1.6 \times 10^{17}$     c)  $1.25 \times 10^{19}$                       d)  $1.6 \times 10^{19}$
17. Two bulbs are working in parallel order. Bulb A is brighter than bulb B. If  $R_A$  and  $R_B$  are their resistance respectively then  
a)  $R_A > R_B$                       b)  $R_A < R_B$                       c)  $R_A = R_B$                       d) None of these
18. The amount of chlorine produced per-second through electrolysis in a plate which consumes 100 KW power at 200 V is (Given, electrochemical equivalent of chlorine =  $0.367 \times 10^{-3}\ \text{gC}^{-1}$ )  
a) 18.35 g                      b) 1.835 g                      c) 183.5 g                      d) 0.1835 g
19. Three resistors each of 2 ohm are connected together in a triangular shape. The resistance between any two vertices will be  
a)  $4/3\ \text{ohm}$                       b)  $3/4\ \text{ohm}$                       c)  $3\ \text{ohm}$                       d)  $6\ \text{ohm}$
20. Two different conductors have same resistance at  $0^\circ\text{C}$ . It is found that the resistance of the first conductor at  $t_1^\circ\text{C}$  is equal to the resistance of the second conductor at  $t_2^\circ\text{C}$ . The ratio of the temperature coefficients of resistance of the conductors,  $\frac{\alpha_1}{\alpha_2}$  is  
a)  $\frac{t_1}{t_2}$                       b)  $\frac{t_2 - t_1}{t_2}$                       c)  $\frac{t_2 - t_1}{t_1}$                       d)  $\frac{t_2}{t_1}$