

DPP

DAILY PRACTICE PROBLEMS

CLASS : XIITH
DATE :

Solutions

SUBJECT : PHYSICS
DPP NO. : 2

Topic :- Current Electricity

- 1 (a)
Ammeter is always connected in series and voltmeter in parallel.


2 (a)

$$S = \frac{G}{\frac{i}{i_g} - 1} = \frac{25}{\frac{5}{50 \times 10^{-6}} - 1} = \frac{25}{10^5 - 1} = \frac{25}{10^5} = 2.5 \times 10^{-4} \Omega$$

3 (a)

$$\begin{aligned} \text{Potential gradient} &= \frac{V}{L} = \frac{iR}{L} = \frac{i\rho L}{AL} = \frac{i\rho}{A} \\ &= \frac{0.2 \times 40 \times 10^{-8}}{8 \times 10^{-6}} = 10^{-2} \text{V/m} \end{aligned}$$

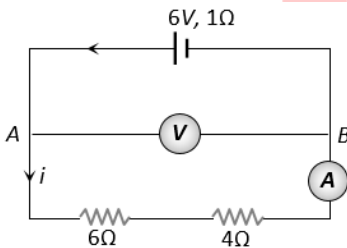- 4 (c)
The given circuit can be redrawn as follows



$$\text{Current } i = \frac{6}{6 + 4 + 1} = \frac{6}{11} \text{A}$$

$$\text{P.D. between A and B, } V = \frac{6}{11} \times 10 = \frac{60}{11} \text{V}$$

- 5 (b)
1 division = $1 \mu\text{A}$
Current for $1^\circ\text{C} = \frac{40 \mu\text{V}}{10} = 4 \mu\text{A}$
 $1 \mu\text{A} = \frac{1}{4} ^\circ\text{C} = 0.25^\circ\text{C}$

- 6 (a)
Two resistances of each side of triangle are connected in parallel. Therefore, the effective

resistance of each arm of the triangle would be $= \frac{r \times r}{r+r} = \frac{r}{2}$. The two arms AB and AC are in series and they together are in parallel with third one.

$$\therefore R'(r/2) + (r/2) = r$$

Total resistance

$$\frac{1}{R} = \frac{1}{r} + \frac{2}{r} = \frac{3}{r}$$

$$R = r/3$$

7

(d)

$$I = neAv_d$$

$$\text{or } v_d = \frac{1}{neA}$$

$$\text{or } v_d \propto \frac{I}{A}$$

$$\therefore \frac{v'd}{vd} = \frac{I'/A'}{I/A} = \frac{2I/2A}{I/A} = 1$$

$$\text{or } v'd = v_d = v$$

8

(d)

Let the resistance of the wire be R , then we know that resistance is proportional to the length of the wire. So each of the four wires will have $R/4$ resistance and they are connected in parallel. So the effective resistance will be

$$\frac{1}{R_1} = \left(\frac{4}{R}\right) \Rightarrow R_1 = \frac{R}{16}$$

9

(b)

By Faraday's law, $m \propto it$

$$\therefore \frac{m_1}{m_2} = \frac{i_1 t_1}{i_2 t_2} \Rightarrow \frac{m}{m_2} = \frac{4 \times 120}{6 \times 40} \Rightarrow m_2 = \frac{m}{2}$$

10

(d)

$$1 \text{ coulomb} \times 1 \text{ volt} = 1 \text{ joule}$$

Hence, option (d) is incorrect.

11

(a)

$$\frac{i}{i_g} = 1 + \frac{G}{S} \Rightarrow \frac{i.G}{V_g} = 1 + \frac{G}{S} \Rightarrow \frac{100 \times 10^{-3} \times 40}{800 \times 10^{-3}} = 1 + \frac{40}{S}$$

$$\Rightarrow S = 10\Omega$$

12

(a)

This is a balanced Wheatstone bridge. Therefore no current will flow from the diagonal resistance 10Ω

$$\therefore \text{Equivalent resistance} = \frac{(10+10) \times (10+10)}{(10+10) + (10+10)} = 10\Omega$$

13

(a)

$$E = at + \frac{1}{2}bt^2 \quad \dots(i)$$

Differentiating Eq. (i), w.r.t, t

We have

$$\frac{dE}{dt} = a + bt$$

When $t = t_n$, ie, neutral temperature, then

$$\frac{dE}{dt} = 0$$

$$\therefore 0 = a + bt_n \text{ or } t_n = -\frac{a}{b}$$

The temperature of inversion

$$t_i = 2t_n = t_0$$

$$= 2t_n - 0 = -\frac{2a}{b}$$

Thermoelectric power

$$P = \frac{dE}{dt} = a + bt$$

14

(c)Since, charge (q)=current (i) \times times (t)

Therefore, charge is equal to area under the curve.

$$\therefore \text{Ist rectangle} = q = lb = 2$$

$$\text{IInd rectangle} = q = lb = 2$$

$$\text{IIIrd triangle} = q = \frac{1}{2}lb = 2$$

Hence, ratio is 1:1:1.

15

(b)

The internal resistance of battery is given by

$$r = \left(\frac{E}{V} - 1\right)R = \left(\frac{40}{30} - 1\right) \times 9 = \frac{9 \times 10}{30} = 3\Omega$$

16

(a)

$$\text{Conductivity } \sigma = \frac{1}{\rho} \quad \dots(i)$$

$$\text{and conductance } G = \frac{1}{R}$$

$$\Rightarrow GR = 1 \quad \dots(ii)$$

$$\text{From equation (i) and (ii) } \sigma = \frac{GR}{\rho}$$

18

(d)Let the current in 12Ω resistance is i Applying loop theorem in closed mesh $AEFCA$

$$12i = -E + E = 0$$

$$\therefore i = 0$$

19 **(b)**

$$P \propto V^2 \Rightarrow \frac{P}{P_0} = \left(\frac{V}{V_0}\right)^2 \Rightarrow P = \left(\frac{V}{V_0}\right)^2 P_0$$

20 **(a)**

$$P = \frac{V^2}{R} \Rightarrow \frac{P_P}{P_S} = \frac{R_S}{R_P} = \frac{(R_1 + R_2)}{R_1 R_2 / (R_1 + R_2)} = \frac{(R_1 + R_2)^2}{R_1 R_2}$$
$$\Rightarrow \frac{100}{25} = \frac{(R_1 + R_2)^2}{R_1 R_2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{1}$$

PE

| ANSWER-KEY | | | | | | | | | | |
|------------|----|----|----|----|----|----|----|----|----|----|
| Q. | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 |
| A. | A | A | A | C | B | A | D | D | B | D |
| | | | | | | | | | | |
| Q. | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 |
| A. | A | A | A | C | B | A | A | D | B | A |
| | | | | | | | | | | |

PE