

# DPP

DAILY PRACTICE PROBLEMS

CLASS : XII<sup>TH</sup>  
DATE :


Solutions

SUBJECT : PHYSICS  
DPP NO. : 3

## Topic :- Current Electricity

- 1 (c)  
For semiconductors, resistance decreases on increasing the temperature

- 2 (b)  
Given circuit is equivalent to

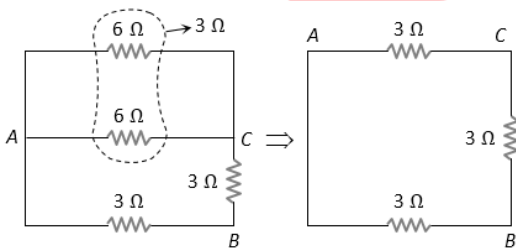

So the equivalent resistance between points A and B is equal to

$$R = \frac{6 \times 3}{6 + 3} = 2\Omega$$

- 3 (d)  
Energy consumed in kWh =  $\frac{\text{watt} \times \text{hour}}{1000}$   
 $\Rightarrow$  For 30 days,  $P = \frac{10 \times 50 \times 10}{1000} \times 30 = 150\text{kWh}$

- 4 (a)  
Ammeter is always connected in series and Voltmeter is always connected in parallel

- 5 (c)  
$$It = \frac{m}{z} = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7}}$$
$$= \frac{5 \times 10^4}{3.387 \times 60 \times 60} \text{Ah} = 4.1 \text{Ah}$$

6

**(d)**

$$\frac{R_1}{R_2} = \frac{(1 + \alpha t_1)}{(1 + \alpha t_2)} \Rightarrow \frac{5}{6} = \frac{(1 + \alpha \times 50)}{(1 + \alpha \times 100)} \Rightarrow \alpha = \frac{1}{200} \text{ per } ^\circ\text{C}$$


Again by  $R_t = R_0(1 + \alpha t)$

$$\Rightarrow 5 = R_0 \left( 1 + \frac{1}{200} \times 50 \right) \Rightarrow R_0 = 4\Omega$$

7

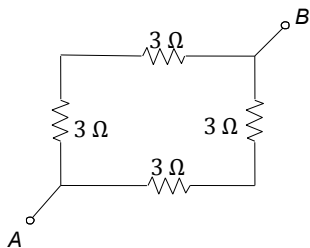
**(d)**

Given, the resistance of wire  $R=12\Omega$ . The wire is bent in square form



$$R_1 = 3 + 3 = 6\Omega$$

$$R_2 = 3 + 3 = 6\Omega$$

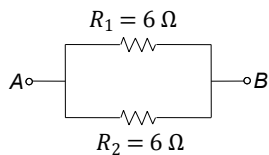

$$\frac{1}{R'} = \frac{1}{6} + \frac{1}{6}$$

$$\text{or } \frac{1}{R'} = \frac{2}{6}$$

$$\text{or } R' = 3\Omega$$

8

**(a)**

$$\text{Chemical equivalent of gold} = \frac{197.1}{3} = 65.7$$

$$\text{Gold to be deposited} = \frac{200 \times 5}{100} = 10\text{g}$$

Electrochemical equivalent of gold

$$z_2 = \frac{W_2}{W_1} z_1 z_2 = \frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \text{gC}^{-1}$$

$$\text{Also } m = zlt, t = \frac{m}{zl}$$

$$\Rightarrow = \frac{10}{\left( \frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \times 2 \right)}$$

$$= 7347.9\text{s}$$


9

**(d)**

$$I^2 \times 6 = 60 \text{ or } I = \sqrt{10} \text{ A}$$

Current through upper branch =  $2\sqrt{10}$  A. Heat produced per second  $3\Omega = (2\sqrt{10})^2 \times 3 \text{ cal} = 120 \text{ cal}$ .

10 (c)

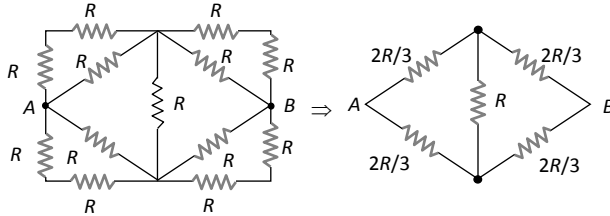

Hence  $R_{eq} = \frac{2R}{3}$  [Since it's a balanced Wheatstone bridge]

11 (d)

Because cell is in open circuit

14 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{ m/s}$$

15 (b)

Let  $R$  be the resistance of each lamp and  $V$  be the voltage supplied to the circuit. Current in the circuit is

$$I_1 = \frac{V}{R + \frac{R \times R}{R + R}} = \frac{2V}{3R}$$

Current flowing through  $B$  or  $C$ ,

$$I_2 = \frac{I_1}{2} = \frac{1}{2} \left( \frac{2V}{3R} \right) = \frac{V}{3R}$$

When  $C$  is fused, the whole current flows through  $A$  and  $B$ .

Then,  $I_2' = V/2R$

So current through  $A$  decreases and current through  $B$  increases. Therefore brilliance of  $A$  decreases and that of  $B$  increase.

16 (c)

As for an electric appliance  $R = \frac{V^2}{P}$ .

For first bulb, its resistance

$$R_1 = \frac{V^2}{P_1} = \frac{250 \times 250}{100} = 625 \Omega$$

For second bulb, its resistance

$$R_2 = \frac{V_2^2}{P_2} = \frac{200 \times 200}{100} = 400 \Omega$$

Now, in series potential divides in proportion to resistance.

$$\text{So, } V_2 = \frac{R_2}{(R_1 + R_2)} V$$

Where  $V$  is supply voltage.

$\therefore$  Potential drop across bulb  $B_2$ .

$$\begin{aligned} V_2 &= \frac{400}{(625 + 400)} \times 250 \\ &= 97.56 \text{ V} \\ &= 98 \text{ V} \end{aligned}$$

17 **(d)**


Equivalent weight of aluminium  $= \frac{27}{3} = 9$

So 1 faraday = 96500 C are required to liberate 9 gm of Al

18 **(a)**

In the following circuit potential difference between

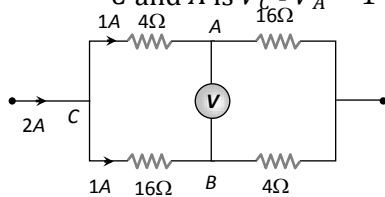C and A is  $V_C - V_A = 1 \times 4 = 4 \dots(i)$




C and B is  $V_C - V_B = 1 \times 16 = 16 \dots(ii)$

On solving equations (i) and (ii) we get

$$V_A - V_B = 12V$$

19 **(a)**

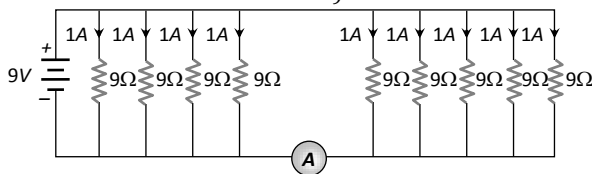Equivalent resistance  $R = \frac{9}{9} = 1\Omega$



Current  $i = \frac{9}{1} = 9A$

Current passing through the ammeter = 5A

20 **(b)**

$$\text{Power, } P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{(60)^2}{160} = 22.5\Omega$$

Now, according to Ohm's law

$$V = IR$$

$$\therefore I = \frac{60}{22.5}$$

$$\Rightarrow I = 2.6A$$

Here,  $t = 60s$

$$\text{As } I = \frac{ne}{t}$$

$$\Rightarrow n = \frac{I \times t}{e}$$

$$= \frac{26 \times 60}{1.6 \times 10^{-19}} \approx 10^{21}$$

PE

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	C	B	D	A	C	D	D	A	D	C
Q.	11	12	13	14	15	16	17	18	19	20
A.	D	C	B	C	B	C	D	A	A	B

PE