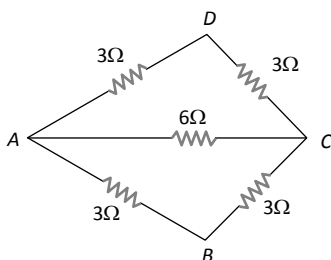





Topic :- Current Electricity


1. For which of the following the resistance decreases on increasing the temperature
a) Copper b) Tungsten c) Germanium d) Aluminium

2. The effective resistance between the points *A* and *B* in the figure is




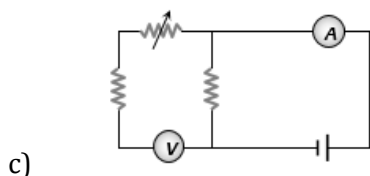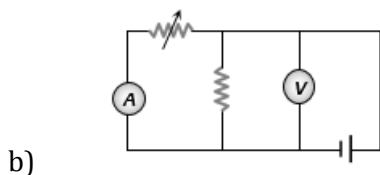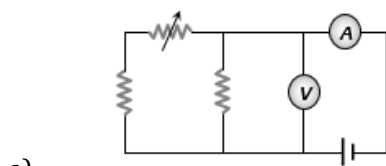- a) 5Ω b) 2Ω c) 3Ω d) 4Ω
3. How much energy in kilowatt hour is consumed in operating ten 50 watt bulbs for 10 hours per day in a month (30 days)
a) 1500 b) 5,000 c) 15 d) 150
4. Express which of the following setups can be used to verify Ohm's law




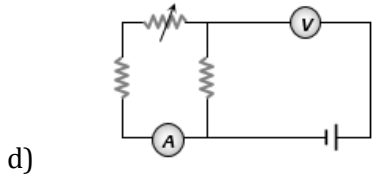

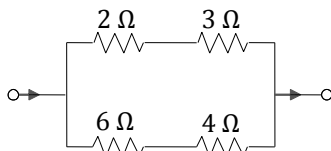5. If in a voltaic cell, 5 g of zinc is consumed, we will get how many ampere hour (given that ECE of zinc is $3.38 \times 10^{-7} \text{kgC}^{-1}$)
 a) 2.05 b) 8.2 c) 4.1 d) $5 \times 3.338 \times 10^{-7}$
6. The resistance of a conductor is 5 ohm at 50°C and 6 ohm at 100°C . Its resistance at 0°C is
 a) 1 ohm b) 2 ohm c) 3 ohm d) 4 ohm
7. A metallic wire of resistance 12Ω is bent to form a square. The resistance between two diagonal points would be
 a) 12Ω b) 24Ω c) 6Ω d) 3Ω
8. A piece of metal weighing 200 g is to be electroplated with 5% of its weight in gold. How long it would take to deposit the required amount of gold, if the strength of the available current is 2 A?
 (Given, electrochemical equivalent of H = $0.0104 \times 10^{-4} \text{gC}^{-1}$ atomic weight of gold = 197.1, atomic weight of hydrogen = 1.008)
 a) 7347.9 s b) 7400.5 s c) 7151.7 s d) 70 s
9. In the circuit shown in figure, the heat produced by the 6Ω resistance is 60 cal s^{-1} . What heat per second is produced across 3Ω resistance?




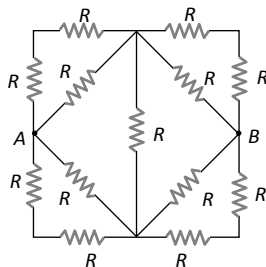- a) 30 cal b) 60 cal c) 100 cal d) 120 cal
10. Thirteen resistance each of resistance R ohm are connected in the circuit as shown in the figure below. The effective resistance between A and B is



- a) $2R \Omega$ b) $\frac{4R}{3} \Omega$ c) $\frac{2R}{3} \Omega$ d) $R \Omega$

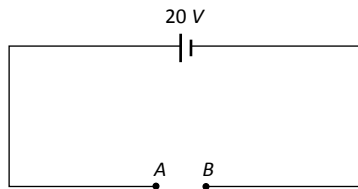11. In the shown circuit, what is the potential difference across A and B



- a) 50 V b) 45 V c) 30 V d) 20 V

12. The internal resistance of a cell is the resistance of

- a) Electrodes of the cell b) Vessel of the cell
c) Electrolyte used in the cell d) Material used in the cell


13. In potentiometer a balance point is obtained, when

- a) The e.m.f. of the battery becomes equal to the e.m.f. of the experimental cell
b) The p.d. of the wire between the +ve end to jockey becomes equal to the e.m.f. of the experimental cell
c) The p.d. of the wire between +ve point and jockey becomes equal to the e.m.f. of the battery
d) The p.d. across the potentiometer wire becomes equal to the e.m.f. of the battery


14. A conductor wire having 10^{29} free electrons/ m^3 carries a current of 20 A . If the cross-section of the wire is 1 mm^2 , then the drift velocity of electrons will be

- a) $6.25 \times 10^{-3}\text{ ms}^{-1}$ b) $1.25 \times 10^{-5}\text{ ms}^{-1}$ c) $1.25 \times 10^{-3}\text{ ms}^{-1}$ d) $1.25 \times 10^{-4}\text{ ms}^{-1}$

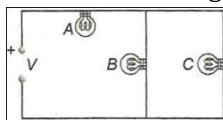15. Figure shown three similar lamps A, B and C connected across a power supply. If the lamp C fuses, how will the light emitted by A and B change?




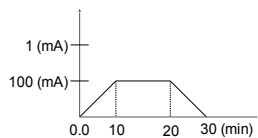- a) No change b) Brilliance of A decreases and that of B increases



- c) Brilliance of both A and B increases d) Brilliance of both A and B decreases

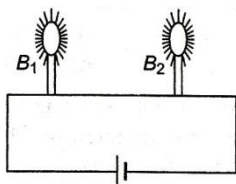
16. Bulb B_1 ($100\text{ W}-250\text{ V}$) and bulb B_2 ($100\text{ W}-200\text{ V}$) are connected across 250 V . What is potential drop across B_2 ?



- a) 200 V b) 250 V c) 98 V d) 48 V


17. The amount of charge required to liberate 9 gm of aluminium (atomic weight = 27 and valency = 3) in the process of electrolysis is (Faraday's number = 96500 coulombs/gm equivalent)
 a) 321660 coulombs b) 69500 coulombs c) 289500 coulomb d) 96500 coulomb

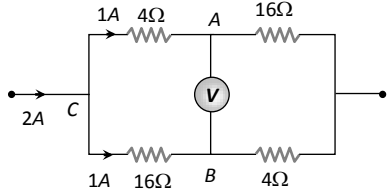18. In the circuit shown below, the reading of the voltmeter V is



- a) 12 V b) 8 V c) 20 V d) 16 V

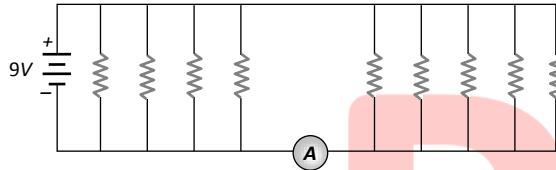19. If each resistance in the figure is of $9\ \Omega$ then reading of ammeter is



- a) 5 A b) 8 A c) 2 A d) 9 A

20. 160W-60V lamp is connected at 60 V DC supply. The number of electrons passing through the lamp in 1 min is (the charge of electron $e = 1.6 \times 10^{-19}\text{C}$)
 a) 10^{19} b) 10^{21} c) 1.6×10^{19} d) 1.4×10^{20}