

DPP

DAILY PRACTICE PROBLEMS

CLASS : XIITH
DATE :

Solutions

SUBJECT : PHYSICS
DPP NO. : 5

Topic :- Current Electricity

1 (a)

In the first case, $Zit = m$

In the second case, $Z \times \frac{i}{4} \times 4t = m$

2 (d)

For conductors, resistance \propto Temperature and for semiconductor, resistance \propto $\frac{1}{\text{Temperature}}$

3 (a)

Since resistance connected in arms CE , ED , CF and FD will form a balanced Wheatstone bridge, therefore, the resistance of arm EF becomes ineffective. Now resistance of arm CED or $CFD = 2 + 2 = 4\Omega$. Effective resistance of these two parallel arm $= \frac{4 \times 4}{4 + 4} = 2\Omega$

Now resistance of arm $ACDB = 2 + 2 + 2 = 6\Omega$, is in parallel with resistance arm $AB = 2\Omega$. Thus, effective resistance between A and B

$$= \frac{6 \times 2}{6 + 2} = \frac{3}{2}\Omega$$

4 (c)

$$i = \frac{dQ}{dt} = \frac{d}{dt}(5t^2 + 3t + 1) = 10t + 3$$

When $t = 5s$, $i = 10 \times 5 + 3 = 53 A$

5 (a)

The current taken by the silver voltmeter

$$I_1 = \frac{n}{Zt} = \frac{1}{11.2 \times 10^{-4} \times 30 \times 60} = 0.496 A$$

and by copper voltmeter

$$I_2 = \frac{1.8}{6.6 \times 10^{-4} \times 30 \times 60} = 1.515 A$$

The current $I = (I_1 + I_2) = 2.011 A$

Power $P = IV = 2.011 \times 12 = 24.132 \text{ J/sec}$

6

(c)

Average current

$$i = \frac{50 + 100 + 50}{3} = \frac{200}{3} \text{ mA}$$

$$z = \frac{m}{it} = \frac{3m}{200 \times 10^{-3} \times 30} = \frac{m}{2}$$

7

(c)

The equivalent current due to motion of electrons is given by

$$I = \frac{e}{t} = \frac{1.6 \times 10^{-19}}{1.594 \times 10^{-18}}$$

$$= 1.0037 \times 10^{-1}$$


$$= 100.37 \times 10^{-3} \text{ A}$$

$$= 100.37 \text{ mA}$$

8

(a)

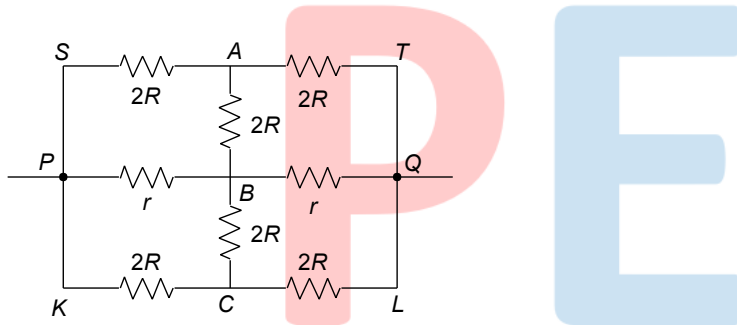In the circuit arrangement $PSTQ$ is a balanced Wheatstone bridge, hence resistance $2R$ joined in arm AB be omitted. Similarly, resistance $2R$ joined in arm BC may also be omitted.



$$\therefore \frac{1}{R_{eq}} = \frac{1}{4R} + \frac{1}{2r} + \frac{1}{4R} = \frac{\mu + 2R + \mu}{4\mu R} = \frac{(R + r)}{2Rr}$$

$$\Rightarrow R_{eq} = \frac{2Rr}{R + r}$$

9

(b)

$$\frac{dT}{dt} = \frac{d}{dt}(at^2 - bt^3) = 2at - 3bt^2$$

When $t = t_n$ (ie, neutral temperature), $\frac{dE}{dt} = 0$

$$\therefore 0 = 2at_n - 3bt_n^2 \text{ or } t_n = \frac{2a}{3b}$$


10

(a)

The circuit may be redrawn as shown in the adjacent figure

$$\text{Here } E_{eq} = 12V, r_{eq} = \frac{2 \times 2}{2 + 2} = 1\Omega$$
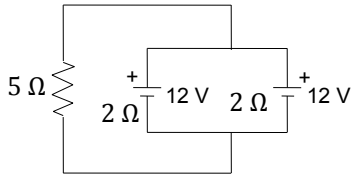
$$i = \frac{E_{\text{eq}}}{R + r_{\text{eq}}} = \frac{12}{5 + 1} = \frac{12}{6} = 2 \text{ A}$$



11 (c)

$$i = nAev_d$$

$$\text{or } v_d = \frac{i}{nAe}$$

Total number of free electrons in the unit length of conductor, $N = nA \times 1$.

Total linear momentum of all free electrons per unit length

$$= (Nm)v_d = nAm \times \frac{i}{nAe} = \frac{i}{(e/m)} = \frac{i}{s}$$

12 (b)


$$\text{As } m = z l t = z \left(\frac{V}{R} \right) t \text{ ie, } m \propto Vt$$

$$\therefore \frac{m_2}{m_1} = \frac{V_2 t_2}{V_1 t_1}$$

$$\text{or } m_2 = \frac{V_2 t_2}{V_1 t_1} \times m_1 = \frac{6 \times 45 \times 2}{12 \times 30} = 1.5 \text{ g.}$$

13 (a)

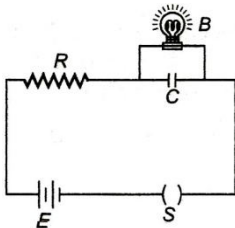Neon bulb is filled with gas, so the resistance is infinite; hence no current flows through it.



$$\text{Now, } V_c = E(1 - e^{-t/RC})$$

$$\Rightarrow 120 = 200(1 - e^{-t/RC})$$

$$\Rightarrow e^{-t/RC} = \frac{2}{5}$$

$$\Rightarrow t = RC \ln 2.5$$


$$\Rightarrow R = \frac{t}{C \ln 2.5} = \frac{5}{2.303 \times 2 \times 10^6 \log 2.5}$$

$$= 2.7 \times 10^6 \Omega$$

14 **(b)**
 $v_d \propto 1/l$. Therefore, drift velocity is halved

15 **(b)**
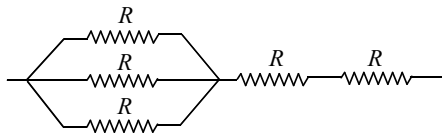
$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$



$$\Rightarrow R_p = \frac{R}{3} \Omega$$

$$\Rightarrow R_s = R + R = 2 R \Omega$$

$$\Rightarrow R_{\text{net}} = R_p + R_s = 2R + \frac{R}{3} = \frac{7R}{3} \Omega$$

16 **(a)**
 The resistivity of metal increases when it is converted into an alloy
 $\therefore \rho' > \rho$

18 **(b)**
 This is because of secondary ionisation which is possible in the gas filled in it


19 **(a)**

Using $R_{T_2} = R_{T_1}[1 + \alpha(T_2 - T_1)]$

$$\Rightarrow R_{100} = R_{50}[1 + \alpha(100 - 50)]$$

$$\Rightarrow 7 = 5[1 + (\alpha \times 50)] \Rightarrow \alpha = \frac{(7 - 5)}{250} = 0.008/^\circ\text{C}$$

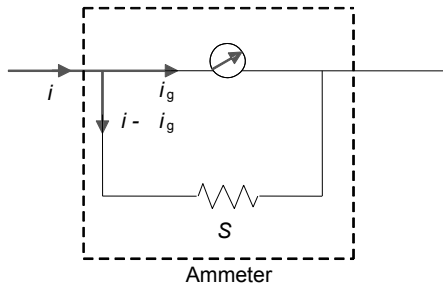20 **(b)**
 Ammeter is made by connecting a low resistance shunt S in parallel with galvanometer G .
 since G and S are in parallel, the potential difference across them is same.



$$i_g \times G = (i - i_g) \times S$$

Given, $G = R, i = 4i_g$

$$S = \frac{i_g}{4i_g - i_g} \times R = \frac{i_g}{3i_g} \times R = \frac{R}{3}$$

PE

ANSWER-KEY

Q.	1	2	3	4	5	6	7	8	9	10
A.	A	D	A	C	A	C	C	A	B	A
Q.	11	12	13	14	15	16	17	18	19	20
A.	C	B	A	B	B	A	A	B	A	B

PE