

# DPP

DAILY PRACTICE PROBLEMS

CLASS : XII<sup>TH</sup>  
DATE :

Solutions

SUBJECT : PHYSICS  
DPP NO. : 6


## Topic :- Current Electricity

1 (a)  
Maximum current flows through bulb (1) Therefore, it will lights brightly.

2 (d)  
$$S = \frac{i_g G}{(i - i_g)} \Rightarrow \frac{G}{S} = \frac{i - i_g}{i_g} = \frac{10 - 1}{1} = \frac{9}{1}$$

4 (d)  
Potentiometer works on null deflection method. In balance condition no current flows in secondary circuit.

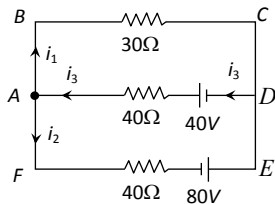6 (b)  
The circuit can be simplified as follows



Applying KCL at junction A

$$i_3 = i_1 + i_2 \quad \dots(i)$$

Applying Kirchhoff's voltage law for the loop ABCDA

$$-30i_1 - 40i_3 + 40 = 0$$

$$\Rightarrow -30i_1 - 40(i_1 + i_2) + 40 = 0$$

$$\Rightarrow 7i_1 + 4i_2 = 4 \quad \dots(ii)$$

Applying Kirchhoff's voltage law for the loop ADEFA

$$-40i_2 - 40i_3 + 80 + 40 = 0$$

$$\Rightarrow -40i_2 - 40(i_1 + i_2) = -120$$

$$\Rightarrow i_1 + 2i_2 = 3 \quad \dots(iii)$$

On solving equation (ii) and (iii)  $i_1 = -0.4A$

- 7 **(c)**  
 From Faraday's law,  $m/E = \text{constant}$   
 where  $m =$  mass of substance deposited,  $E =$  chemical equivalent  
 $\therefore \frac{m_2}{m_1} = \frac{E_2}{E_1} \Rightarrow m_2 = \frac{108}{32} \times 1.6 = 5.4g$
- 8 **(b)**  
 Based on Peltier effect
- 9 **(b)**  
 The current through the voltmeter is same as drawn from the battery outside it
- 10 **(a)**  
 Slope of graph  
 $= \frac{I}{V} = \frac{1}{R}$   
 If experiment is performed at higher temperature then resistance increase and hence slope decrease, choice (a) is wrong.  
 Similarly in choice (b) and (c) resistance increase.  
 But for choice (d) resistance R increases, so slope decreases
- 11 **(d)**  
 Heat produced,  $H = \frac{V^2 t}{R}$ . When voltage is halved, the heat produced becomes one-fourth.  
 Hence time taken to heat the water becomes four time.
- 12 **(c)**  
 $H = \frac{V^2}{R} t \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{4}{2} = \frac{2}{1}$
- 13 **(c)**  
 Given that  
 emf  $E_N = 1.5r_N$   
 Where  $r_N$  is the internal resistance of  $n$ th cell.  
 Total emf  $E = E_1 + E_2 + E_3 + \dots + E_n$   
 $= 1.5[r_1 + r_2 + r_3 + \dots + r_n]$   
 Total internal resistance  
 $r = r_1 + r_2 + r_3 + \dots + r_n$   
 $\therefore$  Current  $i = \frac{E_{\text{total}}}{r_{\text{total}}}$   
 $i = \frac{1.5[r_1 + r_2 + r_3 + \dots + r_n]}{[r_1 + r_2 + r_3 + \dots + r_n]}$   
 Hence,  $i = 1.5A$

14 **(b)**

The given network is a balanced Wheatstone bridge. Its equivalent resistance will be  $R = \frac{18}{5} \Omega$

So current from the battery  $i = \frac{V}{R} = \frac{V}{18/5} = \frac{5V}{18}$

15 **(d)**

The resistance of 40 W bulb will be more and 60 W bulb will be less

16 **(c)**

$$E = aT + bT^2$$


At temperature of inversion,  $E = 0$ ,

$$\therefore aT_i + bT_i^2 = 0$$

$$\Rightarrow T_i = -\frac{a}{b}$$

$$\Rightarrow T_i = -\frac{10 \times 10^{-6}}{(0.02 \times 10^{-6})} = 500^\circ\text{C}$$

17 **(c)**

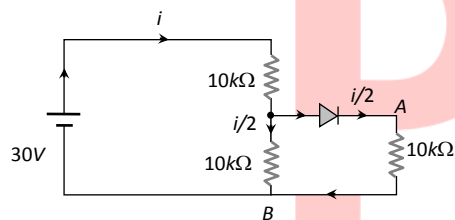

Equivalent resistance  $R = 10 + \frac{10}{2} = 15 \text{ k}\Omega$

Current  $i = \frac{30}{15} = 2 \times 10^{-3} \text{ A}$

Hence, potential difference between A and B

$$V = \left(\frac{2 \times 10^{-3}}{2}\right) \times 10 \times 10^3 = 10 \text{ Volt}$$

18 **(b)**

Let the potential difference across battery is  $V$  and internal resistance of the cell is  $r$ , then

$$E = V + ir \quad \dots(i)$$

$$V = iR \quad \dots(ii)$$

Now, from Eqs. (i) and (ii) we have

$$E = iR + ir = i(R + r) \quad \dots(iii)$$

Now, dividing Eq. (iii) by Eq. (ii), we get

$$\frac{E}{V} = \frac{R + r}{R} = 1 + \frac{r}{R}$$

$$\frac{E}{V} - 1 = \frac{r}{R}$$

$$\text{or } \left(\frac{E - V}{V}\right)R = r$$

Hence, internal resistance


$$r = \left(\frac{E - V}{V}\right)R$$

20

**(b)**

In the given circuit, resistors  $4R$  and  $2R$  are connected in parallel while resistance  $R$  is connected in series to it.

Hence, equivalent resistance is

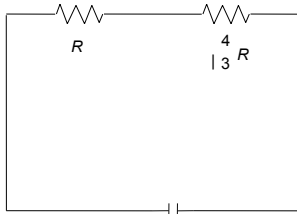

$$\frac{1}{R'} = \frac{1}{4R} + \frac{1}{2R}$$

$$= \frac{6R}{8R^2}$$


$$R' = \frac{8}{6}R$$

$$= \frac{4}{3}R$$

$$\Rightarrow R'' = R + \frac{4}{3}R = \frac{7R}{3}$$

Given, emf is  $E$  volts, therefore

$$i = \frac{E}{R} = \frac{3E}{7R}$$

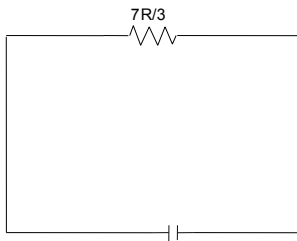

Potential difference across  $R$  is

$$V = ir = \frac{3R}{7R} \times R = \frac{3E}{7}$$

Potential difference across  $2R$  is

$$V' = E - \frac{3E}{7} = \frac{4E}{7}$$

PE

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	A	D	A	D	D	B	C	B	B	A
Q.	11	12	13	14	15	16	17	18	19	20
A.	A	D	C	B	D	C	C	B	B	B

PE