

# DPP

DAILY PRACTICE PROBLEMS


CLASS : XII<sup>TH</sup>  
DATE :

Solutions

SUBJECT : PHYSICS  
DPP NO. : 8
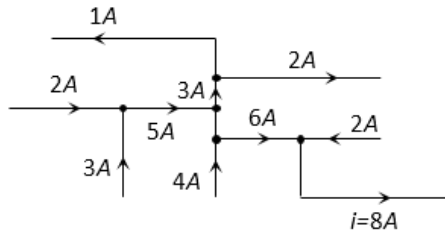
## Topic :- Current Electricity

- 1 (b)  
By using Kirchoff's junction law as shown below




We get  $i = 8A$

- 2 (a)  
$$I = \frac{dq}{dt} = 3t^2 + 2t + 5$$
$$\therefore dq = (3t^2 + 2t + 5)dt$$
$$\therefore q = \int_{t=0}^{t=2} (3t^2 + 2t + 5)dt$$
$$= \frac{3t^3}{3} + \frac{2t^2}{2} + 5t \Big|_0^2 = t^3 + t^2 + 5t \Big|_0^2 = 22 C$$

- 3 (a)  
$$\frac{i}{i_g} = \frac{G + S}{S} \Rightarrow \frac{i_g}{i} = \frac{S}{G + S} = \frac{2.5}{27.5} = \frac{1}{11}$$

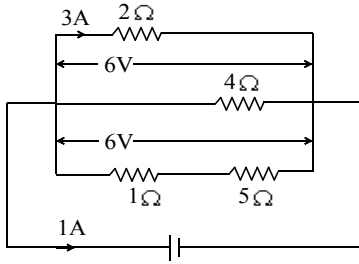- 4 (b)  
Current flowing through  $2\Omega$  resistance is  $3A$ , so P.D. across it is  $3 \times 2 = 6V$   
Current through the bottom line  $= \frac{6}{1+5} = 1A$   
 $\therefore$  Power dissipated in  $5\Omega$  resistance is  
 $P = i^2R = (1)^2 \times 5 = 5W$



5

**(a)**

We know that thermoelectric power

$$S = \frac{dE}{dT}$$

$$\text{Given, } E = K(T - T_r) \left[ T_0 - \frac{1}{2}(T + T_r) \right]$$

By differentiating the above equation w.r.t.  $T$  and putting  $T = \frac{1}{2}T_0$ , we get  $S = \frac{1}{2}kT_0$

6

**(d)**

Three resistances are in parallel,

$$\therefore \frac{1}{R'} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$

The equivalent resistance

$$R' = \frac{R}{3} \Omega = \frac{6}{3} = 2\Omega$$

8

**(a)**

Internal resistance of the cell

$$r = \left[ \frac{E}{V} - 1 \right] R$$

$$r = \left[ \frac{1.5}{1.4} - 1 \right] 14 = 1\Omega$$

9

**(c)**

From Kirchhoff's second law

$$V = \sum ir \quad (\text{for closed mesh})$$

Where  $V$  is potential difference,  $i$  the current and  $r$  the resistance.

$$\therefore E + E = Ir + Ir = 2Ir$$

$$\text{or } I = \frac{E}{r} \quad \dots(i)$$

$$V_x - V_y = E - Ir$$

Putting the value of  $I$  from Eq (i), we get

$$V_x - V_y = E - \frac{E}{r} \times r = 0$$

10 (c)

$$\text{Here, } \frac{P}{Q} = \frac{2}{3}$$

we know

$$\frac{P}{Q} = \frac{l}{100 - l}$$

$$\Rightarrow \frac{2}{3} = \frac{l}{100 - l}$$

$$\Rightarrow l = 40 \text{ cm}$$

11 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{ m/s}$$

12 (b)

Total resistance

$$\text{Or } R = 20 + 40$$

$$R = 60 \Omega$$

Given  $G = 15 \text{ V}$

$$\text{Current } I = \frac{V}{R} = \frac{15}{60}$$

$$I = 0.25 \text{ A}$$

$$\text{Potential gradient} = \frac{V}{l}$$

$$= \frac{20 \times 0.25}{10} = 0.5 \text{ Vm}^{-1}$$

PD across 240 cm

$$E = 0.5 \times 2.4$$

$$E = 1.2 \text{ V}$$

13 (a)



Equivalent resistance of the given network

$$R_{\text{eq}} = 75 \Omega$$

$\therefore$  Total current through battery,

$$i = \frac{3}{75}$$
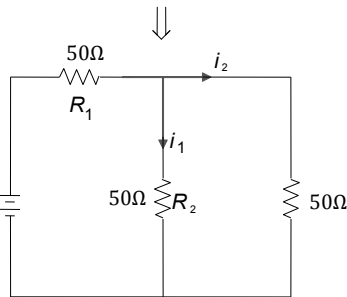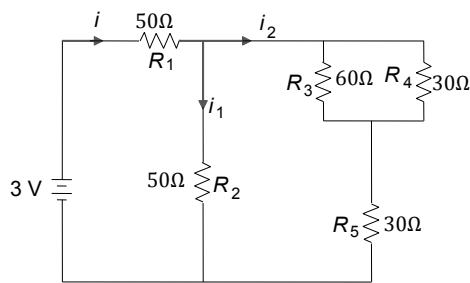
$$i_1 = i_2 = \frac{3}{75 \times 2} = \frac{3}{150}$$



Current through resistance

$$\begin{aligned}
 i_4 &= \frac{3}{150} \times \frac{60}{(30 + 60)} \\
 &= \frac{3}{150} \times \frac{60}{90} \\
 &= \frac{2}{150} \text{ A} \\
 V_4 &= i_4 \times R_4 \\
 &= \frac{2}{150} \times 30 \\
 &= \frac{2}{5} = 0.4 \text{ volt}
 \end{aligned}$$

PE

- 14 (c) Current through a conductor is constant at even cross-section of the conductor

- 15 (c) Mass deposited = density  $\times$  volume of the metal

$$m = \rho \times A \times X \quad \dots(i)$$


$$\text{Hence from Faraday's first law } m = Zit \quad \dots(ii)$$

So from equation (i) and (ii)

$$Zit = \rho \times Ax \Rightarrow x = \frac{Zit}{\rho A}$$

$$= \frac{3.04 \times 10^{-4} \times 10^{-3} \times 1 \times 3600}{9000 \times 0.05} = 2.4 \times 10^{-6} \text{ m} = 2.4 \mu\text{m}$$

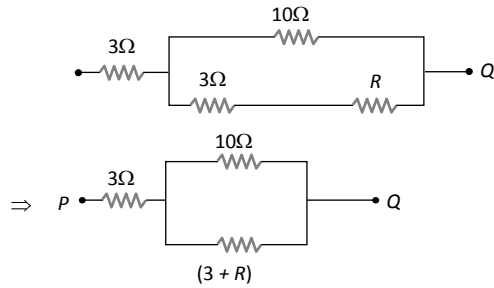- 17 (c) The given circuit can be simplified as follows



$$R = 3 + \frac{10 \times (3 + R)}{10 + 3 + R} = 3 + \frac{30 + 10R}{13 + R}$$

$$R = \frac{39 + 3R + 30 + 10R}{13 + R} = \frac{69 + 13R}{13 + R}$$

$$13R + R^2 = 69 + 13R \Rightarrow R = \sqrt{69} \Omega$$

18 **(b)**  
 $R \propto l^2 \Rightarrow$  If  $l$  doubled then  $R$  becomes 4 times

19 **(c)**  
 Ammeter is used to measure the current through the circuit

20 **(b)**  
 $i = \frac{E}{r + R} \Rightarrow P = i^2 R \Rightarrow P = \frac{E^2 R}{(r + R)^2}$   
 Power is maximum when  $r = R \Rightarrow P_{\max} = E^2 / 4r$

<b>ANSWER-KEY</b>										
Q.	1	2	3	4	5	6	7	8	9	10
A.	B	A	A	B	A	D	B	A	C	C
Q.	11	12	13	14	15	16	17	18	19	20
A.	C	B	A	C	C	C	C	B	C	B

PE