

# DPP

DAILY PRACTICE PROBLEMS

CLASS : XII<sup>TH</sup>  
DATE :


Solutions

SUBJECT : PHYSICS  
DPP NO. : 9

## Topic :- Current Electricity

1 (c)  
 $\theta_0 = 2\theta_n - \theta_i = 2 \times 210 - (600 - 273)$   
 $= 420 - 327 = 93^\circ\text{C}$

2 (c)  
Let the circuit be as shown

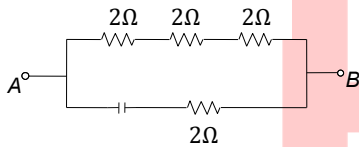

Equivalent resistance between A and B is

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{(2 + 2 + 2)} = \frac{2}{3}$$

$$R = \frac{3}{2} = 1.5\Omega$$

Therefore, 4 resistances are required.

3 (b)

$$\frac{r_{\text{iron}}}{r_{\text{Copper}}} = \sqrt{\frac{\rho_{\text{iron}}}{\rho_{\text{Copper}}}} = \sqrt{\frac{1 \times 10^{-7}}{1.7 \times 10^{-8}}} = 2.4$$

4 (c)  
For a fuse  $I^2 \propto r^3$

$$\therefore \frac{I_1^2}{I_2^2} = \frac{r_1^3}{r_2^3}$$

$$\frac{3^2}{I_2^2} = \left(\frac{0.02}{0.03}\right)^3$$

$$I_2 = 3 \times \left(\frac{3}{2}\right)^{3/2} \text{A}$$

- 5 **(d)**  
Let  $n$  cells be in series and  $m$  in parallel, then

$$\frac{nE}{R + nr} = \frac{E}{R + \frac{r}{m}}$$
$$\Rightarrow n\left[R + \frac{r}{m}\right] = R + nr$$
$$\Rightarrow nRm + nr = Rm + mn r$$
$$\Rightarrow 6 + 2r = 3 + 4r$$
$$\Rightarrow 2r = 3$$
$$\Rightarrow r = 1.5\Omega$$

- 6 **(a)**  
The ratio  $\frac{AC}{CB}$  will remain unchanged.

- 7 **(b)**  
 $V_2 - V_1 = E - ir = 5 - 2 \times 0.5 = 4 \text{ volt}$   
 $\Rightarrow V_2 = 4 + V_1 = 4 + 10 = 14 \text{ volt}$

- 8 **(a)**  
Power in electric bulb

$$P = \frac{V^2}{R}$$

So, resistance of electric bulb

$$R = \frac{V^2}{P}$$

Given,  $P_1 = 25 \text{ W}$ ,  $P_2 = 100 \text{ W}$ ,

$V_1 = V_2 = 220 \text{ volt}$

Therefore, for same potential difference  $V$

$$R \propto \frac{1}{P}$$

Thus, we observe that for minimum power, resistance will be maximum and *vice - versa*.

Hence, resistance of 25 W bulb is maximum and 100 W bulb is minimum.

- 9 **(c)**

Let temperature of cold junction be  $0^{\circ}\text{C}$  and that of hot junction be  $T^{\circ}\text{C}$ . The relation for thermo-emf is given by

$$E = AT - \frac{1}{2} BT^2$$

Given,  $A = 16, B = 0.08$

$$\therefore E = 16T - \frac{1}{2} \times 0.08 \times T^2$$

Since, at temperature of inversion emf is zero, we have


$$0 = 16T - 0.04 T^2$$

$$\Rightarrow T = \frac{16}{0.04} = 400^{\circ}\text{C}$$

10

**(c)**

The equivalent circuit can be redrawn as

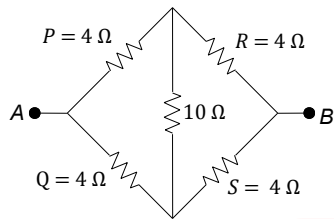

we have,  $\frac{P}{Q} = \frac{R}{S}$

$$ie, \quad \frac{4}{4} = \frac{4}{4}$$

So, the given circuit is a balanced Wheatstone's bridge.

Hence, the equivalent resistance

$$\begin{aligned} R_{AB} &= \frac{(4 + 4) \times (4 + 4)}{(4 + 4) + (4 + 4)} \\ &= \frac{8 \times 8}{8 + 8} = \frac{64}{16} = 4\Omega \end{aligned}$$

11

**(b)**

Force = Electric intensity  $\times$  charge

$$= \frac{\text{Potential difference}}{\text{distance}} \times \text{charge}$$

$$\therefore 4.8 \times 10^{-19} = \frac{V}{5} \times 1.6 \times 10^{-19}$$

or  $V = 15$  volt

12

**(d)**

In stretching of wire  $R \propto \frac{1}{d^4}$ , where  $d$  = Diameter of wire

13

**(d)**

Total current through the circuit

$$i = \frac{10}{\frac{1000}{3} + 500} = \frac{3}{250} A$$

$$\text{Now voltmeter reading} = i_v \times R_V = \frac{2}{3} \times \frac{3}{250} \times 500 = 4V$$

14 **(b)**

$$E = xl = \frac{V}{l} = \frac{iR}{L} \times l \Rightarrow E = \frac{r}{(R + R_h + r)} \times \frac{R}{L} \times l$$

$$\Rightarrow E = \frac{10}{(5 + 4 + 1)} \times \frac{5}{5} \times 3 = 3V$$

15 **(c)**

$$i = nAev_d$$

$$\text{or } v_d = \frac{i}{nAe}ie, v_d \propto \frac{1}{A}$$

As  $A$  increases  $v_d$  decreases, because  $i$  remains constant

16 **(a)**

$R = \rho l/A$  or  $R \propto l/A$ . Thus, resistance is least in a wire of length  $L/2$  and area of cross-section  $2A$

17 **(c)**

$$V_d = \frac{i}{nAe} = \frac{5.4}{8.4 \times 10^{28} \times 10^{-6} \times 1.6 \times 10^{-19}}$$

$$= 0.4 \times 10^{-3} \text{ m/sec} = 0.4 \text{ mm/sec}$$

18 **(c)**

The power of the battery, when charged, is given by

$$P_1 = V_1 I_1$$

The electrical energy dissipated is given by  $E_1 = P_1 t_1$

$$\text{i.e., } E_1 = V_1 I_1 t_1 = 15 \times 10 \times 8 = 1200 \text{ Wh}$$

Similarly, the electrical energy dissipated during the discharge a battery is given by,

$$E_2 = V_2 I_2 t_2 = 14 \times 5 \times 15 = 1050 \text{ Wh}$$

Hence, watt-hour efficiency of the battery is given by

$$\eta = \frac{E_2}{E_1} \times 100 = 0.875 \times 100 = 87.5\%$$

19 **(d)**

Total power spend across two resistors connected

$$\text{in parallel to battery} = \frac{V^2}{R_1} + \frac{V^2}{R_2}$$

$$= \frac{3 \times 3}{2} + \frac{3 \times 3}{2/3} = \frac{36}{2} = 18$$

$$= 3 \times 3 \times 2 \text{ J}$$

20 **(b)**

$$\text{Conductance } C = \frac{1}{R} = \frac{A}{\rho l} \Rightarrow C \propto \frac{1}{l}$$

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	C	C	B	C	D	A	B	A	C	C
Q.	11	12	13	14	15	16	17	18	19	20
A.	B	D	D	B	C	A	C	C	D	B

PE