


Class : XIIth Date : Subject : PHYSICS DPP No. : 4

## **Topic :-**.ELECTROSTATIC POTENTIAL AND CAPACITANCE

1. If the potential of a capacitor having capacity  $6\mu F$  is increased from 10 V to 20 V, then increase in its energy is

a) 
$$12 \times 10^{-6}$$
 J b)  $9 \times 10^{-4}$  J c)  $4.5 \times 10^{-6}$  J d)  $2.25 \times 10^{-6}$  J

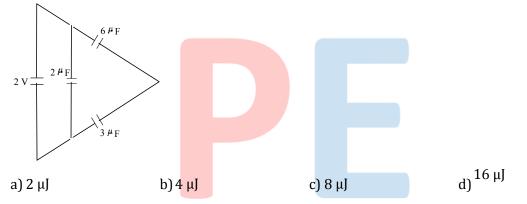2. The total energy stored in the condenser system shown in the figure will be



- 3. Two free protons are separated by a distance of 1 Å. If one proton is kept at least and the other<br/>is released, the kinetic energy of second proton when at infinite sparation is<br/>a)  $23.0 \times 10^{-19}$  J<br/>b)  $11.5 \times 10^{-19}$  J<br/>c)  $2.3 \times 10^{-19}$  J<br/>d) Zero
- 4. The work done in bringing a unit positive charge from infinity distance to a point at distance X from a positive charge Q is W. Then, the potential dat the point is

a) 
$$\frac{WQ}{X}$$
 b)  $W$  c)  $\frac{W}{Q}$  d)  $WQ$ 

5. An electric field is given by  $\vec{E} = (y\hat{i} + x\hat{j})m$  NC<sup>-1</sup>. The work done in moving a 1 C charge from  $\vec{r}_A = (2\hat{i} + 2\hat{j})m$  to  $\vec{r}_B = (4\hat{i} + 2\hat{j})m$  is

a) 
$$+8J$$
 b)  $+4J$  c) Zero d)  $-4J$   
The equivalent capacity between points  $4$  and  $B$  in figure will be while capacitance of each  $-4J$ 

6. The equivalent capacity between points *A* and *B* in figure will be, while capacitance of each capacitor is  $3 \mu$ F.

a) 2 
$$\mu$$
F b) 4  $\mu$ F c) 7  $\mu$ F d) 9  $\mu$ F

	7.	27 identical drops of mercury are charged simultaneously to the same potential of 10 V each. Assuming drops to be spherical, if all the charged drops are made to combine to form one large drop, then the potential of larger drop would be				
		a) 45 V	b)135	c) 270 V	d)90 V	
	8.	A soap bubble is charged to a potential of 16V. Its radius is, then doubled. The potential of the bubble now will be				
		a) 16V	b)8V	c) 4V	d)2V	
	9.	A 10 $\mu$ F capacitor is charges to 500 V and its plates are joined together through a resistance of 10 $\Omega$ . The heat produced in the resistance is				
		a) 500 J	b) 125 J	c) 250 J	d) 1.25 J	
	10.	Work done in carrying a charge $Q'$ once round the circle of radius $r$ with a charge $Q$ at the centre is				
		a) $\frac{1}{4\pi\epsilon_0}\frac{Q}{r}$	b) $\frac{1}{4\pi\varepsilon_0}\frac{\mathcal{Q}\mathcal{Q}'}{r}$	c) Zero	d) $\frac{QQ'}{2r}$	
	11.	An automobile spring extends 0.2 m for 5000 N load. The ratio of potential energy stored in this spring when it has been compressed by 0.2 m to the potential energy stored in a $10\mu$ F capacitor at a potential difference of $10000$ V will be				
		a) 1/4	b) 1	c) 1/2	d)2	
	12.	A parallel plate capacitor of capacitance 100 pF is to be constructed by using paper sheets of 1 mm thickness as dielectric. If the dielectric constant of paper is 4, the number of circular metal foils of diameter 2 cm each required for the purpose is				
		a) 40	b) 2 <mark>0</mark>	c) 30	d)10	
	13.	Two capacitor of capacity $6\mu$ F and $12\mu$ F in series are connected by potential of 150 V. the potential of capacitor of capacity $12\mu$ F will be				
		a) 25 V	b) 50 V	c) 100 V	d) 150 V	
	14.	A parallel plate capacitor or capacity $C_0$ is charged to a potential $V_0$ .				
		I. The energy stored in the capacitor when the battery is disconnected and the plate separation is doubled is $E_1$ .				
		II. The energy stored in the capacitor when the charging battery is kept connected and the $E_1$				
	separation between the capacitor plates is doubled is $E_2$ . Then $\frac{E_1}{E_2}$ value is					
		a) $\frac{4}{1}$	b) $\frac{3}{2}$	c) 2	d) $\frac{1}{2}$	
15. The potential at a point <i>P</i> which is forming a corner of a square of side 93mm w = 33 nC, $Q_2 = -51$ nC, $Q_3 = 47$ nC located at the other three corners is nearly					_	
		a) 16kV	b)4kV	c) 400V	d)160V	
	16.	<ul> <li>b. If the plates of a parallel plate capacitor are not equal in area, then quantity of charge</li> <li>a) On the plates will be same but nature of charge will differ</li> <li>b) On the plates as well as nature of charge will be different</li> <li>c) On the plates will be different but nature of charge will be same</li> </ul>				

d) As well as nature of charge will be same

- 17. Two capacitors of capacitance 2  $\mu$ F and 4 $\mu$ F respectively are connected in series. The combination is connected across a potential difference of 10 V. The ratio of energies stored by capacitors will be
  - a)  $1:\sqrt{2}$  b) 2:1 c) 1:4 d) 4:1
- 18. A  $20\mu$ F capacitor is connected to 45 V battery through a circuit whose resistance is  $2000\Omega$ . What is the final charge on the capacitor?
- a)  $9 \times 10^{-4}$ C b)  $9.154 \times 10^{-4}$ C c)  $9.8 \times 10^{-4}$ C d) None of these 19. The equivalent capacitance between points *A* and *B* for the combination of capacitors shown in
- figure, where all capacitances are in microfarad is

