

Class: XIIth Subject: PHYSICS
Date: DPP No.: 6

Topic:-.semiconductor electronics: materials, devies and simple circuits

1. ′	The conduction	n band in a s	olid is partially	filled at 0 K. Th	e solid sample is a
------	----------------	---------------	-------------------	-------------------	---------------------


- a) Conductor
- b) Semiconductor
- c) Insulator
- d) None of these
- 2. For a given triode $\mu=20$. The load resistance is 1.5 times the anode resistance. The maximum gain will be
 - a) 16

b) 12

c) 10

d) None of the above

3. The output of given logic circuit is

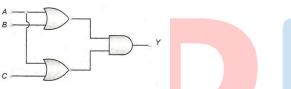

- a) A + B + C
- $b)(A+B)\cdot (A+C)$
- c) A · (B · C)
- $d)A \cdot (B + C)$
- 4. A transistor is operated in common-emitter configuration at $V_c = 2V$ such that a change in the base current from 100 μA produces a change in the collector current from 5 mA to 10 mA. The current gain is
 - a) 75

- b) 100
- c) 150

d)50

- 5. p n junction is said to be forward biased, when
 - a) The positive pole of the battery is joined to the p-semiconductor and negative pole to the n-semiconductor
 - The positive pole of the battery is joined to the n-semiconductor and negative pole to the n-semiconductor and p-semiconductor
 - c) The positive pole of the battery is connected to n-semiconductor and p-semiconductor
 - d) A mechanical force is applied in the forward direction
- 6. A p-type material is electrically
 - a) Positive
 - b) Negative
 - c) Neutral
 - d) Depends on the concentration of p impurities
- 7. The slope of plate characteristic of a vacuum tube diode for certain operating point on the curve is $10^{-3} \frac{mA}{V}$. The plate resistance of the diode and its nature respectively
 - a) 100 kilo-ohms static

b) 1000 kilo-ohms static

c) 1000 kilo-ohms dynamic


d) 100 kilo-ohms dynamic

- 8. Bonding in a germanium crystal (semi-conductor) is
 - a) Metallic
- b) Ionic
- c) Vander Waal's type d) Covalent
- 9. In a semiconducting material the mobilities of electrons and holes are μ_e and μ_h respectively. Which of the following is true
 - a) $\mu_e > \mu_h$
- b) $\mu_e < \mu_l$
- c) $\mu_e = \mu_h$
- d) μ_e < 0; μ_h > 0
- 10. The voltage gain of triode amplifier is 30 and input voltage is $V_i = \sin 100\pi t$, then output voltage will be
 - a) $30 \sin 100 \pi t$
- b) $\sin 100 \pi t$
- c) $-30 \sin 100 \pi t$
- d) $\sin 100 \pi t$
- 11. In a common-base mode of a transistor, the collector current is 5.488 mA for an emitter current of 5.60 mA. The value of the base current amplification factor (β) will be
 - a) 49

b)50

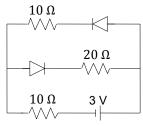c) 51

- d)48
- 12. In the network show, the current flowing through the battery of negligible internal resistance is




- a) 0.10 A
- b) 0.15 A
- c) 0.20 A
- d) 0.30 A
- 13. In a transistor if collector current is 25 mA and base current is 1 mA, then current amplification factor α is
 - a) $\frac{25}{24}$

b) $\frac{24}{25}$

c) $\frac{25}{26}$

- d) $\frac{26}{25}$
- 14. In a triode amplifier, the value of maximum gain is equal to
 - a) Half the amplification factor
- b) Amplification factor
- c) Twice the amplification factor
- d) Infinity
- 15. Which one of the following is the weakest kind of bonding in solids
 - a) Ionic
- b) Metallic
- c) Vander Waals
- d) Covalent

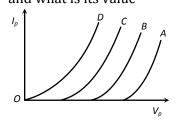- 16. The logic behind 'NOR' gate is that it gives
 - a) High output when both the inputs are low
 - b) Low output when both the inputs are low
 - c) High output when both the inputs are high
 - d) None of these
- 17. In the figure four plate characteristics of a triode at different grid voltages are shown. The difference between successive grid voltage is 1 *V*. Which curve will have maximum grid voltage and what is its value



- a) A, $V_q = +4 V$
- b) B, $V_q = +4 V$
- c) A, $V_a = 0$
- d) D, $V_q = 0$

- 18. The expected energy of the electrons at absolute zero is called
 - a) Fermi energy
- b) Emission energy
- c) Work function
- d) Potential energy

- 19. In a transistor the base is
 - a) An insulator

- b) A conductor of low resistance
- c) A conductor of high resistance
- d) An extrinsic semiconductor
- 20. If control grid is made negative, then the plate current will
 - a) Increase

b) Remain constant

c) Decrease

d) Cannot say from given data

