

## Topic :- SEMICONDUCTOR ELECTRONICS: MATERIALS, DEVICES AND SIMPLE CIRCUITS

1 (c)

The resistance of semiconductor decreases with the increase in temperature

2 (d)

$$\lambda = \frac{hc}{E} = \frac{6.62 \times 10^{-34} \times 3 \times 10^8}{(1.14 \times 1.6 \times 10^{-19})} = 10,888 \text{ \AA}$$

3 (c)

$$\begin{aligned} \text{Voltage gain} &= \frac{\text{Output voltage}}{\text{Input voltage}} \\ \Rightarrow V_{out} &= V_{in} \times \text{Voltage gain} \\ \Rightarrow V_{out} &= V_{in} \times \text{Current gain} \times \text{Resistance gain} \\ &= V_{in} \times \beta \times \frac{R_L}{R_{BE}} = 10^{-3} \times 100 \times \frac{10}{1} = 1V \end{aligned}$$

4 (d)

$$r_p = \frac{\Delta V_p}{\Delta i_p} = \frac{150 - 100}{(12 - 7.5) \times 10^{-3}} = \frac{50}{4.5} \times 10^3 = 11.1 k\Omega$$

5 (c)

$$\alpha = \frac{I_c}{I_e} < 1 \text{ or } I_c < I_e.$$

6 (b)

The input of OR gate is  $Y = A + B$

7 (d)

In a forward biased  $p$ - $n$  junction, the applied potential is opposite to the junction barrier potential  $V_B$ . The consequence of this is the effective barrier potential reduces. Hence, the graph (d) is correctly shown.

8 (d)

Number density of atoms in silicon specimen =  $5 \times 10^{28}$  atoms/ $\text{m}^2$  =  $5 \times 10^7$  silicon atoms, so total number of indium atoms doped per atoms, so total number of indium atoms doped per  $\text{cm}^3$  of silicon will be  
 $n = 5 \times 10^{22} / 5 \times 10^7 = 10^{15}$  atoms  $\text{cm}^{-3}$ .

9 (c)

For 'NAND' gate (option c), output =  $\overline{0.1} = \overline{0} = 1$

10 (c)

The junction diode  $I$  will provide output when forward biased. It will be so during negative half cycle of input AC voltage applied.


11 (c)

If inputs are  $A$  and  $B$  then output for NAND gate is  $Y = \overline{AB}$

$\Rightarrow$  If  $A = B = 1, Y = \overline{1.1} = \overline{1} = 0$

12 (d)

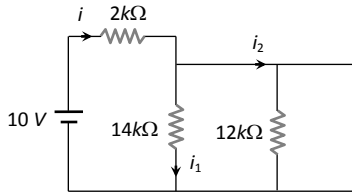Equivalent circuit can be redrawn as follows



$$i = \frac{10}{2} = 5 \text{ mA} = i_2$$

$$i_1 = 0$$

13 (c)

Because As is pentavalent impurity

14 (c)

$$V_{dc} = V_{ac} = \frac{2V_0}{\pi} = \frac{2 \times 6.28}{3.14} = 4V$$

15 (c)

$$E_g = h\nu = \frac{hc}{\lambda} = \left( \frac{6.63 \times 10^{-34} \times 3 \times 10^8}{2480 \times 10^{-9} \times 1.6 \times 10^{-19}} \right) = 0.5 \text{ eV}$$


16 (b)

$V_k =$  knee voltage = 0.3 V

$$\therefore \text{Resistance} = \frac{\Delta V}{\Delta i} = \frac{(2.3 - 0.3)}{(10 - 0) \times 10^{-3}} = 200\Omega = 0.2k\Omega$$

17 (b)

In reverse biasing, the applied voltage  $V$  on the  $n$ -side is positive and is negative on the  $p$ -side. The applied bias  $V$  and the barrier potential  $V_B$  are in the same direction making the effective junction potential  $V + V_B$ . As a result, the junction width will increase. The higher junction potential would restrict the flow of majority carriers to a much greater extent. However, such a field will favour the flow of minority carriers. So, reverse bias current will be due to the minority carriers only.

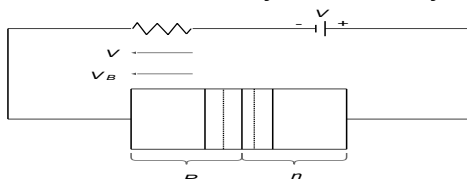

18 (c)

The current through the battery is

$$I = \frac{10V}{5\Omega + 5\Omega} = \frac{10V}{10\Omega} = 1A$$

20

**(b)**

In common emitter amplifier

Voltage gain = current gain  $\times$  resistance gain

$$\text{Or } A_V = \beta \times \frac{R_o}{R_i}$$

$$\text{Or } \frac{V_o}{V_i} = \beta \frac{R_o}{R_i}$$

$$\text{Or } \frac{3}{0.01} = 100 \times \frac{R_o}{1 \times 10^3}$$

$$\text{Or } R_o = \frac{3}{0.01} = 3 \text{ k}\Omega$$

PE

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	C	D	C	D	C	B	D	D	C	C
Q.	11	12	13	14	15	16	17	18	19	20
A.	C	D	C	C	C	B	B	C	C	B

PE