

## SUBJECT :- PHYSICS

CLASS :- 12<sup>th</sup>


CHAPTER :- CAPACITANCE

PAPER CODE :- CWT-2

ANSWER KEY											
1.	(C)	2.	(D)	3.	(C)	4.	(D)	5.	(B)	6.	(B)
8.	(A)	9.	(A)	10.	(B)	11.	(B)	12.	(D)	13.	(B)
15.	(C)	16.	(B)	17.	(C)	18.	(C)	19.	(A)	20.	(D)
22.	100	23.	12	24.	4	25.	2	26.	200	27.	6
29.	48	30.	32							28.	420

## SOLUTIONS

1. (C)

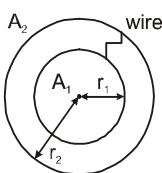



Sol.

All given charge of  $A_1$  goes to  $A_2$   
Therefore  $C = 4\pi\epsilon_0 r_2$

2. (D)

Sol.  $V_A = V_B$  So  $V=0$ ,  $Q=CV \Rightarrow C = \frac{Q}{V} = \infty$ 

3. (C)

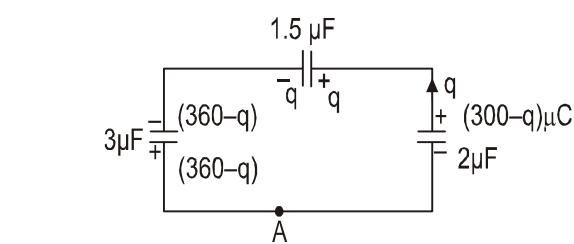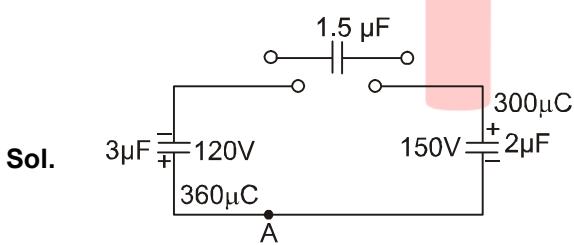

$$V_A + \frac{(300-q)}{2} - \frac{q}{1.5} + \frac{360-q}{3} = V_A \quad \dots \dots \dots (i)$$

by solve this equation we get

$$\Rightarrow q = 180 \mu\text{C}$$

Charge on  $1.5\mu\text{F}$  capacitor is  $= 150\mu\text{C}$ Charge on  $2\mu\text{F}$  capacitor is

$$= 300 - 180 = 120\mu\text{C}$$

Therefore charge flows through A from left to right.

4. (D)

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{30} + \frac{1}{15} = \frac{3+2+4}{60}$$

$$C_{eq} = \frac{60}{9} = \frac{20}{3} \mu\text{F}$$

Total charge in this series combination is

$$= \frac{20}{3} \times 90 \quad q = 600\mu\text{C}$$

Potential difference between the plate of  $C_1$  is  $= \frac{q}{C_1} = \frac{600}{20} = 30\text{V}$ Potential difference between the plate of  $C_2$ 


$$is \frac{q}{C_2} = \frac{600}{30} = 20\text{V}$$

Potential difference between the plate of  $C_3$ 

$$is \frac{q}{C_3} = \frac{600}{15} = 40\text{V}$$

5. (B)

Sol. The two plates acts as a dipole

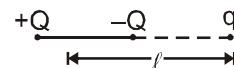



$\therefore$  Force on charge  $q$  ;  
 $F = Eq$

$$= \left( \frac{2kQd}{\ell^3} \right) \cdot q = \frac{Qqd}{2\pi\epsilon_0\ell^3}$$

Because area of the plate is increased.


6. (B)

Sol. Equivalent circuit is

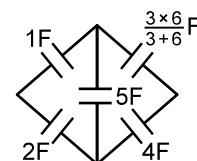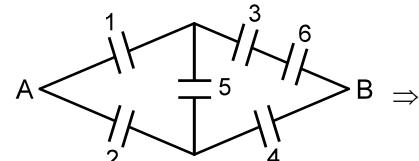

$$= 2F$$

7. (C)

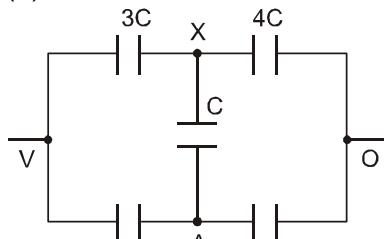

Sol.

$$(x - V) 3 + (x - 0) 4 + (x - (V - x)) 1 = 0$$

$$3x - 3V + 4x + 2x - V = 0$$

$$9x = 4V \quad x = \frac{4V}{9}$$

$$V_A - V_B = (V - x) - x = V - 2x$$

$$\Rightarrow V - \frac{8V}{9} = \frac{V}{9} = 3 \text{ volt}$$

$$\Rightarrow V = 27 \text{ volt.}$$

8. (A)

Sol. (A)  $Q_1' = Q_1 + Q_2 = 150\mu\text{C}$

$$\frac{Q_1'}{Q_2} = \frac{C_1}{C_2} = \frac{1}{2} \Rightarrow Q_1' = 50\mu\text{C}$$

$$Q_2' = 100\mu\text{C}$$

25 $\mu\text{C}$  charge will flow from smaller to bigger sphere .

9. (A)

10. (B)

Sol.  $W = \frac{CV^2}{2}$        $V^2 = \frac{2U}{C} = \frac{2 \times 0.16}{2 \times 10^{-6}}$   
 $V = 400 \text{ Volt}$

11. (B)

Sol.  $W = V_f - V_i = \frac{1}{2}CV_f^2 - \frac{1}{2}CV_i^2$   
 $= \frac{1}{2}C(40^2 - 20^2) \quad W = 600 \text{ C}$   
 $W_1 = \frac{1}{2}C(50^2 - 40^2) = \frac{900}{2} \text{ C}$   
 $W_1 = \frac{900}{2} \cdot \frac{W}{600} = \frac{3}{4} W \quad \text{Ans}$

12. (D)


Sol.  $V = \frac{V_1C_1 + V_2C_2}{C_1 + C_2}$   
 $400 = \frac{100 \times 10 + 0}{C_1 + C_2}$   
 $C_1 + C_2 = 25 \mu\text{F}$   
 $C_2 = 25 - 10$   
 $= 15 \mu\text{F}$

13. (B)

Sol.  $V = \frac{C_1V_1 + C_2V_2}{C_1 + C_2} = \frac{(900 + 2500)\mu\text{Fvolt}}{(3 + 5)\mu\text{F}}$   
 $= \frac{3400 \text{ Volt}}{8}$   
 $= 455 \text{ Volt}$

14. (D)

Sol. Equilient figure

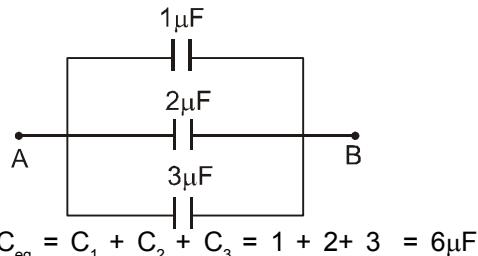

$$C_{eq} = C_1 + C_2 + C_3 = 1 + 2 + 3 = 6\mu\text{F}$$

15. (C)

Sol.  $t_1 > t_2$   
 $R_1C_1 > R_2C_2$  for same  $q_{max}$   
 $q_{01} = q_{01} = E_1C_1 = E_2C_2$   
If  $R_1 > R_2$ ,  $C_1 = C_2$  &  $E_1 = E_2$ .

16. (B)

Sol.  $C' = \frac{\epsilon_0 A}{d/2} = \frac{2\epsilon_0 A}{d} = 2C$

17. (C)

Sol. Now, charge remains same on the plates.

$$U_0 = \frac{Q^2}{2C} \text{ (given)}$$

$$\text{Now energy} = U' = \frac{Q^2}{2C'} = \frac{Q^2}{2CK} = \frac{U_0}{K}$$

18. (C)

19. (A)

Sol.  $V_{C_2} = V_{C_2} = V$   
 $C_1 = C$   
 $C_2 = KC$   
 $q_1 = C_1V_{C_1} = CV$   
 $q_2 = C_2V_{C_2} = KCV$   
 $q_1 < q_2$ .

20. (D)

Sol. If potential difference across an isolated charged capacitor is doubled by doubling separation between plates, the energy stored is capacitor from  $U = \frac{Q^2}{2C}$  becomes double of previous value.  
Hence statement 1 is false.

**21.**  $0.2\mu\text{C}$

**Sol.**  $C' = C + C + C = 3C$  (When connect in parallel)  
 $\therefore q = CV = 3CV$

$$\Rightarrow CV = \frac{1.8}{3} = 0.6\mu\text{C}$$

After discharging

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} = \frac{3}{C}$$

$$q = \frac{CV}{3} = q = \frac{0.6}{3} = 0.2\mu\text{C}$$


**22.** 100

$$\text{Sol. } q = CV = 500 \times 10^{-6} \times 20 = 10^{-2}$$

$$t = \frac{q}{dq/dt} = \frac{10^{-2}}{100 \times 10^{-6}} = 10^2 = 100 \text{ second}$$

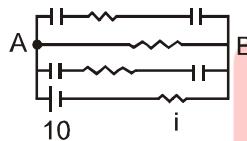**23.**  $12\mu\text{C}$

**Sol.** Charge on each capacitor will be same. In steady state current through capacitor will be zero




$$\text{current in steady state} = i = \frac{10}{5} = 2 \text{ amp}$$




$$\text{potential across AB} = iR = 2 \times 4 = 8 \text{ V.}$$

Potential across each capacitor = 4 V  
on each plate  $Q = CV = 3 \times 4 = 12\mu\text{C}$

**24.**  $4\mu\text{F}$

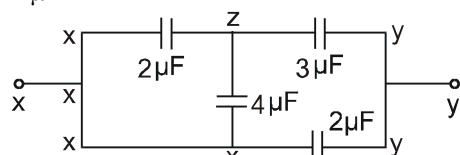

Rearrange the circuit

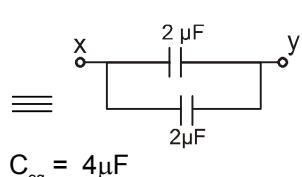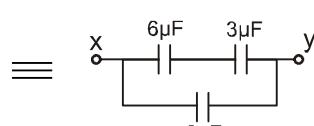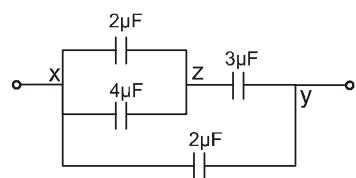

$$C_{\text{eq}} = 4\mu\text{F}$$

**25.**  $2\mu\text{C}$

**Sol.** In steady state no current flows through capacitor. The potential difference across capacitor and resistor of resistance  $R_2$  is same.

$$\therefore \text{charge on capacitor} = CV = C \times \frac{R_2}{R_1 + R_2} \times 3$$

$$= 1\mu\text{F} \times \frac{1}{5+1} \times 3 = 2\mu\text{C.}$$

**26.**  $200\mu\text{J}$

**Method I**

Force between plates

$$F = \frac{Q^2}{2A\epsilon_0} = \frac{\left(\frac{\epsilon_0 A}{x} V\right)^2}{2A\epsilon_0} = \frac{\epsilon_0 A V^2}{2x^2}$$

where  $x$  is separation between plates

$$dW = F dx$$

$$W = \int_d^{2d} \frac{\epsilon_0 A V^2}{2x^2} dx = \frac{\epsilon_0 A V^2}{4x} \Big|_d^{2d} = \frac{CV^2}{4} = 200 \mu\text{J}$$

**Method II**

$$U_f + W_B + W_{\text{ext}} = U_i + \text{loss}$$

Process is slow so energy loss is zero work done by battery =  $W_B = QE$

$$Q = Q_f - Q_i = 20 - 40 = -20$$

$$W_B = -20 \times 20$$

$$\frac{1}{2} 2 \times 20^2 - 20 \times 20 + W_{\text{ext}} = \frac{1}{2} 1 \times 20^2 + 0 \\ W_{\text{ext}} = 200 \mu\text{J}$$


**27.** 6

**Sol.** Electric field inside dielectric  $\frac{\sigma}{K\epsilon_0} = 3 \times 10^4$

$$\Rightarrow \sigma = 2.2 \times 8.85 \times 10^{-12} \times 3 \times 10^4$$

$$= 6 \times 10^{-7} \text{ C/m}^2$$

**28.** 420 N

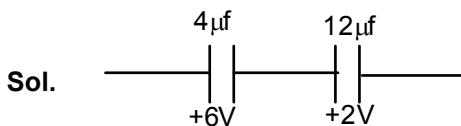

$$Q_1 = 24\mu\text{C}, \quad Q_2 = 18\mu\text{C}$$

$$Q = 42\mu\text{C}$$

$$E = 10^7 \times 42 \times 10^{-6}$$

**29.** 48

$$\text{Sol. } q_3 = \frac{C_3}{C_2 + C_3} \cdot Q \quad q_3 = \frac{3}{3+2} \times 80 = \frac{3}{5} \times 80 = 48\mu\text{C}$$

**30.** 32

$$\text{Sol. } W = \frac{1}{2} CV^2 = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \times \frac{(8 \times 10^{-18})^2}{100 \times 10^{-6}} \\ = \frac{1}{2} \times \frac{64 \times 10^{-36}}{100 \times 10^{-6}} = 32 \times 10^{-32} \text{ J}$$