

JEE MAIN : CHAPTER WISE TEST PAPER-3

SUBJECT :- PHYSICS

CLASS :- 12th

CHAPTER :- CURRENT ELECTRICITY


DATE.....

NAME.....

SECTION.....


(SECTION-A)

- In the presence of an applied electric field (\vec{E}) in a metallic conductor.
 - (A) The electrons move in the direction of \vec{E}
 - (B) The electrons move in a direction opposite to \vec{E}
 - (C) The electrons may move in any direction randomly, but slowly drift in the direction of \vec{E} .
 - (D) The electrons move randomly but slowly drift in a direction opposite to \vec{E} .
- A heater coil is cut into two equal parts and only one part is now used in the heater. The heat generated will now be :
 - (A) doubled
 - (B) four times
 - (C) one-fourth
 - (D) half
- There are two wires of the same length and of the same material and radii r and $2r$. The ratio of their specific resistance is
 - (A) 1 : 2
 - (B) 1 : 1
 - (C) 1 : 4
 - (D) 4 : 1
- If the length and cross-section of a wire is doubled, then the resistance will
 - (A) become half
 - (B) increase two times
 - (C) remain unchanged
 - (D) increase four times
- When the resistance of copper wire is 0.1Ω and the radius is 1 mm, then the length of the wire is (specific resistance of copper is $3.14 \times 10^{-8} \text{ ohm x m}$)
 - (A) 10 cm
 - (B) 10 m
 - (C) 100 m
 - (D) 100 cm

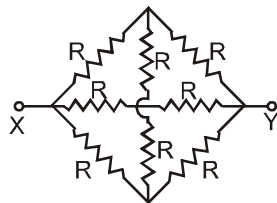


6. Find the equivalent resistance between the X and Y
- (A) $2R/3$
 - (B) $R/3$
 - (C) $2R$
 - (D) $3R$

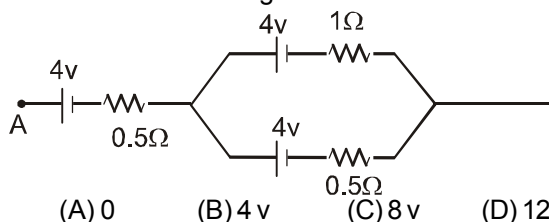7. Find the equivalent emf of the three batteries as shown in the figure.



- The unit of potential gradient is
 - (A) volt
 - (B) volt/ampere
 - (C) volt/meter
 - (D) volt x meter
- The potentiometer wire 10 m long and 20 ohm resistance is connected to a 3 volt emf battery and a 10 ohm resistance. The value of potential gradient in volt/m of the wire will be
 - (A) 1.0
 - (B) 0.2
 - (C) 0.1
 - (D) 0.02
- Two coils connected in series have resistances 600Ω and 300Ω at 20°C and temperature coefficient of resistivity 0.001 k^{-1} and 0.004 k^{-1} respectively. The resistance of the combination at temperature 50°C is
 - (A) 426Ω
 - (B) 954Ω
 - (C) 1806Ω
 - (D) 214Ω
- Read the following statements carefully :
 Y : The resistivity of semiconductor decreases with increase of temperature.
 Z : In a conducting solid, the rate of collisions between free electrons and ions increases with increase of temperature.
 Select the correct statement (s) from the following :
 - (A) Y is true but Z is false
 - (B) Y is false but Z is true
 - (C) Both Y and Z are true
 - (D) Y is true and Z is the correct reason for Y

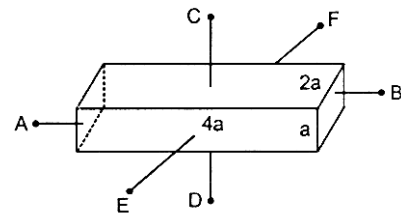
12. A conductor with rectangular cross section has dimension $(a \times 2a \times 4a)$ as shown in fig. Resistance across AB is x , across CD is y and across EF is z . Then




- (A) $x = y = z$
- (B) $x > y > z$
- (C) $y > z > x$
- (D) $x > z > y$

13. Two wires of same dimension but resistivities ρ_1 and ρ_2 are connected in series. The equivalent resistivity of the combination is
- (A) $\rho_1 + \rho_2$
 - (B) $1/2 (\rho_1 + \rho_2)$
 - (C) $\sqrt{\rho_1 \rho_2}$
 - (D) $2(\rho_1 + \rho_2)$

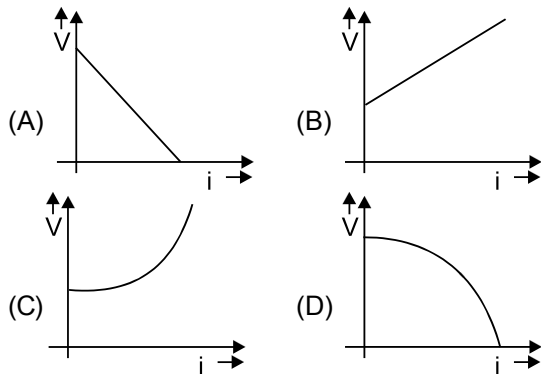
14. If internal resistance of a cell is proportional to current drawn from the cell. Then the best representation of terminal potential difference of a cell with current drawn from cell will be:



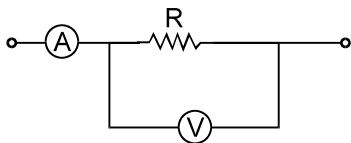15. In the circuit shown the readings of ammeter and voltmeter are 4A and 20V respectively. The meters are non-ideal, then R is



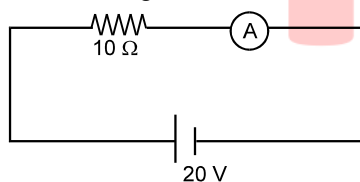- (A) $5\ \Omega$
 (B) less than $5\ \Omega$
 (C) greater than $5\ \Omega$
 (D) between $4\ \Omega$ and $5\ \Omega$.
16. The ammeter shown in figure consists of a $480\ \Omega$ coil connected in parallel to a $20\ \Omega$ shunt. Find the reading of the ammeter.



- (A) $\frac{50}{73}\text{ A}$ (B) $\frac{40}{53}\text{ A}$ (C) $\frac{50}{93}\text{ A}$ (D) $\frac{73}{50}\text{ A}$


17. **STATEMENT-1** : The current density \vec{j} at any point in ohmic resistor is in direction of electric field \vec{E} at that point.

STATEMENT-2 : A point charge when released from rest in a region having only electrostatic field always moves along electric lines of force.

- (A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1
 (B) Statement-1 is True, Statement-2 is True; Statement-2 is **NOT** a correct explanation for Statement-1
 (C) Statement-1 is True, Statement-2 is False
 (D) Statement-1 is False, Statement-2 is True.

18. Time taken by a 836 W heater to heat one litre of water from 10°C to 40°C is :
 (A) 50 s (B) 100 s (C) 150 s (D) 200 s

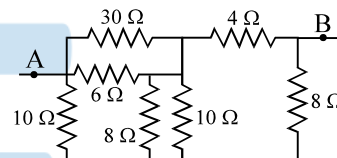19. Seven resistors are connected as shown in the diagram.




The equivalent resistance in ohms of this network between A and B is


- (A) 6 (B) 8 (C) 12 (D) 20
20. Resistance P, Q, S and R are arranged in a cyclic order to form a balanced Wheatstone's network. The ratio of power consumed in the branches (P + Q) and (R + S) is
 (A) 1 : 1 (B) R : P
 (C) $P^2 : Q^2$ (D) $P^2 : R^2$

(SECTION-B)

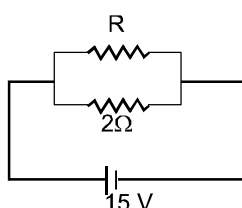21. A wire when connected to 220 V mains supply has power dissipation P_1 . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is P_2 . Then $P_2 : P_1$ is x : y. so find the value of $x+y = ?$
22. If in the circuit, power dissipation is 150 W then R is Ω .




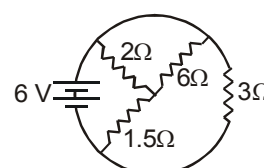23. A wire has a resistance of 12 ohms. If it is bent in the form of a circle. The effective resistance between (in Ω) the two points on any diameter is equal to
24. The total current (Amp.) supplied to the circuit by the battery is :



25. An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If the lengths and radii of the wires are in the ratio of $4/3$ and $2/3$, then the ratio of the currents passing through the wire will be $P : Q$. find the value of Q
26. In a potentiometer experiment the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of 2Ω , the balancing length becomes 120 cm. The internal resistance Ω of the cell is :
27. The resistance of bulb filament is $100\ \Omega$ at a temperature of 100°C . If its temperature coefficient of resistance be 0.005 per $^\circ\text{C}$, its resistance will become $200\ \Omega$ at a temperature of $^\circ\text{C}$.
28. An electric bulb is rated 220 volt - 100 watt. The power (in watt) consumed by it when operated on 110 volt will be

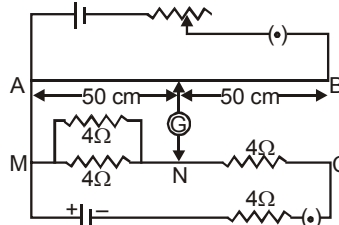29. The current in the primary circuit of a potentiometer is $0.2\ \text{A}$. The specific resistance and cross-section of the potentiometer wire are 4×10^{-7} ohm metre and $8 \times 10^{-7}\ \text{m}^2$ respectively. The potential gradient (in V/m) will be equal to :
30. In the following figure, the p.d. between the points M and N is balanced at 50 cm length. The balancing length in cm, for the p.d. between points N and C will be



PE