

JEE MAIN ANSWER KEY & SOLUTIONS

SUBJECT :- PHYSICS

CLASS :- 12th

PAPER CODE :- CWT-3

CHAPTER :- CURRENT ELECTRICITY

ANSWER KEY

1. (D)	2. (A)	3. (B)	4. (C)	5. (B)	6. (A)	7. (C)
8. (C)	9. (B)	10. (B)	11. (C)	12. (D)	13. (B)	14. (D)
15. (C)	16. (A)	17. (C)	18. (C)	19. (A)	20. (B)	21. 5
22. 6	23. 3	24. 4	25. 3	26. 2	27. 400	28. 25
29. 0.1	30. 100					

SOLUTIONS


1. (D)
Sol. In the presence of an applied electric field (\vec{E}) in a metallic conductor. The electrons also move randomly but slowly drift in a direction opposite to \vec{E} .

2. (A)
Sol. $H_1 = \frac{V^2}{R} t$
 $H_2 = \frac{V^2}{R/2} t$
 $\therefore \frac{H_2}{H_1} = 2 \Rightarrow H_2 = 2H_1$

3. (B)
Sol. Specific resistance depends only on the material of the wire.

4. (C)
Sol. $R = \frac{\rho l}{A} = \frac{\rho \times 2l}{2A} = \frac{\rho l}{A}$ (unchanged)

5. (B)
Sol. $R = \frac{\rho l}{A} \Rightarrow 0.1 = \frac{3.14 \times 10^{-8} \times l}{\pi(1 \times 10^{-3})^2} \Rightarrow l = 10 \text{ m}$

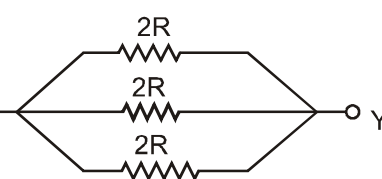6. (A)
Sol. 
 $R_{eq} = \frac{2R}{3}$

7. (C)
Sol. $\epsilon_{eq} = 4 + \frac{\frac{4}{1} + \frac{4}{0.5}}{\frac{1}{1} + \frac{1}{0.5}}$
 $= 4 + \frac{12}{3} = 8 \text{ v.}$

8. (C)
Sol. Potential gradient = $\frac{V}{l}$

9. (B)
Sol. $r_{eq} = 10 + 20 = 30$, $I = \frac{3}{30} = \frac{1}{10}$, $V = \epsilon - IR = 3 - \frac{1}{10} \times 10 = 2$
 Potential gradient = $\frac{V}{l} = \frac{2}{10} = 0.2$

10. (B)
Sol. $R_1 = R_{01} (1 + \alpha_1 \Delta\theta) = 600 (1 + 0.001 \times 30) = 618 \Omega$
 $R_2 = R_{02} (1 + \alpha_2 \Delta\theta) = 300 (1 + 0.004 \times 30) = 336 \Omega$
 $R_{eq} = R_1 + R_2 = 618 + 336 = 954 \Omega$


11. (C)
Sol. In semiconductor resistance decrease with increase in the temperature. Therefore resistivity also decrease. In conducting solid resistance increase with increase the temperature because the rate of collisions between free electron and ions increases with increase of temperature both the statements are true.

12. (D)
Sol. $X = \frac{\rho \times 4a}{a \times 2a} = 2 \frac{\rho}{a}$
 $Y = \frac{\rho \times a}{4a \times 2a} = \frac{1}{8} \frac{\rho}{a}$
 $Z = \frac{\rho \times 2a}{4a \times a} = \frac{1}{2} \frac{\rho}{a}$
 so, $X > Z > Y$


13. (B)
Sol. $\rho_{eq} \frac{2l}{A} = \rho_1 \frac{l}{A} + \rho_2 \frac{l}{A}$
 $\rho_{eq} = 1/2 (\rho_1 + \rho_2)$

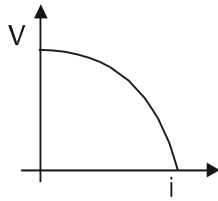14. (D)

Sol. Given $r \propto i \Rightarrow r = ki$
 $V = E - ir = E - i(ki) \Rightarrow V = -i^2 k + E$



15. (C)

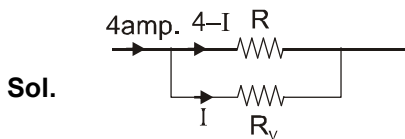

Sol.

$(4 - I)R = IR_v = 20 \quad (4 - I)R = 20$
 $4 - I$ is less than 4
 So that, R is greater than 5Ω

16. (A)

Sol. $R_{eq} = 10 + \frac{480 \times 20}{480 + 20} = 10 + \frac{96}{5} = \frac{146}{5}$

current passes through the battery.

$I = \frac{20 \times 5}{146} = \frac{100}{146} = \frac{50}{73}$ amp.

17. (C)

Sol. From relation $\vec{j} = \sigma \vec{E}$, the current density \vec{j} at any point in ohmic resistor is in direction of electric field \vec{E} at that point. In space having non-uniform electric field, charges released from rest may not move along ELOF. Hence statement 1 is true while statement 2 is false.

18. (C)

Sol. Let time taken in boiling the water by the heater is t sec. Then

$$Q = ms\Delta T \Rightarrow \frac{Pt}{J} = ms\Delta T$$

$$\frac{836}{4.2} t = 1 \times 1000 (40^\circ - 10^\circ)$$


$$\frac{836}{4.2} t = 1000 \times 30$$

$$t = \frac{1000 \times 30 \times 4.2}{836}$$

= 150 second **Ans.**

19. (A)

Sol. The given circuit is equivalent to

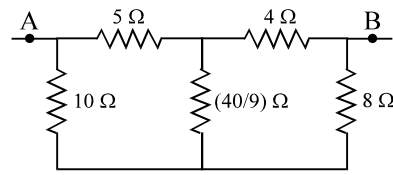

As $10 \times 4 = 5 \times 8$ this is balanced Wheatstone network

$$\text{Therefore } R = \frac{(5+4) \times (10+8)}{9+18} = 6 \text{ ohm}$$

20. (B)

Sol. For balanced bridge, $P/Q = R/S$
 power dissipation in resistance R with voltage V is V^2/R .

$$\therefore \frac{P_{P+Q}}{P_{R+S}} = \frac{R+S}{P+Q} = \frac{R}{P}$$

21. 5

Sol. Using the formula $P = \frac{V^2}{R}$... (i)

Where R is resistance of wire, V is voltage across wire and P is power dissipation in wire

$$\text{and } R = \frac{\rho \ell}{A} \quad \dots \text{(ii)}$$

From Eqs. (i) and (ii)

$$P_1 = \frac{V^2}{\rho \ell / A} = \frac{V^2}{\rho \ell} \cdot A$$

$$P_1 = \frac{V^2}{\rho \ell} \cdot A \quad \dots \text{(iii)}$$

In 2nd case

Let R_2 is net resistance.

$$R_2 = \frac{R \times R}{R + R} = \frac{R}{2}$$

Where, R is the resistance of half wire.

$$\therefore R_2 = \frac{\rho \cdot \left(\frac{\ell}{2}\right)}{A \cdot 2} = \frac{\rho \ell}{4A}$$

$$\therefore P_2 = \frac{V^2}{\rho \ell} \cdot 4A$$

... (iv)


Hence, from Eqs. (iii) and (iv)

$$\frac{P_1}{P_2} = \frac{1}{4} \Rightarrow \frac{P_2}{P_1} = \frac{4}{1} \Rightarrow x+y = 4+1 = 5$$

22. 6

Sol. $\frac{15^2}{R_{eq}} = 150$ (i)
 $R_{eq} = \frac{2R}{2+R}$ (ii)
 Solving (i) and (ii), $R = 6 \Omega$ **Ans.**

23. 3

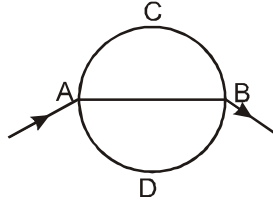

Sol.

$$\frac{1}{R_{eq}} = \frac{1}{R_{ACB}} + \frac{1}{R_{ADB}}$$

$$2\pi r = L$$

$$ACB = \pi r$$

$$\pi r = \frac{L}{2} = \frac{12}{2} = 6$$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{6}$$

$$R_{eq} = 3$$

24. 4

Sol. $\therefore 2\Omega$ and 6Ω are in parallel

$$\Rightarrow R_{eq} = \frac{3 \times (1.5 + 1.5)}{3 + (1.5 + 1.5)} = \frac{3}{2} \Omega$$

$$i = \frac{6}{R_{eq}} = 4A$$
 Ans.

25. 3

Sol. ρ : same

In parallel $\Rightarrow i_1 R_1 = i_2 R_2$

$$\Rightarrow \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{\rho l_2 / A_2}{\rho l_1 / A_1} = \frac{l_2}{l_1} \times \frac{r_1^2}{r_2^2}$$

$$\therefore \frac{l_1}{l_2} = \frac{4}{3} \text{ and } \frac{r_1}{r_2} = \frac{2}{3}$$

$$\Rightarrow \frac{i_1}{i_2} = \frac{1}{3} \quad \frac{P}{Q} = \frac{1}{3} = Q = 3$$
 Ans.

26. 2

Sol. The internal resistance of the cell .

$$r = \left(\frac{l_1 - l_2}{l_2} \right) R$$

$$= \frac{240 - 120}{120} \times 2 = 2\Omega$$
 Ans.

27. 400

Sol. Let resistance of bulb filament is R_0 at 0°C , then from expression

$$R = R_0 (1 + \alpha \Delta T)$$

$$\therefore 100 = R_0 (1 + 0.005 \times 100)$$

$$200 = R_0 (1 + 0.005 \times x)$$

where x is temperature in $^\circ\text{C}$ at which resistance become 200Ω .

Dividing the above two equation

$$\frac{200}{100} = \frac{1 + 0.005x}{1 + 0.005 \times 100} \Rightarrow x = 400^\circ\text{C}$$

28. 25

Sol. $P = V^2/R$, putting values we get $R = (22)^2$ ohm

When operated at 110 V , $P' = (110)^2/R = 25$ watt

29. 0.1

Sol. $x = \frac{V}{l} = \frac{IR}{l} = \frac{IR \left(\frac{\rho l}{A} \right)}{l} = \frac{I\rho}{A}$

$$x = \frac{0.2 \times 4 \times 10^{-7}}{8 \times 10^{-7}} = \frac{0.8}{8} = 0.1 \text{ V/m.}$$

30. 100

Sol. $V \propto l$
 $l \propto R$

$$\frac{l_1}{l_2} = \frac{R_1}{R_2} \Rightarrow \frac{50}{l} = \frac{4+4}{4}$$

$$l = 100 \text{ cm}$$