

## JEE MAIN ANSWER KEY &amp; SOLUTIONS

## SUBJECT :- PHYSICS

CLASS :- 12<sup>th</sup>

CHAPTER :- ALTERNATING CURRENT

PAPER CODE :- CWT-6

ANSWER KEY												
1.	(B)	2.	(D)	3.	(C)	4.	(B)	5.	(C)	6.	(A)	
8.	(D)	9.	(D)	10.	(A)	11.	(D)	12.	(A)	13.	(A)	
15.	(B)	16.	(B)	17.	(C)	18.	(A)	19.	(B)	20.	(B)	
22.	0.36	23.	400	24.	4	25.	0.1	26.	119	27.	3	
29.	3	30.	25								28.	125

## SOLUTIONS

1. (B)

Sol.  $E = 10 \cos \left( 2\pi \times 50 \times \frac{1}{600} \right) = 5\sqrt{3}$

2. (D)

Sol. D.C. Voltmeter measures Average value only

3. (C)

Sol.  $(2)^2 R = P_2 \dots \text{(i)}$

$I_{\text{rms}}^2 \times R = 3P_2 \dots \text{(ii)}$

4. (B)

Sol.  $I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$

P.d. across resistance =  $R I_{\text{rms}}$ .

5. (C)

Sol.  $\tan \phi = \tan 45^\circ = \frac{\omega L}{R}$

$X_L = \omega L = R$ .

6. (A)

Sol. At resonance ( $V_C = V_L$ )

$V = I_{\text{rms}} \times R$

$= \frac{V_{\text{rms}}}{Z} \times R \quad (\text{here } z = R)$

$V = V_{\text{rms}} = 100 \text{ volt}$

&amp;

$I_{\text{rms}} = \frac{100}{50} = 2 \text{ Amp.}$

7. (A)

Sol.  $I_{\text{rms}} = \frac{60}{120} = \frac{1}{2} \text{ Amp.} \quad V_L = I_{\text{rms}} \times (\omega L)$

$40 = \frac{1}{2} \times (40 \times 10^3) \times L, \quad L = 20 \text{ mH}$

At resonance  $V_C = I_{\text{rms}} \left( \frac{1}{\omega C} \right) = V_L$

$C = \frac{1}{2} \times \frac{1}{4 \times 10^3} \times \frac{1}{40}$

$C = \frac{25}{8} \mu\text{F.}$

8. (D)

Sol.  $\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{8}{1}$

$V_2 = 8 \times 120 = 960 \text{ volt}$

$I = \frac{960}{10^4} = 96 \text{ mA.}$

9. (D)

Sol.  $V_{\text{rms}}^2 = \frac{\int_0^T (e_1 \sin \omega t + e_2 \cos \omega t)^2 dt}{T}$

$= \sqrt{\frac{e_1^2 + e_2^2}{2}}$

where  $\omega = \frac{2\pi}{T}$ .

10. (A)

Sol.  $P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \cos \phi$   
Here  $\phi = 90^\circ$  so  $P_{\text{av}} = 0$

11. (D)

Sol.  $I_0 = \frac{V_0}{X_C} = \frac{200\sqrt{2}}{1/\omega C}; \quad I_{\text{RMS}} = \frac{I_0}{\sqrt{2}} = 200 \text{ mA}$

12. (A)

Sol. Power factor =  $\frac{R}{Z} = \frac{30}{50} = \frac{3}{5}$

here  $Z = \sqrt{R^2 + (x_L - y_C)^2}$

$= \sqrt{(30)^2 + (60 - 20)^2}$

$Z = 50$

$I = \frac{V}{Z} = \frac{100}{50} = 2 \text{ Amp.}$


13. (A)


Sol. Statement-1 is True, Statement-2 is True;  
Statement-2 is a correct explanation for Statement-1

- 14.** (C)  
**Sol.** Given:  $L = 10 \text{ H}$ ,  $f = 50 \text{ Hz}$ .  
 For maximum power  $X_C = X_L$   
 $\frac{1}{\omega C} = \frac{1}{\omega L}$ ,  $C = \frac{1}{\omega^2 L}$   
 $C = \frac{1}{4\pi^2 \times 50 \times 50 \times 10}$   
 $\therefore C = 0.1 \times 10^{-5} \text{ F} = 1 \mu\text{F}$

- 15.** (B)  
**Sol.**  $i_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$

when  $\omega$  increases,  $i_{\text{rms}}$  increases so the bulb glows brighter

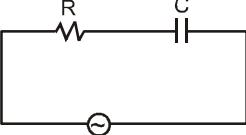- 16.** (B)  
**Sol.** Case I   $Z$   
 $= \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$

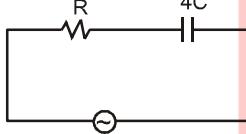Case II   
 $I_R^A = \frac{V}{Z}$        $Z' < Z$   
 $I_R^B = \frac{V}{Z'}$        $I_R^A < I_R^B$

$V_R^A < V_R^B$

$\text{So. } V_C^A > V_C^B$

$\therefore V_R^2 + V_C^2 = V_0^2$

- 17.** (C)  
**Sol.** The current lags the EMF by  $\pi/2$ , so the circuit should contain only an inductor.

- 18.** (A)  
**Sol.** Initially at resonance:  $X_L = X_E \Rightarrow Z = R$ .

$\therefore i_0 = \frac{\varepsilon_0}{R} = 10\sqrt{2} \text{ A}$

After increasing frequency:  $X_L > X_c$   
 $\omega L > 1/\omega C$

$\omega > \frac{1}{\sqrt{LC}} \Rightarrow \omega > \omega_0 \text{ (i.e. frequency increases)}$

$\text{and } i' = \frac{\varepsilon_0}{\sqrt{R^2 + X^2}} = \frac{\varepsilon_0}{\sqrt{2R}} = i_0 / \sqrt{2} = 10 \text{ amp.}$

- 19.** (B)  
**Sol.** Wattless current  $= I_{\text{rms}} \sin \phi$   
 Where  $\tan \phi = \frac{\omega L}{R} = \frac{2\pi f L}{R}$   
 and  $I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{V_{\text{rms}}}{\sqrt{R^2 + (\omega L)^2}}$

- 20.** (B)  
**Sol.** Resonance occurs in a series LCR circuit to an AC source at a specific frequency when the inductive reactance equals the capacitive reactance, resulting in the circuit's lowest impedance. At this frequency, the circuit draws maximum current from the source: thus, the maximum power is dissipated in the circuit. Therefore, Statement I is true.  
 In a circuit containing only a resistor, the power dissipated is given by.  
 $P = VI = I^2R$   
 The voltage and current are in phase in a purely resistive circuit, which maximizes the power. Therefore, Statement II is also true.  
 Therefore, the correct answer is Both Statement I and Statement II are true.

- 21.** 75  
**Sol.**  $P = V_{\text{rms}} I_{\text{rms}} \cos \phi$   
 $550 = 220 \times I_{\text{rms}} \times 0.8$   
 $\frac{2.5}{0.8} = I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{220}{Z}$   
 $Z = \frac{220 \times 8}{25}$   
 $\cos \phi = 0.8 = \frac{R}{Z}$   
 $\Rightarrow R = 0.8 \times \frac{44 \times 8}{5}$

$\sqrt{R^2 + X_L^2} = z = 1.25 R$

$R^2 + X_L^2 = \frac{25}{16} R^2$

$X_L^2 = \frac{9}{16} R^2$

$X_L = \frac{3R}{4} = \frac{1}{\omega C}$

$C = \frac{4}{3\omega R} = \frac{4}{3 \times 2\pi \times 50 \times 0.8 \times 44 \times 8}$   
 $= \frac{1}{3 \times 4 \times 44 \times 8 \times \pi} = 75.39 \mu\text{F}$

**22.** 0.36

**Sol.**  $C = C' \times 200 = 0.014 \times 200 = 2.8 \mu\text{S}$

$$L = \frac{1}{\omega^2 C} = \frac{1}{4\pi^2 f^2 C}$$

$$= \frac{1}{4\pi^2 \times (50 \times 10^3)^2 \times 22.8 \times 10^{-6}}$$

$$= 0.36 \times 10^{-3} \text{ H}$$

$$= 0.36 \text{ mH}$$

**23.** 400

**Sol.** The circuit is in resonance

$$i = \frac{200}{R} = 2 \text{ A}$$

$$P = i^2 R = 4 \times 100$$

$$= 400 \text{ W}$$

**24.** 4

**Sol.** R.M.S value of supply voltage,  $V = 200$  volts

Across resistance, rms voltage,  $V_R = \sqrt{(200)^2 - (120)^2} = 160$  Volts

$$\therefore \text{Current, } i = \frac{160}{40} = 4 \text{ Amperes}$$

**25.** 0.1

**Sol.**  $\frac{24}{10 \times 10^{-3}} = Z = \sqrt{(\omega L)^2 + R^2}$

$$\sqrt{R^2 + (\omega L)^2} = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$$

$$(\omega L) = -\omega L + \frac{1}{\omega C}$$

$$L = \frac{1}{2\omega^2 C} = \frac{1}{2 \times 100\pi \times 100\pi \times 10^{-6}} = 5 \text{ H}$$

$$(2400)^2 = (500\pi)^2 + R^2$$

$$R = \sqrt{(2400)^2 - (5\pi \times 100)^2}$$

$$= 100\sqrt{(24)^2 - 25\pi^2}$$

$$= 10 \times \sqrt{326} \approx 1800$$

$$I = 0.1 \text{ A}$$

**26.** 119

**Sol.**  $\tan \phi = \frac{\omega L_1}{R_1} = \frac{3}{4}$

$$\omega L_1 = \frac{3}{4} R_1$$

$$1 = \frac{100}{\sqrt{\frac{9}{16} R_1^2 + R_1^2}}$$

$$R_1 = 80 \Omega \quad \omega L_1 = 60 \Omega$$

$$\frac{\omega L_2}{R_2} = \frac{4}{3} \Rightarrow \omega L_2 = \frac{4}{3} R_2$$

$$5 = \frac{100}{\sqrt{\frac{16}{9} R_2^2 + R_2^2}} \Rightarrow R_2 = 12 \Omega ; \omega L_2 = 16 \Omega$$

$$Z = \sqrt{(\omega L_1 + \omega L_2)^2 + (R_1 + R_2)^2} = 119 \Omega$$

**27.** 3

**Sol.**  $V_R \cos \theta = 4\sqrt{3} \quad \theta = 30^\circ$

$$8 \cos \theta = 4\sqrt{3} \quad V_L^1 = V_L$$

$$= \cos (30^\circ - 30^\circ) = 3$$

**28.** 125

**Sol.**  $P_r = \frac{V_{\text{rms}}^2}{R}$  as at resonance  $Z = R$

$$= \frac{250 \times 250}{5} = 125 \times 10^2 \text{ W}$$

**29.** 3

**Sol.**  $\tan \phi \frac{|X_L - X_C|}{R}$

$$\Rightarrow X_C = X_L + R = 9 + 1 = 10 \Omega$$

$$C = \frac{1}{\omega X_C}$$

$$= \frac{1}{300 \times 10} = \frac{1}{3} \times 10^{-3} \text{ F}$$

**30.** 25

**Sol.** The total impedance is given by.

$$Z = \sqrt{R^2 (X_L - X_C)^2} = \sqrt{80^2 + (100 - 40)^2} = 100 \Omega$$

Therefore, the current in the circuit is given by.

$$\Rightarrow i_0 = \frac{V_0}{Z} = \frac{2500}{100} \text{ A} = 25 \text{ A}$$