

JEE MAIN ANSWER KEY & SOLUTIONS

SUBJECT :- PHYSICS

CLASS :- 12th

PAPER CODE :- CWT-10

CHAPTER :- SEMICONDUCTOR

ANSWER KEY



1. (C)	2. (C)	3. (A)	4. (A)	5. (B)	6. (A)	7. (C)
8. (D)	9. (C)	10. (D)	11. (A)	12. (B)	13. (A)	14. (A)
15. (C)	16. (C)	17. (C)	18. (A)	19. (B)	20. (B)	21. 5
22. 1250	23. 9	24. 2	25. 5	26. 14	27. 25	28. 120
29. 3	30. 25					

SOLUTIONS

1. (C)

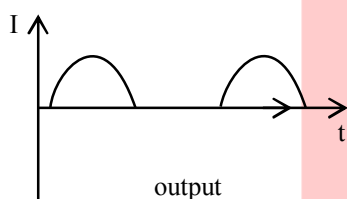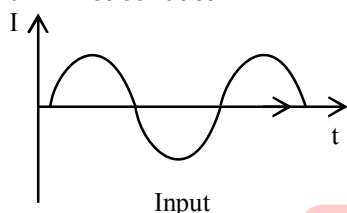
2. (C)

Sol. The diode will be forward biased in one half cycle and will conduct where as it will be reverse biased in negative half cycle and will not conduct.



3. (A)

Sol.

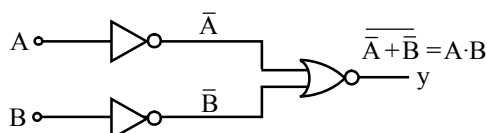

The out put will be of AND gate.

A	B	Y = A · B
0	0	0
0	1	0
1	0	0
1	1	1

The output will be high only when both the inputs are high hence correct .

4. (A)

Sol.

$$\alpha = \frac{I_c}{I_e} = \frac{I_c}{I_c + I_b} = 0.985$$

$$I_c = 0.985 (I_c + I_b)$$

$$I_c = 0.985 I_c + 0.985 I_b$$

$$0.985 I_b = 0.015 I_c = 0.015 \times 2 \text{ mA}$$

$$I_b = \frac{0.015 \times 2}{0.985} = 0.03 \text{ mA}$$

$$I_b \approx 0.03 \text{ mA}$$

5. (B)

Sol. $Y = \overline{\overline{A} \cdot \overline{B}} = A + B$ i.e. OR gate

6. (A)

Sol. Phosphorus is V group element.

7. (C)

Sol. n-type semi-conductor is neutral, net charge is zero.

8. (D)

Sol. $E = \frac{hc}{\lambda}$

$$\lambda = \frac{19.8 \times 10^{-26}}{1.10 \times 1.6 \times 10^{-19}} = 11284 \text{ \AA}$$

9. (C)

10. (D)

Sol. $E_{in} = \frac{\Delta V_b}{d} = \frac{0.6}{10^{-6}} = 6 \times 10^5 \text{ V/m}$

11. (A)

Sol. $I = \frac{V_{net}}{R_{net}} = \frac{8 - 0.5}{2.2 \times 10^{-3}} \text{ Amp.}$

$$= \frac{7.5}{2.2} \text{ mA} = 3.4 \text{ mA}$$

12. (B)

Sol. $\frac{A_P}{A_R} = \frac{\alpha^2 A_R}{A_R} = \alpha^2$

13. (A)

Sol. $\beta = \frac{\Delta I_C}{\Delta I_B} \Rightarrow \Delta I_C = \beta \times \Delta I_B = 80 \times 250 \mu\text{A}$

14. (A)

Sol. Upper diode is in forward bias,

$$\text{So, } i = V/R = 2V/20\Omega = 0.1 \text{ A}$$

15. (C)

16. (C)

Sol $\alpha = \frac{I_C}{I_E}, \beta = \frac{I_C}{I_B}, I_E = I_C + I_B, \frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$
 $\frac{I}{\alpha} = 1 + \frac{1}{\beta} \Rightarrow \alpha = \frac{\beta}{\beta + 1}$

17. (C)

Sol. $400 i_1 = 4$
 $i_2 = 10^{-2} \quad 400 i_3 = 4$
 $i_3 = 10^{-4}$
 $i = \frac{8}{400} = 2 \times 10^{-2}$
 $i_2 = 10^{-2}$
 $P = 4 \times 10^{-2}$
 $P = 40 \text{ mw}$

18. (A)

19. (B)

Sol. $I = \frac{5}{50} \text{ A}$

20. (B)

Sol. $P = VI \Rightarrow I = \frac{P}{V} = \frac{100}{0.5} \times 10^{-3}$
 $I = \frac{1}{5}$
 $I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{1.5 - 0.5}{R} = \frac{1}{R}$
 $R = 5$

21. 5

Sol. $VRC = ICRC$
 $0.6 = (IC)(600)$
 $IC = 1 \text{ mA}$
 $\frac{I_C}{\beta} = \frac{1 \text{ mA}}{20} = 0.5 \text{ mA}$
 $IB = \frac{1}{20} = 0.05 \text{ mA}$
 $0.5 \times 10 = 5$

22. 1250

Sol. $AP = AVB \therefore |A_V| = B \frac{R_0}{R_i}$
 $\therefore AP = \frac{A_V^2}{\left(\frac{R_0}{R_i}\right)} = \frac{(50)^2}{(200/100)} = \frac{2500}{2} = 1250$

23. 9


Sol. $I = n_e A v_d$
 $\frac{I_e}{I_h} = \frac{n_e \times (v_d)_e}{n_h \times (v_d)_h}$

Here, $\frac{n_e}{n_h} = \frac{7}{5}, \frac{I_e}{I_h} = \frac{7}{4}$

$\frac{7}{4} = \frac{7}{5} \times \frac{(v_d)_e}{(v_d)_h} \Rightarrow \frac{(v_d)_e}{(v_d)_h} = \frac{5}{4}$
 $= \frac{5}{7} \times \frac{7}{4} = \frac{m}{n}$

Here $m = 5$ & $n = 4$ then $m + n = 9$.

24. 2
Sol

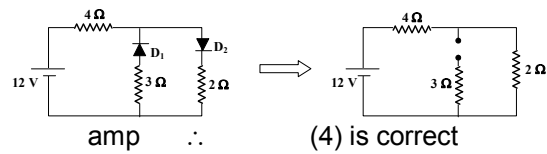

25. 5

Sol. $n_e n_h = n_i^2$
 $n_e = \frac{(1.5 \times 10^{16})^2}{4.5 \times 10^{22}} = 5 \times 10^9 / \text{m}^3 = 5$


26. 14
Sol. Conserving energy,

$\frac{1}{2} m v^2 = \frac{1}{2} m (6 \times 10^5)^2 - 0.4 \text{ eV}$
 $\Rightarrow v = \sqrt{(6 \times 10^5)^2 - \frac{2 \times 1.6 \times 10^{-19} \times 0.4}{9 \times 10^{-31}}}$
 $= \sqrt{36 \times 10^{10} - \frac{1.28}{9} \times 10^{12}}$
 $\Rightarrow v = \frac{14}{3} \times 10^5 \text{ m/s}$
 $\Rightarrow v = 14$

27. 25

Sol. $B = \frac{I_C}{I_B} \quad I_C = \frac{0.6}{1000} = 6 \times 10^{-4} \text{ A}$
 $24 = \frac{6 \times 10^{-4} \text{ A}}{I_B}$
 $I_B = \frac{1}{4} \times 10^{-4} \text{ A} = 25 \times 10^{-6} \text{ A}$

28. 120
Sol.

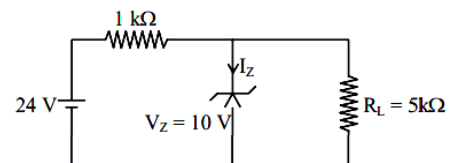

$i = \frac{10 \text{ V}}{5 \text{ k}\Omega} = 2 \text{ mA}$
 $I = \frac{14 \text{ V}}{1 \text{ k}\Omega} = 14 \text{ mA}$
 $\therefore I_Z = I_Z V_Z = 120 \text{ mW}$


29. 3

Sol. Energy corresponding to wavelength
4000Å

$$E = \frac{hc}{\lambda} = \frac{12400}{400}$$

$$= 3.1 \text{ eV} \approx 3 \text{ eV}$$

30. 25
Sol. Diode or forward biased

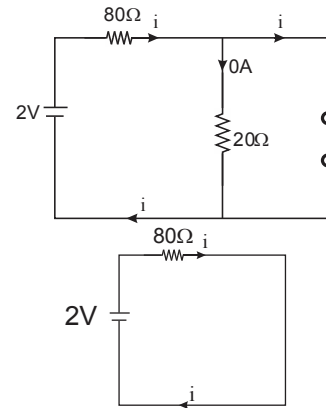

$$i = \frac{2}{80} = 0.025 \text{ A} = 25\text{mA}$$

PE