

NEET ANSWER KEY & SOLUTIONS

SUBJECT :- PHYSICS

CLASS :- 12th

CHAPTER :- CAPACITANCE

PAPER CODE :- CWT-2

ANSWER KEY											
1.	(C)	2.	(C)	3.	(B)	4.	(A)	5.	(B)	6.	(B)
8.	(C)	9.	(C)	10.	(B)	11.	(D)	12.	(C)	13.	(A)
15.	(C)	16.	(C)	17.	(B)	18.	(A)	19.	(A)	20.	(D)
22.	(A)	23.	(B)	24.	(C)	25.	(D)	26.	(B)	27.	(C)
29.	(B)	30.	(B)	31.	(B)	32.	(D)	33.	(A)	34.	(D)
36.	(A)	37.	(D)	38.	(C)	39.	(B)	40.	(C)	41.	(C)
43.	(D)	44.	(C)	45.	(A)	46.	(A)	47.	(B)	48.	(B)
50.	(B)										

SOLUTIONS

SECTION-A

1. (C)

Sol. Battery is disconnected so Q will be constant as $C \propto K$. So with introduction of dielectric slab capacitance will increase using $Q = CV$, V will decrease and using $U = \frac{Q^2}{2C}$, energy will decrease.

2. (C)

3. (B)

Sol. $U = \int_0^V CV dV = \frac{1}{2} CV^2$

4. (A)

Sol. $U = \frac{1}{2} CV^2 = \frac{1}{2} \times 50 \times 10^{-6} \times (10)^2 = 2.5 \times 10^{-3} J$

5. (B)

6. (B)

Sol. $C_{medium} = K \times C_{air}$

7. (B)

Sol. By using $V_{big} = n^{2/3} V_{small}$

$$\Rightarrow \frac{V_{Big}}{V_{small}} = (8)^{2/3} = \frac{4}{1}$$

8. (C)

Sol. $W = \frac{Q^2}{2C} \Rightarrow W = 4W$

9. (C)

Sol. Because the charges are produced due to induction and moreover the net charge of the condenser should be zero.

10. (B)

Sol. Initially $F = qE$ and $E = \frac{\sigma}{\epsilon_0}$ $\therefore F = \frac{q\sigma}{\epsilon_0}$
If one plate is removed, then E becomes $\frac{\sigma}{2\epsilon_0}$
So $F = \frac{q\sigma}{2\epsilon_0} = \frac{F}{2}$

11. (D)

Sol. In this process capacity increases, so battery supplies additional charge to capacitor.

13. (A)

Sol. Initially when key is closed, the capacitor acts as short-circuit, so bulb will light up. But finally the capacitor becomes fully charged, so it will act as open circuit, so bulb will not glow.

14. (B)

Sol. $C = \frac{K\epsilon_0 A}{d}; \therefore \frac{C_1}{C_2} = \frac{K_1}{K_2} \Rightarrow \frac{C}{C_2} = \frac{5}{20} \Rightarrow C_2 = 4C$

15. (C)


Sol. $\Delta V = \frac{1}{2} \frac{C \times C}{(C+C)} |V - (-V)|^2 = CV^2$

16. (C)

Sol. Initially charge on the capacitor $Q = 10 \times 12 = 120 \mu C$
Finally charge on the capacitor $Q' = (5 \times 10) \times 12 = 600 \mu C$
So charge supplied by the battery later $= Q' - Q = 480 \mu C$

17.	(B)		29.	(B)
Sol.	(B) The energy stored $= \frac{1}{2} QV$		Sol.	Power
18.	(A)			$= \frac{\frac{1}{2} CV^2}{t} = \frac{1 \times 40 \times 10^{-6} \times (3000)^2}{2 \times 2 \times 10^{-3}} = 90 \text{ kW}$
Sol.	$U = \frac{1}{2} CV^2 = \frac{1}{2} \times 12 \times 10^{-12} \times (50)^2$ $= 1.5 \times 10^{-8} \text{ J}$		30.	(B)
19.	(A)		31.	(B)
Sol.	$C = \frac{\epsilon_0 KA}{d} \Rightarrow \frac{C_1}{C_2} = \frac{K_1}{K_2} \times \frac{d_2}{d_1}$ $\frac{2}{C_2} = \frac{1}{2.8} \times \frac{(0.4 / 2)}{(0.4)} \Rightarrow C_2 = 11.2 \mu\text{F}$		Sol.	In general electric field between the plates of a charged parallel plate capacitor is given by $E = \frac{\sigma}{\epsilon_0 K}$
20.	(D)		32.	(D)
21.	(C)		Sol.	$Q_1 = 10^{-2} \text{ C}$, $Q_2 = 5 \times 10^{-2} \text{ C}$
Sol.	$C \propto \frac{1}{d} \Rightarrow \frac{C_1}{C_2} = \frac{d_2}{d_1} \text{ so } \frac{C_2}{10} = \frac{8}{4} \Rightarrow C_2 = 20 \mu\text{F}$			Total charge of the system $Q = 6 \times 10^{-6} \text{ C}$
22.	(A)			Charge on small sphere
Sol.	Energy density			$Q'_1 = \frac{Q r_1}{r_1 + r_2} = \frac{6 \times 10^{-2} \times 1}{1 + 2} = 2 \times 10^{-2} \text{ C}$
	$= \frac{1}{2} \epsilon_0 E^2 = \frac{1}{2} \epsilon_0 \left(\frac{\sigma}{\epsilon_0} \right)^2 = \frac{\sigma^2}{2\epsilon_0} = \frac{q^2}{2\epsilon_0 A^2}$		33.	(A)
23.	(B)		Sol.	When a lamp is connected to D.C. line with a capacitor. It will form an open circuit. Hence, the lamp will not glow.
Sol.	$U = \frac{Q^2}{2C} = \frac{(40 \times 10^{-6})^2}{2 \times 10^{-6} \times 10} = \frac{16 \times 10^{-10}}{2 \times 10^{-5}} = 8 \times 10^{-5} \text{ J}$ $= 8 \times 10^{-5} \times 10^7 = 800 \text{ erg}$		34.	(D)
24.	(C)		Sol.	$Q_1 = CV$ and $Q_2 = CV$
Sol.	Capacitance with dielectric $C_{medium} = \frac{K\epsilon_0 A}{d}$			Applying charge conservation
	$\Rightarrow C_{medium} \propto \frac{K}{d}$			$CV_1 + CV_2 = Q_1 + Q_2$
25.	(D)			$CV_1 + CV_2 = 2CV \Rightarrow V_1 + V_2 = 2V$
Sol.	$U = \frac{1}{2} CV^2 = \frac{1}{2} 5 \times 10^{-6} \times (20 \times 10^3)^2 = 1 \text{ kJ}$		35.	(C)
26.	(B)		Sol.	The given arrangement becomes an arrangement of $(n-1)$ capacitors connected in parallel. So $C_R = (n-1)C$
Sol.	$U = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} (nC) V^2$			
27.	(C)			
Sol.	$C = \frac{\epsilon_0 A}{d} \Rightarrow \epsilon_0 = \frac{Cd}{A} \Rightarrow \epsilon_0 \rightarrow$ $\frac{\text{Farad} \times \text{m}}{\text{m}^2} \rightarrow \frac{F}{m}$			
28.	(B)			
Sol.	$V = n^{2/3} v = (8)^{2/3} v = 4v \text{ i.e. 4 times.}$			

SECTION-B

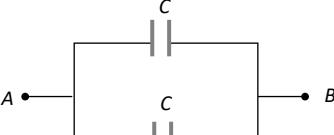
36. (A)
- Sol. The given circuit is equivalent to a parallel combination two identical capacitors
Hence equivalent capacitance between A and B is
- 

$$C = \frac{\epsilon_0 A}{d} + \frac{\epsilon_0 A}{d}$$

$$= \frac{2\epsilon_0 A}{d}$$

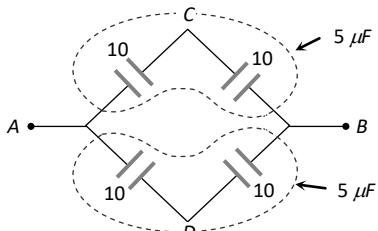37. (D)

Sol. In the given system, no current will flow through the branch CD so it can be removed



Effective capacitance of the system
 $= 5 + 5 = 10 \mu F$

38. (C)

Sol. $C_R = C_1 + C_2 = \frac{k_1 \epsilon_0 A_1}{d} + \frac{k_2 \epsilon_0 A_2}{d}$

$$= \frac{2 \times \epsilon_0 \frac{A}{2}}{d} + \frac{4 \times \epsilon_0 \frac{A}{2}}{d} = 2 \times \frac{10}{2} + 4 \times \frac{10}{2} = 30 \mu F$$

39. (B)

Sol. Total capacitance of given system

$$C_{eq} = \frac{8}{5} \mu F$$

$$U = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \times \frac{8}{5} \times 10^{-6} \times 225 = 180 \times 10^{-6} J$$
$$= 180 \times 10^{-6} \times 10^7 erg = 1800 erg$$

40. (C)

Sol. $\frac{1}{C_R} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

$$\Rightarrow C_R = (C_1^{-1} + C_2^{-1} + C_3^{-1})^{-1}$$

41. (C)

Sol. $C_1 = 2C$ and $C_2 = C/2$, so $C_1/C_2 = 4:1$


42. (A)

Sol. In parallel combination $V_1 = V_2$

$$\text{or } \frac{q_1}{C_1} = \frac{q_2}{C_2} \Rightarrow \frac{q_1}{q_2} = \frac{C_1}{C_2}$$

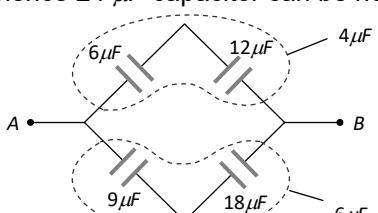43. (D)

Sol. Given circuit can be drawn as follows. It is a balance whetstone bridge type network, hence $24 \mu F$ capacitor can be neglected



Equivalent capacitance between A and $B = 4 + 6 = 10 \mu F$.


44. (C)

Sol. Equivalent capacitance of parallel combination is $C_p = C_1 + C_2 + C_3$.

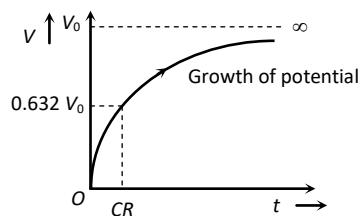
45. (A)

Sol. For charging of capacitor $q = q_0 \left(1 - e^{-\frac{t}{CR}} \right)$

and potential difference $V = V_0 \left(1 - e^{-\frac{t}{CR}} \right)$



46. (A)

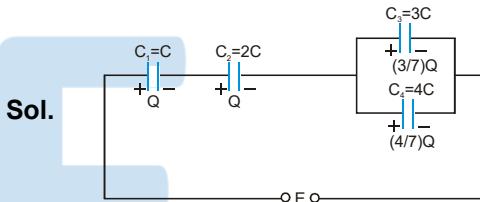

At $C_1 = V_1 = \frac{Q}{C}$ and $U_1 = \frac{Q^2}{2C}$


At $C_2 = V_2 = \frac{Q}{2C}$ and $U_2 = \frac{Q^2}{4C}$

At $C_3 = V_3 = \frac{Q}{7C}$ and $U_3 = \frac{3Q^2}{98C}$

At $C_4 = V_4 = \frac{Q}{7C}$ and $U_4 = \frac{4Q^2}{98C}$

Therefore $V_{max} = V_1$ and $V_{min} = V_3 = V_4$ and $U_{max} = U_1$ and $U_{min} = U_3$

47. (B)

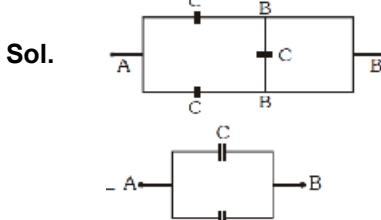

(one capacitor gets short)

$$\Rightarrow C_{eq} = C_1 + C_2 = C + C = 2C$$

48. (B)

49. (B)

Sol. Force between plates of parallel capacitor,

$$F = qE = q \left[\frac{\sigma}{2\epsilon_0} \right]$$

$$\therefore \text{Surface charge density } \sigma = \frac{q}{A}$$

$$\therefore F = q \left[\frac{q}{2A\epsilon_0} \right] \Rightarrow F = \frac{q^2}{2A\epsilon_0}$$

So, net charge across a capacitor, $q = CV$

$$F = \frac{C^2 V^2}{2A\epsilon_0} \left[C = \frac{A\epsilon_0}{d} \right]$$

$$\Rightarrow F = \frac{\left(\frac{A\epsilon_0}{d} \right) \times CV^2}{2A\epsilon_0} = \frac{CV^2}{2d}$$

P

50. (B)

Sol. Energy stored, in parallel plate capacitor is given by

$$U = \frac{1}{2} \frac{q^2}{C}$$

$$\text{but } \sigma = \frac{q}{A} \text{ and } C = \frac{\epsilon_0 A}{d}$$

$$\therefore U = \frac{1}{2} \frac{(\sigma A)^2}{\left(\frac{\epsilon_0 A}{d} \right)}$$

$$\text{or } = \frac{A\sigma^2 d}{2\epsilon_0}$$

$$\text{or } = \frac{1}{2} \left(\frac{\sigma}{\epsilon_0} \right)^2 \times \epsilon_0 Ad$$

$$\text{or } U = \frac{1}{2} E^2 \epsilon_0 Ad$$

Energy stored per unit volume i.e. energy density is thus given by

$$u = \frac{U}{V} = \frac{U}{Ad} = \frac{1}{2} \epsilon_0 E^2$$

$$\Rightarrow = \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2 = \frac{1}{2} \epsilon_0 \frac{V^2}{d^2}$$

E