

NEET : CHAPTER WISE TEST-3

SUBJECT :- PHYSICS

CLASS :- 12th


CHAPTER :- CURRENT ELECTRICITY

DATE.....


NAME.....

SECTION.....

(SECTION-A)

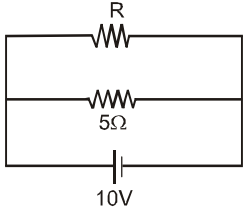
1. The temperature coefficient of resistance for a wire is $0.00125 / ^\circ C$. At 300K its resistance is 1 ohm. The temperature at which the resistance becomes 2 ohm is
 (A) 1154 K (B) 1100 K
 (C) 1400 K (D) 1127 K
2. The resistivity of a wire
 (A) Increases with the length of the wire
 (B) Decreases with the area of cross-section
 (C) Decreases with the length and increases with the cross-section of wire
 (D) None of the above statement is correct
3. Ohm's law is true
 (A) For metallic conductors at low temperature
 (B) For metallic conductors at high temperature
 (C) For electrolytes when current passes through them
 (D) For diode when current flows
4. The specific resistance of a wire is ρ , its volume is $3 m^3$ and its resistance is 3 ohms, then its length will be
 (A) $\sqrt{\frac{1}{\rho}}$ (B) $\frac{3}{\sqrt{\rho}}$
 (C) $\frac{1}{\rho}\sqrt{3}$ (D) $\rho\sqrt{\frac{1}{3}}$
5. The resistance of a wire of uniform diameter d and length L is R . The resistance of another wire of the same material but diameter $2d$ and length $4L$ will be
 (A) $2R$ (B) R
 (C) $R/2$ (D) $R/4$
6. There is a current of 1.344 amp in a copper wire whose area of cross-section normal to the length of the wire is $1 mm^2$. If the number of free electrons per cm^3 is 8.4×10^{22} , then the drift velocity would be
 (A) 1.0 mm / sec (B) 1.0 m / sec
 (C) 0.1 mm / sec (D) 0.01 mm / sec
7. The power dissipated in the circuit shown in the figure is 30 Watts. The value of R is :

 (A) 20 Ω (B) 15 Ω
 (C) 10 Ω (D) 30 Ω
8. A certain piece of silver of given mass is to be made like a wire. Which of the following combination of length (L) and the area of cross-sectional (A) will lead to the smallest resistance
 (A) L and A
 (B) $2L$ and $A/2$
 (C) $L/2$ and $2 A$
 (D) Any of the above, because volume of silver remains same
9. The resistance of a wire is 10Ω . Its length is increased by 10% by stretching. The new resistance will now be
 (A) 12 Ω (B) 1.2 Ω
 (C) 13 Ω (D) 11 Ω
10. The resistance of a wire is R . If the length of the wire is doubled by stretching, then the new resistance will be
 (A) $2R$ (B) $4R$
 (C) R (D) $\frac{R}{4}$
11. The resistivity of a wire depends on its
 (A) Length
 (B) Area of cross-section
 (C) Shape
 (D) Material
12. σ_1 and σ_2 are the electrical conductivities of Ge and Na respectively. If these substances are heated, then
 (A) Both σ_1 and σ_2 increase
 (B) σ_1 increases and σ_2 decreases
 (C) σ_1 decreases and σ_2 increases
 (D) Both σ_1 and σ_2 decrease

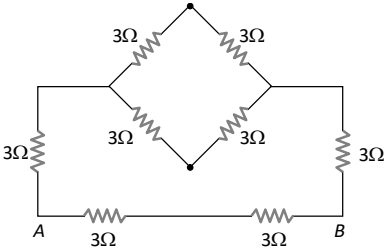13. Masses of three wires of copper are in the ratio of 1 : 3 : 5 and their lengths are in the ratio of 5 : 3 : 1. The ratio of their electrical resistances are
 (A) 1 : 3 : 5 (B) 5 : 3 : 1
 (C) 1 : 15 : 125 (D) 125 : 15 : 1
14. The charge of an electron is 1.6×10^{-19} C. How many electrons strike the screen of a cathode ray tube each second when the beam current is 16 mA
 (A) 10^{17} (B) 10^{19}
 (C) 10^{-19} (D) 10^{-17}
15. A nichrome wire 50 cm long and one square millimetre cross-section carries a current of 4A when connected to a 2V battery. The resistivity of nichrome wire in ohm metre is
 (A) 1×10^{-6} (B) 4×10^{-7}
 (C) 3×10^{-7} (D) 2×10^{-7}
16. What length of the wire of specific resistance $48 \times 10^{-8} \Omega m$ is needed to make a resistance of 4.2Ω (diameter of wire = 0.4 mm)
 (A) 4.1 m (B) 3.1 m
 (C) 2.1 m (D) 1.1 m
17. We have two wires A and B of same mass and same material. The diameter of the wire A is half of that B. If the resistance of wire A is 24 ohm then the resistance of wire B will be
 (A) 12 Ohm
 (B) 3.0 Ohm
 (C) 1.5 Ohm
 (D) None of the above
18. The lead wires should have
 (A) Larger diameter and low resistance
 (B) Smaller diameter and high resistance
 (C) Smaller diameter and low resistance
 (D) Larger diameter and high resistance
19. The electric field E , current density J and conductivity σ of a conductor are related as
 (A) $\sigma = E / j$ (B) $\sigma = j / E$
 (C) $\sigma = jE$ (D) $\sigma = 1 / jE$
20. There are 8 equal resistances R . Two are connected in parallel, such four groups are connected in series, the total resistance of the system will be
 (A) $R / 2$ (B) $2 R$
 (C) $4 R$ (D) $8 R$

21. Equivalent resistance between A and B will be
- 
- (A) 2 ohm (B) 18 ohm
 (C) 6 ohm (D) 3.6 ohm
22. A wire has a resistance of 12 ohm. It is bent in the form of equilateral triangle. The effective resistance between any two corners of the triangle is
 (A) 9 ohms (B) 12 ohms
 (C) 6 ohms (D) $8/3$ ohms
23. Lamps used for household lighting are connected in
 (A) Series
 (B) Parallel
 (C) Mixed circuit
 (D) None of the above
24. The equivalent resistance of resistors connected in series is always
 (A) Equal to the mean of component resistors
 (B) Less than the lowest of component resistors
 (C) In between the lowest and the highest of component resistors
 (D) Equal to sum of component resistors
25. Four wires of equal length and of resistances 10 ohms each are connected in the form of a square. The equivalent resistance between two opposite corners of the square is
 (A) 10 ohm (B) 40 ohm
 (C) 20 ohm (D) $10/4$ ohm
26. Three resistances, each of 1 ohm, are joined in parallel. Three such combinations are put in series, then the resultant resistance will be
 (A) 9 ohm (B) 3 ohm
 (C) 1 ohm (D) $\frac{1}{3}$ ohm
27. Two wires of same metal have the same length but their cross-sections are in the ratio 3 : 1. They are joined in series. The resistance of the thicker wire is 10Ω . The total resistance of the combination will be
 (A) 40Ω (B) $\frac{40}{3} \Omega$
 (C) $\frac{5}{2} \Omega$ (D) 100Ω


28. Three resistances $4\ \Omega$ each of are connected in the form of an equilateral triangle. The effective resistance between two corners is
 (A) $8\ \Omega$ (B) $12\ \Omega$
 (C) $\frac{3}{8}\ \Omega$ (D) $\frac{8}{3}\ \Omega$

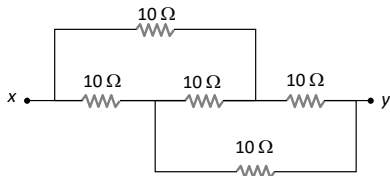29. The equivalent resistance between x and y in the circuit shown is



- (A) $10\ \Omega$ (B) $40\ \Omega$
 (C) $20\ \Omega$ (D) $\frac{5}{2}\ \Omega$

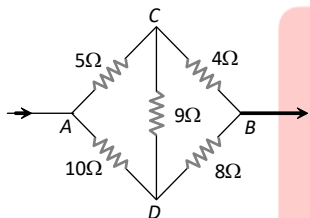30. Five resistors are connected as shown in the diagram. The equivalent resistance between A and B is



- (A) $6\ \text{ohm}$ (B) $9\ \text{ohm}$
 (C) $12\ \text{ohm}$ (D) $15\ \text{ohm}$

31. If three resistors of resistance $2\ \Omega$, $4\ \Omega$ and $5\ \Omega$ are connected in parallel then the total resistance of the combination will be
 (A) $\frac{20}{19}\ \Omega$ (B) $\frac{19}{20}\ \Omega$
 (C) $\frac{19}{10}\ \Omega$ (D) $\frac{10}{19}\ \Omega$

32. When a wire of uniform cross-section a , length l and resistance R is bent into a complete circle, resistance between any two of diametrically opposite points will be
 (A) $\frac{R}{4}$ (B) $\frac{R}{8}$
 (C) $4R$ (D) $\frac{R}{2}$

33. Kirchoff's first law *i.e.* $\sum i = 0$ at a junction is based on the law of conservation of
 (A) Charge
 (B) Energy
 (C) Momentum
 (D) Angular momentum

34. A $50V$ battery is connected across a $10\ \text{ohm}$ resistor. The current is $4.5\ \text{amperes}$. The internal resistance of the battery is
 (A) Zero (B) $0.5\ \text{ohm}$
 (C) $1.1\ \text{ohm}$ (D) $5.0\ \text{ohm}$

35. A cell whose e.m.f. is $2\ V$ and internal resistance is $0.1\ \Omega$, is connected with a resistance of $3.9\ \Omega$. The voltage across the cell terminal will be
 (A) $0.50\ V$ (B) $1.90\ V$
 (C) $1.95\ V$ (D) $2.00\ V$

(SECTION-B)

36. The reading of a high resistance voltmeter when a cell is connected across it is $2.2\ V$. When the terminals of the cell are also connected to a resistance of $5\ \Omega$ the voltmeter reading drops to $1.8\ V$. Find the internal resistance of the cell
 (A) $1.2\ \Omega$ (B) $1.3\ \Omega$
 (C) $1.1\ \Omega$ (D) $1.4\ \Omega$

37. Electromotive force is the force, which is able to maintain a constant
 (A) Current
 (B) Resistance
 (C) Power
 (D) Potential difference

38. Kirchoff's I law and II law of current, proves the
 (A) Conservation of charge and energy
 (B) Conservation of current and energy
 (C) Conservation of mass and charge
 (D) None of these


39. A milli voltmeter of 25 milli volt range is to be converted into an ammeter of 25 ampere range. The value (in ohm) of necessary shunt will be :
 (A) 0.001 (B) 0.01
 (C) 1 (D) 0.05

40. To convert a galvanometer into a voltmeter, one should connect a
 (A) High resistance in series with galvanometer
 (B) Low resistance in series with galvanometer
 (C) High resistance in parallel with galvanometer
 (D) Low resistance in parallel with galvanometer

41. Resistance of $100\ \text{cm}$ long potentiometer wire is $10\ \Omega$, it is connected to a battery ($2\ \text{volt}$) and a resistance R in series. A source of $10\ \text{mV}$ gives null point at $40\ \text{cm}$ length, then external resistance R is
 (A) $490\ \Omega$ (B) $790\ \Omega$
 (C) $590\ \Omega$ (D) $990\ \Omega$

42. The current flowing in a coil of resistance $90\ \Omega$ is to be reduced by 90%. What value of resistance should be connected in parallel with it
 (A) $9\ \Omega$ (B) $90\ \Omega$
 (C) $1000\ \Omega$ (D) $10\ \Omega$

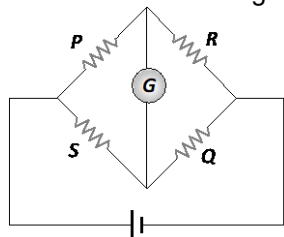
43. In the circuit given, the correct relation to a balanced Wheatstone bridge is



- (A) $\frac{P}{Q} = \frac{R}{S}$ (B) $\frac{P}{Q} = \frac{S}{R}$
 (C) $\frac{P}{R} = \frac{S}{Q}$ (D) None of these


44. In an electrical cable there is a single wire of radius $9\ \text{mm}$ of copper. Its resistance is $5\ \Omega$. The cable is replaced by 6 different insulated copper wires, the radius of each wire is $3\ \text{mm}$. Now the total resistance of the cable will be
 (A) $7.5\ \Omega$ (B) $45\ \Omega$
 (C) $90\ \Omega$ (D) $270\ \Omega$

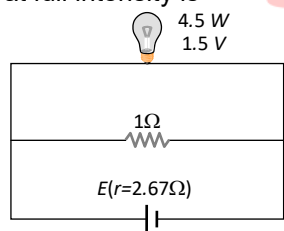45. A torch bulb rated as $4.5\ \text{W}$, $1.5\ \text{V}$ is connected as shown in the figure. The *e.m.f.* of the cell needed to make the bulb glow at full intensity is



- (A) $4.5\ \text{V}$ (B) $1.5\ \text{V}$
 (C) $2.67\ \text{V}$ (D) $13.5\ \text{V}$

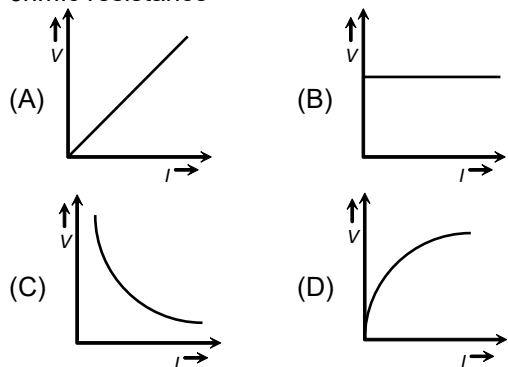
46. Which of the adjoining graphs represents *ohmic* resistance



47. Assertion : The drift velocity of electrons in a metallic wire will decrease, if the temperature of the wire is increased.

Reason : On increasing temperature, conductivity of metallic wire decreases.

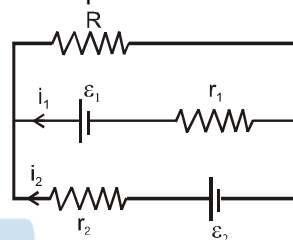- (A) If both assertion and reason are true and the reason is the correct explanation of the assertion.
 (B) If both assertion and reason are true but reason is not the correct explanation of the assertion.
 (C) If assertion is true but reason is false.
 (D) If the assertion and reason both are false.
48. See the electrical circuit shown in this figure. Which of the following equations is a correct equation for it ?



- (A) $\varepsilon_1 - (i_1 + i_2)R - i_1 r_1 = 0$
 (B) $\varepsilon_2 - i_2 r_2 - \varepsilon_1 - i_1 r_1 = 0$
 (C) $-\varepsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$
 (D) $\varepsilon_1 - (i_1 + i_2)R + i_1 r_1 = 0$

49. By ammeter, which of the following can be measured

- (A) Electric potential
 (B) Potential difference
 (C) Current
 (D) Resistance

50. **Column-I** gives certain physical terms associated with flow of current through a metallic conductor.

Column-II Gives some mathematical relations involving electrical quantities. Match

Column-I and **Column-II** with appropriate relations.

- | Column-I | Column-II |
|--------------------------------|--------------------------|
| (A) Drift Velocity | (P) $\frac{m}{ne^2\rho}$ |
| (B) Electrical Resistivity (Q) | (Q) neV_d |
| (C) Relaxation Period (R) | (R) $\frac{eE}{m}\tau$ |
| (D) Current Density (S) | (S) $\frac{E}{J}$ |
- (A) (A)-(R), (B)-(Q), (C)-(S), (D)-(P)
 (B) (A)-(R), (B)-(S), (C)-(P), (D)-(Q)
 (C) (A)-(R), (B)-(S), (C)-(Q), (D)-(P)
 (D) (A)-(R), (B)-(P), (C)-(S), (D)-(Q)